



A circuit consists of b branches and n nodes. A direct algebraic approach : 2b method Example. R_6 b₆ \sim <u>b</u>4 b₅ В B С Α R_5 R_4 b_2 ${}_{R_2}$ b₁ E_1 ·E₃ b₃ D C.T. Pan









Just enough information to find the solution.

Problem : Too many variables !!

C.T. Pan

It is not efficient !

Question : Is it possible to find an optimal

method with minimum unknowns?

n Nodal analysis is based on a systematic application of KCL and is a general method.

n Mesh Analysis is based on a systematic application of KVL and can be used for planar circuits only.

C.T. Pan

C.T. Pan

4.1 Introduction

n Fundamental loop analysis is based on a systematic application of KVL to the fundamental loops. It requires the definition of tree.

n Fundamental cutset analysis is based on a systematic application of KCL to the fundamental cutsets. It also requires the definition of tree.

10

n Node: A point where two or more elements join
n Path: A trace of adjoining basic elements with no elements included more than once
n Branch: A path that connects two nodes
n Essential node: A node where three or more elements join
n Essential branch: A path that connects two essential nodes without passing through an essential node

4.1 Introduction

n Loop: A path whose last node is the same as the starting node

n Mesh: A loop that does not enclose any other loops

n Planar circuit: A circuit that can be drawn on a plane with no crossing branches









For each oriented graph \hat{G} one can construct a *tree T*.

A tree T of \hat{G} is a connected graph which (a) contains all the nodes.

(b) without forming any loop.

The branches which do not belong to tree T are called *links*.

Each tree branch defines a unique cutset (or super node), called fundamental cutset.

C.T. Pan

C.T. Pan

4.1 Introduction

Each link together with its unique path connecting the two nodes of the link defines a unique loop , called fundamental loop.

A network with b branches, *n* nodes, and *l* links will satisfy the fundamental theorem of network topology :

$$\underline{b=l+n-1}$$

Theorem

C.T. Pan

C.T. Pan

Given a connected graph G of n nodes and b branches, and a tree T of G

n There is unique path along the tree between any pair of nodes.

n There are n-1 tree branches and b-(n-1) links.

4.1 Introduction

- n Every link of T and the unique tree path between its nodes constitute a unique loop, called the fundamental loop associated with the link.
- n Every tree branch of T together with some links defines a unique cut set of G, called the fundamental cut set associated with the tree branch.









Example 4.1.5



n=5 , b=8 T₂ = { b_5 , b_6 , b_7 , b_8 }

Fundamental cut sets :

Cut set of $b_5 = \{b_1, b_2, b_5\}$ Cut set of $b_6 = \{b_2, b_3, b_6\}$ Cut set of $b_7 = \{b_3, b_4, b_7\}$ Cut set of $b_8 = \{b_1, b_4, b_8\}$

Choose tree branch current direction as reference. Cut only one tree branch.





- Instead of using branch voltages and branch currents as unknowns, one can choose nodal voltages as unknowns. Only n-1 nodal voltages are required.
- n Each branch voltage can be obtained from nodal voltages and the corresponding branch currents can be calculated by its component model.
- n KVL is automatically satisfied.

n One need only find the independent KCL equations, and the component model is used to express the branch current in terms of nodal voltages.

 $G\underline{e} = \underline{I}_s$

C.T. Pan

n Any unknown can be calculated once the nodal voltage vector is solved.

29



















Example 4.2.3. (Case 2A) (trivial case)





Example 4.2.4. (Case 2B) (supernode)



$$A C C C P C C P C C P C C C P C C C P C C C P C C P C C P C C P C C P C C P C C P C P C P C C P$$





Example 4.2.5 (Case 2C)





4.2 The Node-Voltage Method For the supernode containing nodes a and b: $e_b(1) + (e_b - e_c)2 + (e_a - e_c)3 = 1A + 2A \dots (1)$ For node c: $(e_c - e_b)2 + e_c(4) + (e_c - e_a)3 = 0 \dots (2)$























(c) A mesh in a planar circuit is a loop that does not contain any other loop within it.

(d) Instead of choosing branch currents as unknown variables, one can choose mesh currents as unknown variables to reduce the number of equations which must be solved simultaneously.

58







































For this case with dependent source, we need one more step, namely to express the controlling parameter I_0 in terms of mesh currents.

$$\mathbf{I}_0 = -i_4 \tag{E}$$

Substitute (C), (D), and (E) into (A) and (B) :

 $[i_4 - (i_1 + 5 + 3i_4)]*8 + i_4*2 = -10$

$$(i_1 + 5)*6 + i_1*2 + (i_1 + 5 + 3i_4)*4 + [(i_1 + 5 + 3i_4) - i_4]*8=0$$























(1) First consideration: choose the method which contains minimum number of unknowns that requires simultaneous solution. For a circuit contains b branches, n nodes, among them there are m_v voltage sources and m_i current sources, including dependent source, then the number of unknowns to be solved simultaneously is $n-1-m_v$: for nodal analysis $b-(n-1)-m_i$: for mesh analysis

89

90

C T Pan

C.T. Pan

4.3 The Mesh Current Method

(2)Second consideration: Depends on the solution required, if nodal voltages are required, it may be expedient to use nodal analysis. If branch or mesh currents are required it may be better to use mesh analysis.



- n Two other variations besides nodal and mesh analysis are introduced, namely the fundamental loop analysis and the fundamental cutset analyses.
- n They are useful for understanding how to write the state equation of a circuit.

91

92

4.4 Fundamental Loop Analysis

<u>Theorem</u>

C.T. Pan

C.T. Pan

Given an oriented graph G of n nodes and b branches, and a tree T of G, then

- 1. Between any pair of nodes there is a unique path along the tree.
- 2. There are n-1 tree branches and b-n+1 links.

4.4 Fundamental Loop Analysis Theorem

- 3. Every link of T and the corresponding unique tree path between its two terminals constitute a unique loop, called the fundamental loop associated with this link.
- 4. Every tree branch of T together with some links defines a unique cutset of G, called the fundamental cutset associated with this tree branch.





4.4 Fundamental Loop Analysis



<u>Step 1</u>

Pick an arbitrary tree T. Number the links from 1 to | and then tree branches from | +1 to b.

95

96

4.4 Fundamental Loop Analysis

<u>Step 2</u>

C.T. Pan

Choose link currents J1, J2, J3 as unknowns and adopt each link current direction as the reference of the corresponding fundamental loop current.

Write down KVL equations for the **l** fundamental loops.









4.4 Fundamental Loop Analysis Step 5

Solve equation (D) and calculate I_B and V_B .

Note that

C.T. Pan

C.T. Pan

- 1. Link currents are used as the unknowns.
- 2. The number of links is the same as that of the mesh currents. Because they are all optimal methods in terms of using minimum number of unknown current variables.



- 3. The resulting circuit loop equations depend on the choice of a tree.
- 4. Compared with mesh analysis, the fundament loop analysis is more general, i.e. not restricted to planar circuits, but requires defining a tree.

102

4.5 Fundamental Cutset Analysis

Use the same example as an demonstration.



Given the oriented graph G.

Step 1

Pick a tree T. Number the links from 1 to | and then tree branches from |+1 to b.

104

4.5 Fundamental Cutset Analysis

Step 2

C.T. Pan

Choose the tree branch voltages e_1 , e_2 , e_3 as unknowns and adopt the tree branch current as the reference direction of the associated fundamental cutset. Write down KCL equations for the n-1 fundamental cutsets.

Cutset 1 for branch 4
$$\Rightarrow$$
 $i_4 + i_1 + i_2$
Cutset 2 for branch 5 \Rightarrow $i_5 + i_1 - i_3 =$
Cutset 3 for branch 6 \Rightarrow $i_6 + i_2 + i_3$









4.5 Fundamental Cutset Analysis Step 5

Solve equation (D) and calculate I_B and V_B .

Note that

- 1. Tree branch voltages are used as unknowns.
- 2. The number of tree branches is the same as that of the nodal analysis. Because they are all optimal methods in terms of using minimum number of unknown voltages.



Summary <u>Table 1</u> Comparison of Nodal and Fundamental Cutset Analyses						
	Methods	Nodal Analysis	Fundamental Cutset Analysis			
	KCL	$NI_{B} = 0$	$CI_{B} = 0$			
	KVL	$V_{\scriptscriptstyle B} = N^{\scriptscriptstyle T} e$	$V_{\rm B} = C^{\rm T} e_{\rm t}$			
	Component Model	$I_{\scriptscriptstyle B} = I_{\scriptscriptstyle S} + [G](V_{\scriptscriptstyle B} - V_{\scriptscriptstyle S})$	$I_{\scriptscriptstyle B} = I_{\scriptscriptstyle S} + [G](V_{\scriptscriptstyle B} - V_{\scriptscriptstyle S})$			
		Ax = b	Ax = b			
	Equation to be Solved	$A = N[G]N^{T}$	$A = C[G]C^{T}$			
		$b = N[G]V_s - NI_s$	$b = C[G]V_s - CI_s$			
		x = e	$x = e_t$			
e : node voltage vector						
c.t. Pan e_t : tree branch voltage vector 111						

	S	Summary	
<u>Tabl</u>	le 2 Comparison of I Methods	Mesh and Fundamen Nodal Analysis	tal Loop Analyses Fundamental Cutset Analysis
	KCL	$I_{B} = M^{T} J_{m}$	$I_{B} = L^{T}J$
	KVL	$MV_{B} = 0$	$LV_{B} = 0$
	Component Model	$V_{\scriptscriptstyle B} = E_{\scriptscriptstyle S} + [R](I_{\scriptscriptstyle B} - I_{\scriptscriptstyle S})$	$V_{\scriptscriptstyle B} = V_{\scriptscriptstyle S} + [R](I_{\scriptscriptstyle B} - I_{\scriptscriptstyle S})$
	Equation to be Solved	$Ax = b$ $A = M[R]M^{T}$ $b = M[R]I_{s} - ME_{s}$ $x = J_{m}$	$Ax = b$ $A = L[R]L^{T}$ $b = L[R]I_{s} - LV_{s}$ $x = J$
C.T. Par	J _m : mesh cur J : link curre	rent vector ent vector	112







Summary
n Objective 1 : Understand and be able to use the
node-voltage method to solve a circuit.
nObjective 2 : Understand and be able to use the mesh-current method to solve a
circuit.
voltage method or the mesh –current
method is preferred approach to solving a particular circuit.
C.T. Pan /116



Summary								
n Problem : 4.9								
4.17								
4.24								
4.31								
4.39								
4.43								
n Due within one week.								
C.T. Pan	118							