

# CHAPTER 5




## TWO-PORT CIRCUITS

# CONTENTS

- 5.1 Definition of Two-Port Circuits
- 5.2 Classification of Two-Port Parameters
- 5.3 Finding Two-Port Parameters
- 5.4 Analysis of the Terminated Two-Port Circuit
- 5.5 Interconnected Two-Port Circuits
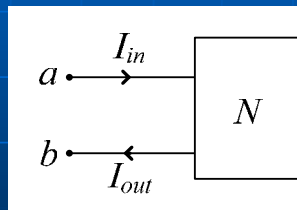
## 5.1 Definition of Two-Port Circuits


Consider a linear two-terminal circuit  $N$  consisting of no independent sources as follows :



For  $a, b$  two terminals, if  $I_{in} = I_{out}$ , then it constitutes a port.
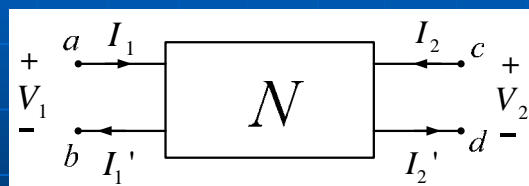
## 5.1 Definition of Two-Port Circuits


Now consider the following linear four-terminal circuit containing no independent sources.



with  $I_1 = I_1'$   
 $I_2 = I_2'$

Then terminals  $a, b$  constitute the input port and terminals  $c, d$  constitute the output port.

## 5.1 Definition of Two-Port Circuits

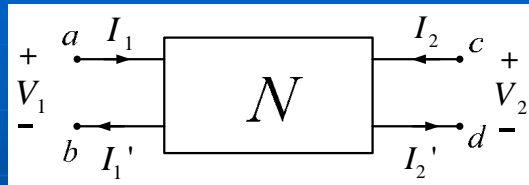

No external connections exist between the input and output ports.

The two-port model is used to describe the performance of a circuit in terms of the voltage and current at its input and output ports.

## 5.1 Definition of Two-Port Circuits

Two-port circuits are useful in communications, control systems, power systems, and electronic systems.

They are also useful for facilitating cascaded design of more complex systems.

## 5.2 Classification of Two-Port Parameters


There are four terminal variables , namely  $V_1, V_2, I_1, I_2$  , only two of them are independent.

Hence , there are only six possible sets of two-port parameters.

$${}^4C_2 = \frac{4 \times 3}{2 \times 1} = 6$$

## 5.2 Classification of Two-Port Parameters

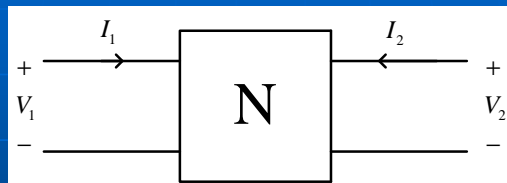(1) The impedance , or  $Z$  , parameters




$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}, \quad Z_{ij} : \text{in } \Omega$$

For two-port networks , four parameters are generally required to represent the circuit.

## 5.2 Classification of Two-Port Parameters


(2) The admittance , or Y , parameters

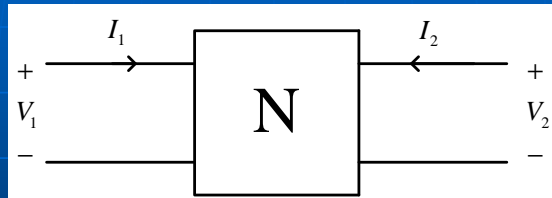

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}, \quad Y_{ij} : \text{in } S$$

## 5.2 Classification of Two-Port Parameters


(3) The hybrid , or h , parameters

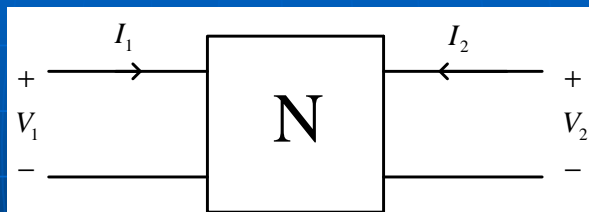

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}, \quad \begin{array}{l} h_{11} : \text{in } \Omega \\ h_{22} : \text{in } S \\ h_{12} \text{ \& } h_{22} \text{ scalars} \end{array}$$

## 5.2 Classification of Two-Port Parameters

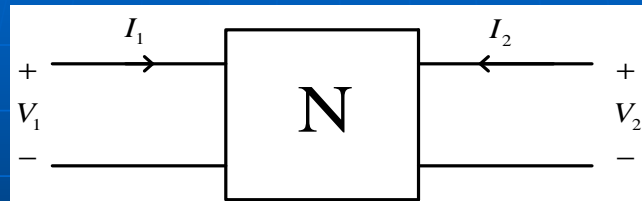
(4) The inverse hybrid , or  $g$  , parameters



$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}, \quad \begin{array}{l} g_{11} : \text{in } S \\ g_{22} : \text{in } \Omega \\ g_{12} \text{ \& } g_{21} \text{ scalars} \end{array}$$

## 5.2 Classification of Two-Port Parameters

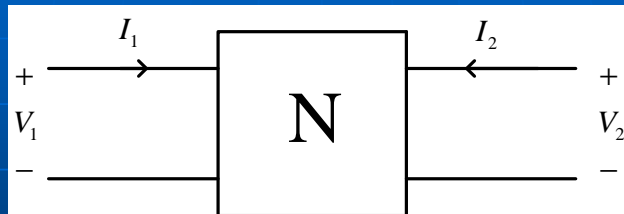
(5) The transmission , or  $a$  , parameters



$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}, \quad \begin{array}{l} a_{12} : \text{in } \Omega \\ a_{21} : \text{in } S \\ a_{11} \text{ \& } a_{22} \text{ scalars} \end{array}$$

## 5.2 Classification of Two-Port Parameters

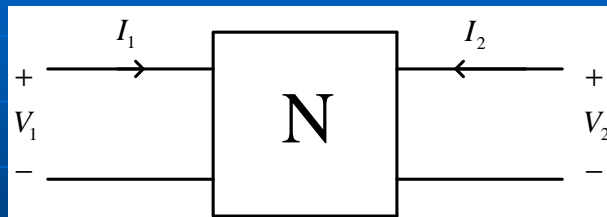(6) The inverse transmission, or  $b$ , parameters



$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} b_{11} & b_{12} \\ b_{21} & b_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ -I_1 \end{bmatrix}, \quad \begin{array}{l} b_{12} : \text{in } \Omega \\ b_{21} : \text{in } S \\ b_{11} \text{ \& } b_{22} \text{ scalars} \end{array}$$

## 5.3 Finding Two-Port Parameters


Method 1 : Calculate or measure by invoking appropriate short-circuit and open-circuit conditions at the input and output ports.

Method 2 : Derive the parameters from another set of two-port parameters.
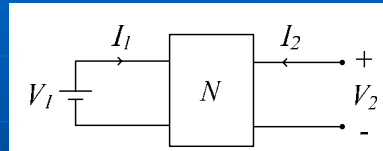
## 5.3 Finding Two-Port Parameters

Method 1 : Choose Z parameters as an illustration.

$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$




when  $I_2 = 0$  , output port is open

$$\begin{aligned} V_1 &= z_{11}I_1, \quad \left. z_{11} = \frac{V_1}{I_1} \right|_{I_2=0}, \text{ input impedance} \\ V_2 &= z_{21}I_1, \quad \left. z_{21} = \frac{V_2}{I_1} \right|_{I_2=0}, \text{ transfer impedance} \end{aligned}$$

## 5.3 Finding Two-Port Parameters

When  $I_1 = 0$  , input port is open

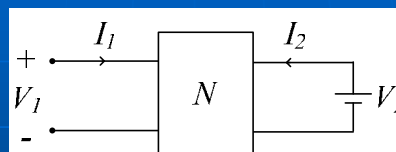

$$\begin{aligned} V_1 &= z_{12}I_2, \quad \left. z_{12} = \frac{V_1}{I_2} \right|_{I_1=0}, \text{ transfer impedance} \\ V_2 &= z_{22}I_2, \quad \left. z_{22} = \frac{V_2}{I_2} \right|_{I_1=0}, \text{ output impedance} \end{aligned}$$

When the two-port does not contain any dependent source, then  $z_{12}=z_{21}$ .



## 5.3 Finding Two-Port Parameters

$z_{11}$  &  $z_{22}$  are called driving-point impedances.


$z_{12}$  &  $z_{21}$  are called transfer impedances.

When  $z_{11}=z_{22}$ , the two-port circuit is said to be symmetrical.

When  $z_{12}=z_{21}$ , the two-port circuit is called a reciprocal circuit.

## 5.3 Finding Two-Port Parameters

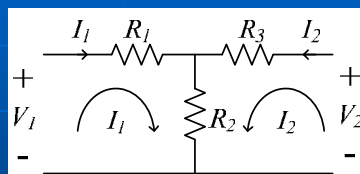Example 1 : Find the Z parameters of the T-network




Assign mesh currents as shown :

$$\begin{bmatrix} \hat{e} \\ \hat{e} \end{bmatrix} \begin{bmatrix} R_1 + R_2 & R_2 \\ R_2 & R_2 + R_3 \end{bmatrix} \begin{bmatrix} \hat{u} \\ \hat{u} \end{bmatrix} = \begin{bmatrix} \hat{e} \\ \hat{e} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\begin{cases} z_{11} = R_1 + R_2 \\ z_{12} = z_{21} = R_2 \\ z_{22} = R_2 + R_3 \end{cases}$$
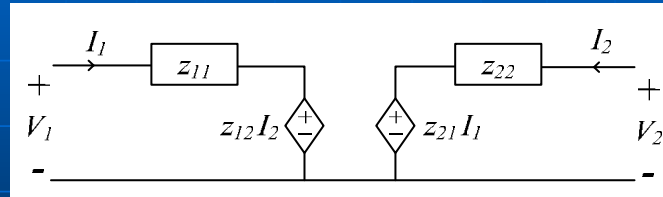
## 5.3 Finding Two-Port Parameters

A two-port can be replaced by the following equivalent circuit.




$$V_1 = z_{11}I_1 + z_{12}I_2$$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

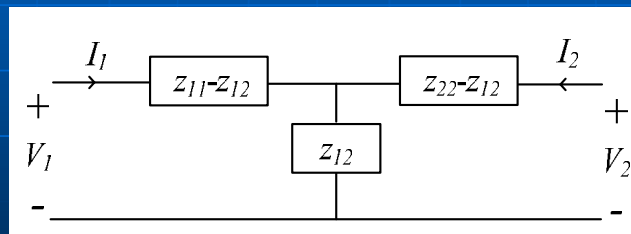
## 5.3 Finding Two-Port Parameters

In case the two-port is reciprocal,  $z_{12}=z_{21}$ , then it can also be represented by the T-equivalent circuit.




## 5.3 Finding Two-Port Parameters

Example 2 : Find the Z parameters

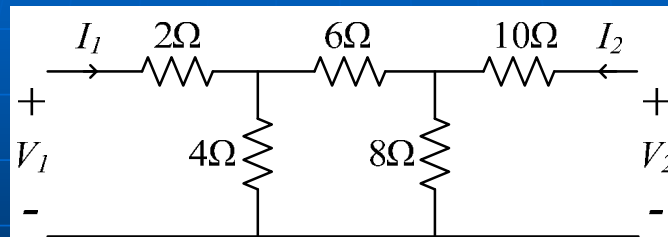

Assign mesh currents as follows and write down the mesh equation.

## 5.3 Finding Two-Port Parameters

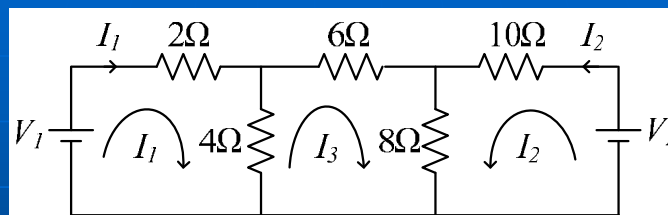

$$\begin{bmatrix} 2+4 & 0 & -4 \\ 0 & 10+8 & 8 \\ -4 & 8 & 4+6+8 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ 0 \end{bmatrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \\ 0 \end{bmatrix}$$

## 5.3 Finding Two-Port Parameters

$$A \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} + BI_3 = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} \quad \dots (1)$$

$$C \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} + DI_3 = 0 \quad \dots (2)$$

$$\text{From (2), } I_3 = -D^{-1}C \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \quad \dots (3)$$


Substitute (3) into (1)

$$A \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} - BD^{-1}C \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = [A - BD^{-1}C] \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

$$\therefore [Z] = A - BD^{-1}C$$


## 5.3 Finding Two-Port Parameters

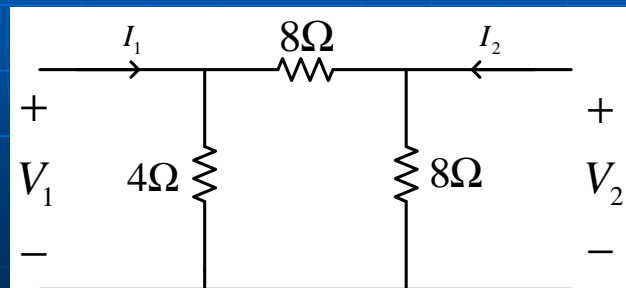Example 3: Find the Z parameters of the following circuit by definition of Z parameters.



## 5.3 Finding Two-Port Parameters

Step1: Let  $I_2 = 0$  and apply  $V_1$

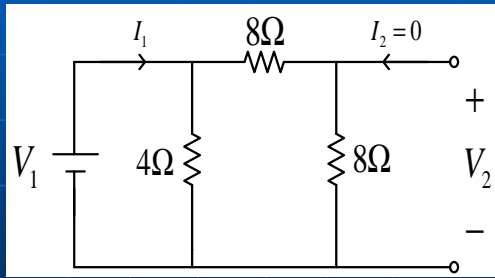

$$I_1 = V_1 / (4\Omega // (8+8)\Omega) = \frac{20}{64} V_1$$


$$V_2 = \frac{8}{8+8} V_1 = \frac{1}{2} V_1$$

$$\therefore z_{11} = \frac{V_1}{I_1} = \frac{64}{20} = \frac{16}{5} \Omega$$

$$z_{21} = \frac{V_2}{I_1} = \frac{\frac{1}{2} V_1}{I_1} = \frac{1}{2} z_{11} = \frac{8}{5} \Omega$$

## 5.3 Finding Two-Port Parameters

Step2: Let  $I_1 = 0$  and apply  $V_2$

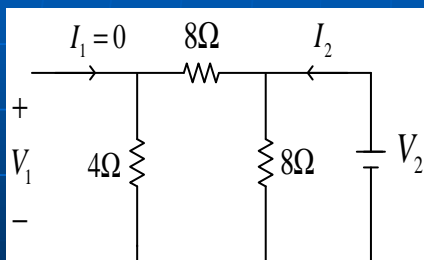

$$I_2 = V_2 / (8\Omega // (8+4)\Omega) = \frac{5}{24} V_2$$

$$V_1 = \frac{4}{4+8} V_2 = \frac{1}{3} V_2$$


$$\therefore z_{22} = \frac{V_2}{I_2} = \frac{24}{5} \Omega$$

$$z_{12} = \frac{V_1}{I_2} = \frac{\frac{1}{3} V_2}{I_2} = \frac{1}{3} z_{22} = \frac{8}{5} \Omega$$


$$\therefore [Z] = \begin{bmatrix} 16/5 & 8/5 \\ 8/5 & 24/5 \end{bmatrix} \Omega$$

## 5.3 Finding Two-Port Parameters

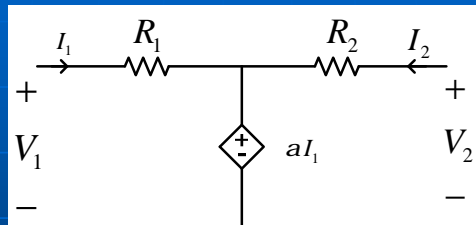Example 4: Containing dependent source case




Step1: Let  $I_2 = 0$  and apply  $V_1$

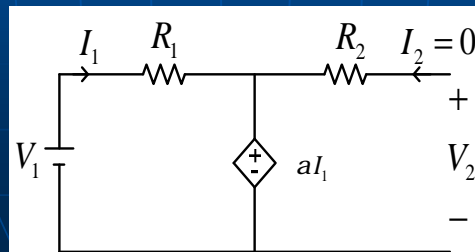

C.T. Pan

27

## 5.3 Finding Two-Port Parameters

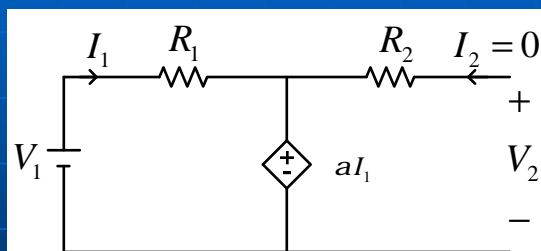

$$I_1 = \frac{V_1 - aI_1}{R_1}$$

$$\Rightarrow I_1 = \frac{V_1}{R_1 + a}$$

$$V_2 = aI_1$$

$$\therefore z_{11} = \frac{V_1}{I_1} = R_1 + a$$


$$z_{21} = \frac{V_2}{I_1} = a$$

C.T. Pan

28

## 5.3 Finding Two-Port Parameters

Step2: Let  $I_1 = 0$  and apply  $V_2$

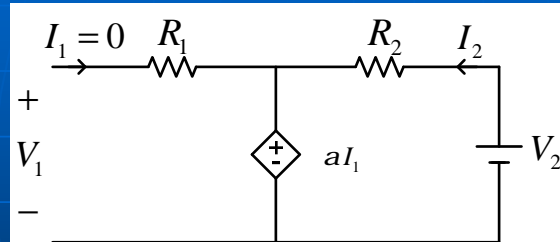


$$\begin{aligned} I_1 &= 0 \\ \therefore I_2 &= \frac{V_2}{R_2} \\ V_1 &= 0 \end{aligned}$$


$$\begin{aligned} \therefore z_{12} &= \frac{V_1}{I_2} = 0 \\ z_{22} &= \frac{V_2}{I_2} = R_2 \end{aligned} \quad , \quad \therefore [Z] = \begin{bmatrix} R_1 + a & 0 \\ a & R_2 \end{bmatrix}$$

## 5.3 Finding Two-Port Parameters

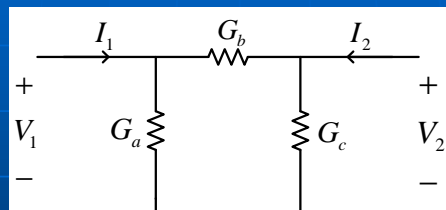
Example 5: Find the y parameters of the following circuit.



Use nodal analysis

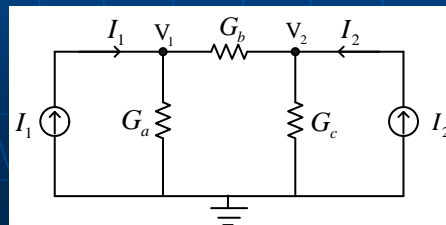

## 5.3 Finding Two-Port Parameters

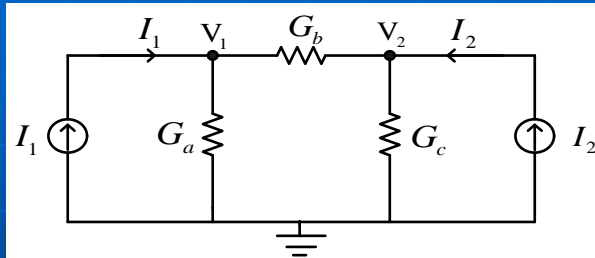

Nodal equation


$$\begin{bmatrix} G_a + G_b & -G_b \\ -G_b & G_b + G_c \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$\therefore [y] = \begin{bmatrix} G_a + G_b & -G_b \\ -G_b & G_b + G_c \end{bmatrix} \text{ in } S \text{ unit}$$

Note that  $y_{12} = y_{21} = -G_b$
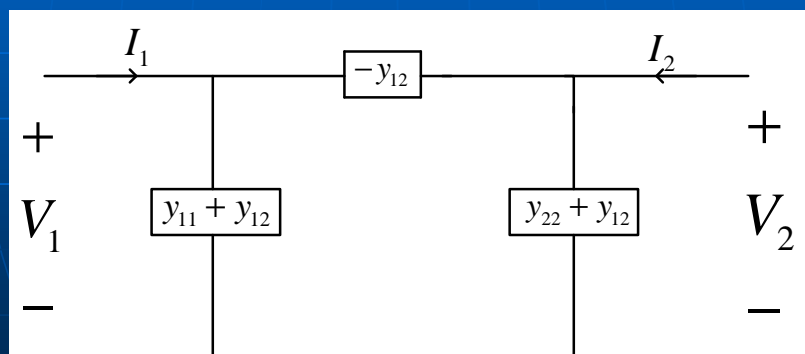
## 5.3 Finding Two-Port Parameters


A linear reciprocal two-port can be represented by the following equivalent  $\Pi$  circuit .




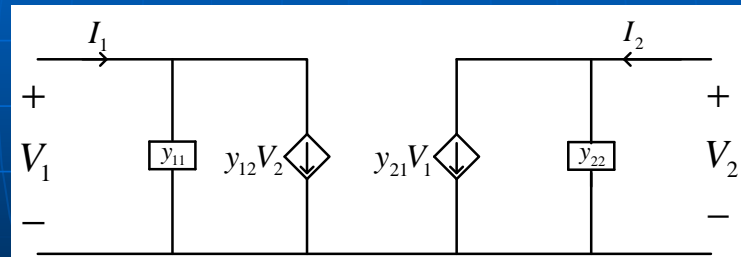
## 5.3 Finding Two-Port Parameters

Similarly, a linear two-port can also be represented by the following equivalent circuit with dependent sources.




$$I_1 = y_{11}V_1 + y_{12}V_2$$

$$I_2 = y_{21}V_1 + y_{22}V_2$$
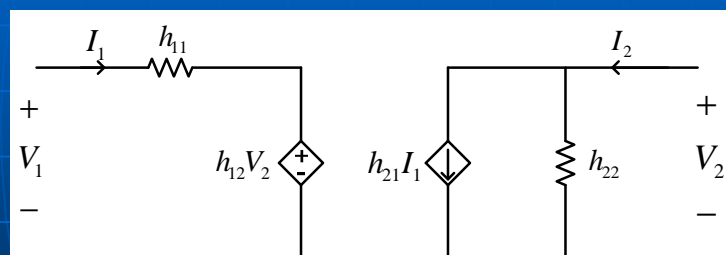
## 5.3 Finding Two-Port Parameters

A linear two-port can be represented by the following equivalent circuit.




$$V_1 = h_{11}I_1 + h_{12}V_2$$


$$I_2 = h_{21}I_1 + h_{22}V_2$$

## 5.3 Finding Two-Port Parameters

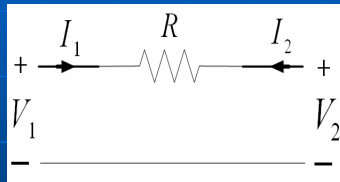Example 6 : Find the transmission parameters of the following circuits



(a)

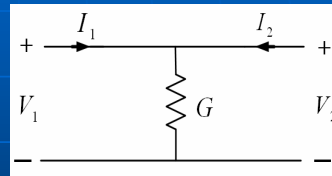


(b)

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

## 5.3 Finding Two-Port Parameters


For circuit (a) and when  $I_2=0$

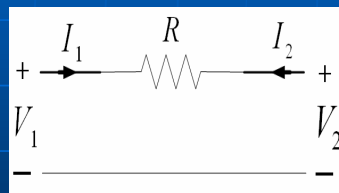

$$\begin{aligned} I_1 = -I_2 = 0 & \quad \therefore a_{21} = \frac{I_1}{V_2} = 0 \\ V_2 = V_1 & \quad \therefore a_{11} = \frac{V_1}{V_2} = 1 \end{aligned}$$

## 5.3 Finding Two-Port Parameters

For circuit (a) and when  $V_2=0$

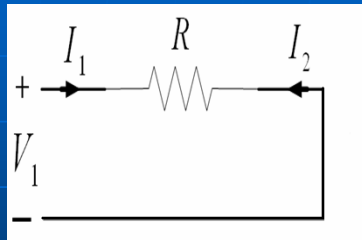


$$V_1 = RI_1 \quad \therefore a_{12} = \frac{V_1}{-I_2} = \frac{V_1}{I_1} = R$$

$$I_1 = -I_2 \quad \therefore a_{22} = \frac{I_1}{-I_2} = 1$$

$$\therefore \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} = \begin{bmatrix} 1 & R \\ 0 & 1 \end{bmatrix}$$

## 5.3 Finding Two-Port Parameters

Similarly, for circuit (b)

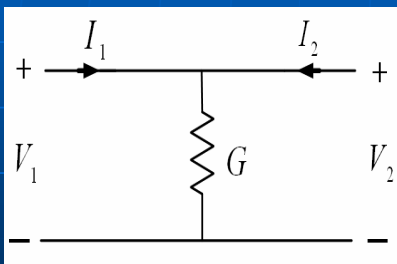

$$\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} = \begin{bmatrix} 1 & 0 \\ G & 1 \end{bmatrix}$$

## 5.3 Finding Two-Port Parameters

Method (2)

The 6 sets of parameters relate the same input and output terminal variables, hence they are interrelated.

A systematical procedure for obtaining a set of parameters from another one is given as follows for reference.

## 5.3 Finding Two-Port Parameters

Step1: Arrange the given two port parameters in the following standard form:

$$k_{11} V_1 + k_{12} I_1 + k_{13} V_2 + k_{14} I_2 = 0$$

$$k_{21} V_1 + k_{22} I_1 + k_{23} V_2 + k_{24} I_2 = 0$$

Step2: Separate the independent variables and the dependent variables of the desired parameter set.

Step3: Find the solution of the dependent variable vector.

## 5.3 Finding Two-Port Parameters

Example 7: Given Z parameters, find  $h$  parameters.

Step1 From  $V_1 = z_{11}I_1 + z_{12}I_2$

$$V_2 = z_{21}I_1 + z_{22}I_2$$

In the standard form

$$\underline{1V_1 - z_{11}I_1 + 0V_2 - z_{12}I_2 = 0}$$

$$\underline{0V_1 + z_{21}I_1 - 1V_2 + z_{22}I_2 = 0}$$

## 5.3 Finding Two-Port Parameters

Step2

$$\begin{bmatrix} 1 & -z_{12} \\ 0 & z_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} z_{11} & 0 \\ -z_{21} & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}$$

Step3

$$\begin{aligned} & \text{solve } \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} \\ \begin{bmatrix} V_1 \\ I_2 \end{bmatrix} &= \begin{bmatrix} 1 & -z_{12} \\ 0 & z_{22} \end{bmatrix}^{-1} \begin{bmatrix} z_{11} & 0 \\ -z_{21} & 1 \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} \\ &= \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix} \end{aligned}$$

## 5.3 Finding Two-Port Parameters

A different solution approach

$$V_1 = z_{11}I_1 + z_{12}I_2 \quad \dots\dots(A)$$

$$V_2 = z_{21}I_1 + z_{22}I_2 \quad \dots\dots(B)$$

From (B) one can obtain

$$I_2 = \frac{-z_{21}}{z_{22}}I_1 + \frac{1}{z_{22}}V_2 \quad \dots(C)$$
$$= h_{21}I_1 + h_{22}I_2$$

From (A) and (C)

$$V_1 = z_{11}I_1 + z_{12}(h_{21}I_1 + h_{22}I_2)$$
$$= (z_{11} + z_{12}h_{21})I_1 + z_{12}h_{22}I_2$$
$$\text{@ } h_{11}I_1 + h_{12}V_2$$

## 5.3 Finding Two-Port Parameters

Example 8 :

Two sets of measurements are made on a two-port resistive circuit. The first set is made with port 2 open, and the second set is made with port 2 short-circuited. The results are as follows :

*Port 2 open*

$$V_1 = 10\text{mV}$$

$$I_1 = 10\mu\text{A}$$

$$V_2 = -40\text{V}$$

*Port 2 short - circuited*

$$V_1 = 24\text{mV}$$

$$I_1 = 20\mu\text{A}$$

$$I_2 = 1\text{mA}$$

Find  $h$  parameters from there measurements.

## 5.3 Finding Two-Port Parameters

$$V_1 = h_{11} I_1 + h_{12} V_2 \quad \dots\dots\dots (A)$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \dots\dots\dots (B)$$

When port 2 is short circuited,  $V_2=0$

$$V_1=24\text{mV}, I_1=20 \mu\text{A}, I_2=1\text{mA}$$

Hence, from (A) and (B)

$$24\text{mV} = h_{11}(20 \mu\text{A}) + 0$$

$$1\text{mA} = h_{21}(20 \mu\text{A}) + 0$$

$$\therefore h_{11} = 1.2 \text{K}\Omega, h_{21} = 50 \quad \dots\dots\dots (C)$$

## 5.3 Finding Two-Port Parameters

When port 2 is open,  $I_2=0$

$$V_1=10\text{mV}, I_1=10 \mu\text{A}, V_2=-40\text{V}$$

Hence, from (A), (B) and (C)

$$10\text{mV} = 1.2 \text{K}\Omega (10 \mu\text{A}) + h_{12} (-40\text{V})$$

$$0 = 50 (10 \mu\text{A}) + h_{22} (-40\text{V})$$


$$\therefore h_{12} = 5 \times 10^{-5}, h_{22} = 12.5 \mu\text{S}$$

## 5.4 Analysis of the Terminated Two-Port Circuit

### Reciprocal Theorem

Version 1 : For a reciprocal circuit, the interchange of an ideal voltage source at one port with an ideal ammeter at the other port produces the same ammeter reading.
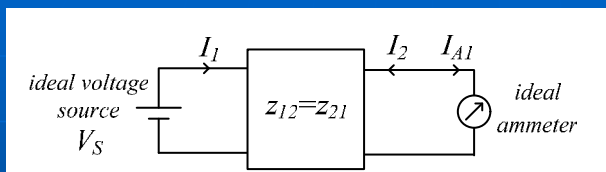
## 5.4 Analysis of the Terminated Two-Port Circuit



$$\begin{aligned} V_1 &= z_{11}I_1 + z_{12}I_2 \\ V_2 &= z_{21}I_1 + z_{22}I_2 \end{aligned}$$

$$\text{Q } V_1 = V_S, I_2 = -I_{AI}, V_2 = 0$$


$$V_S = z_{11}I_1 + z_{12}(-I_{AI})$$

$$0 = z_{12}I_1 + z_{22}(-I_{AI})$$

$$\backslash I_{AI} = \frac{z_{12}V_S}{z_{11}z_{22} - z_{12}^2}$$


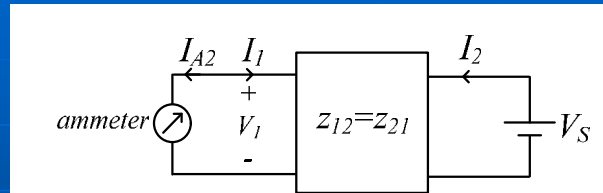
## 5.4 Analysis of the Terminated Two-Port Circuit



$$\begin{aligned} \text{Q } V_1 &= 0, I_{A2} = -I_1, V_2 = V_S \\ \setminus \quad 0 &= z_{11}(-I_{A2}) + z_{12}I_2 \\ V_S &= z_{12}(-I_{A2}) + z_{22}I_2 \\ \setminus \quad I_{A2} &= \frac{z_{12}V_S}{z_{11}z_{22} - z_{12}^2} = I_{A1} \end{aligned}$$



## 5.4 Analysis of the Terminated Two-Port Circuit

The effect of reciprocity on the two-port parameters is given by



$$\begin{aligned} z_{12} &= z_{21}, \text{ or } y_{12} = y_{21} \\ a_{11}a_{22} - a_{12}a_{21} &= 1, \text{ or } \\ b_{11}b_{22} - b_{12}b_{21} &= 1, \text{ or } \\ h_{12} &= -h_{21}, \text{ or } g_{12} = -g_{21} \end{aligned}$$

## 5.4 Analysis of the Terminated Two-Port Circuit

Examples of symmetric two ports.

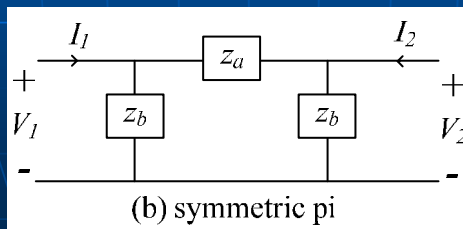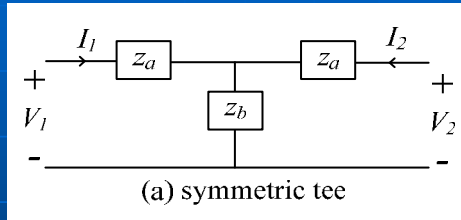

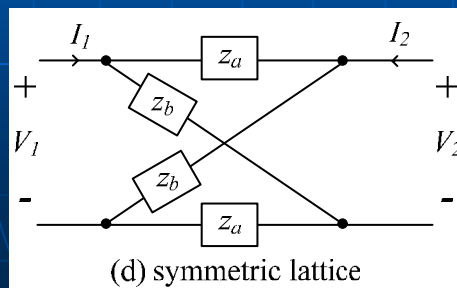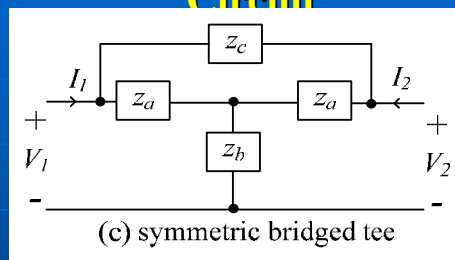
## 5.4 Analysis of the Terminated Two-Port Circuit


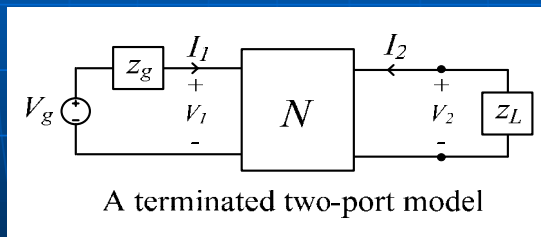
## 5.4 Analysis of the Terminated Two-Port Circuit

There are mainly 6 interested characteristics for a terminated two-port circuit in practical applications.



## 5.4 Analysis of the Terminated Two-Port Circuit

input impedance  $Z_{in} @ V_1 / I_1$


output current  $I_2$

Thevenin equivalent looking into port 2.

current gain  $I_2 / I_1$

voltage gain  $V_2 / V_1$

voltage gain  $V_2 / V_g$

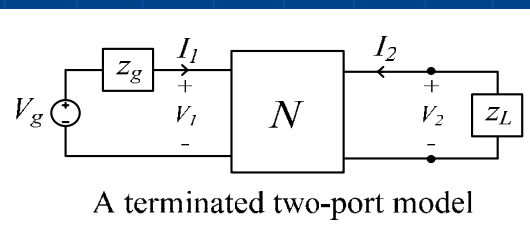


## 5.4 Analysis of the Terminated Two-Port Circuit

The derivation of any one of the desired expressions involves the algebraic manipulation of the two-port equations along with the two constraint equations imposed at input and output terminals.

## 5.4 Analysis of the Terminated Two-Port Circuit

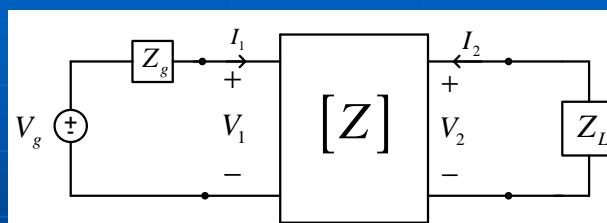Example 9 : Use Z parameters as an illustration



two-port equation


$$V_1 = z_{11}I_1 + z_{12}I_2 \quad \mathbf{L L} \quad (A)$$

$$V_2 = z_{21}I_1 + z_{22}I_2 \quad \mathbf{L L} \quad (B)$$
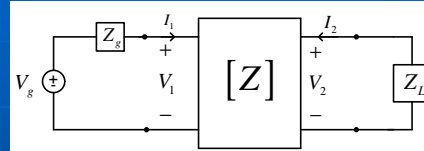
## 5.4 Analysis of the Terminated Two-Port Circuit

input port constraint

$$V_g = I_1 z_g + V_1 \quad \mathbf{LL} \quad (C)$$



Output port constraint

$$V_2 = -z_L I_2 \quad \mathbf{LL} \quad (D)$$

(1) Find  $Z_{in} = V_1 / I_1$


From (D) and (B) ,

$$I_2 = \frac{-z_{21} I_1}{z_{22} + z_L} \quad \mathbf{LL} \quad (E)$$
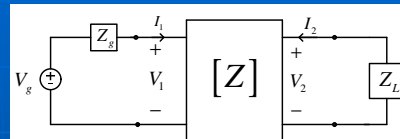
## 5.4 Analysis of the Terminated Two-Port Circuit

Substitute (E) into (A)

$$Z_{in} = z_{11} - \frac{z_{12} z_{21}}{z_{22} + z_L}$$



(2) Find  $I_2$  : From (A) and (C)

$$I_1 = \frac{V_g - z_{12} I_2}{z_{11} + z_g} \quad \mathbf{LL} \quad (F)$$

Substitute (F) into (E)

$$I_2 = \frac{-z_{21} V_g}{(z_{11} + z_g)(z_{22} + z_L) - z_{12} z_{21}} \quad \mathbf{LL} \quad (G)$$

## 5.4 Analysis of the Terminated Two-Port Circuit

(3) Find  $V_{TH}$  and  $Z_{TH}$  at port 2 :

With  $I_2=0$  , from (A) , (B) and (F)

$$\begin{aligned} V_1 &= z_{11}I_1 \\ V_2 &= z_{21}I_1 \Rightarrow V_2 = \frac{z_{21}}{z_{11}}V_1 \quad \mathbf{LL} \quad (H) \\ I_1 &= \frac{V_g}{z_{11} + z_g} \quad \mathbf{LLLLLLLL} \quad (I) \end{aligned}$$

From (C) , (H) and (I)

$$\therefore V_{TH} = V_2 = \frac{z_{21}}{z_g + z_{11}}V_g$$

## 5.4 Analysis of the Terminated Two-Port Circuit

With  $V_g=0$  , then  $V_1 = -z_g I_1 \quad \mathbf{LL} \quad (J)$

From (A) and (J) ,  $I_1 = \frac{-z_{12}I_2}{z_{11} + z_g}$

$$\therefore Z_{TH} = \frac{V_2}{I_2} = z_{22} - \frac{z_{12}z_{21}}{z_{11} + z_g}$$

(4) Find current gain  $I_2/I_1$

From (E) ,  $\frac{I_2}{I_1} = -\frac{z_{21}}{z_L + z_{22}}$

## 5.4 Analysis of the Terminated Two-Port Circuit

(5) Find voltage gain  $V_2/V_1$  :

From (B) and (D)

$$V_2 = z_{21}I_1 + z_{22}\left(-\frac{V_2}{z_L}\right)$$

$$\therefore V_2 = \frac{z_{21}z_L}{z_L + z_{22}}I_1 \text{ LLLLLLLL (K)}$$

From (A) , (D) , and (K)

$$V_1 = \frac{(z_{11}z_L + z_{11}z_{22} - z_{12}^2)}{z_L + z_{22}}I_1$$

$$\therefore \frac{V_2}{V_1} = \frac{z_{21}z_L}{z_{11}z_L + z_{11}z_{22} - z_{12}^2} \text{ LLLLLL (L)}$$

## 5.4 Analysis of the Terminated Two-Port Circuit


(6) Find  $V_2/V_g$  :

$$\text{Q } \frac{V_2}{V_g} = \frac{V_2}{V_1} \frac{V_1}{V_g} = \frac{V_2}{V_1} \frac{Z_{in}}{(z_g + Z_{in})}$$

$$= \frac{z_{21}z_L}{(z_{11} + z_g)(z_{22} + z_L) - z_{12}z_{21}}$$

## 5.4 Analysis of the Terminated Two-Port Circuit

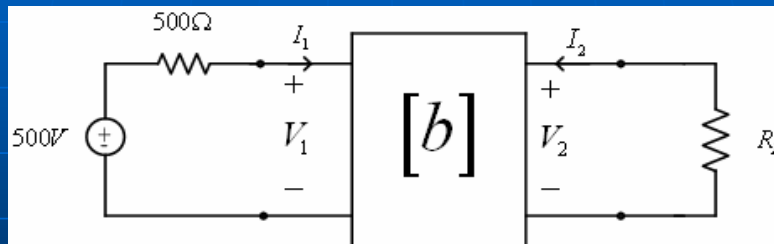Example 10 : Given the following circuit, find  $V_2$  when  $R_L = 5K\Omega$



$$\begin{aligned} b_{11} &= -20 & b_{12} &= -3000\Omega \\ b_{21} &= -2ms & b_{22} &= -0.2 \end{aligned}$$

## 5.4 Analysis of the Terminated Two-Port Circuit


Example 10: (cont.)

$$V_2 = b_{11}V_1 - b_{12}I_1 \dots\dots\dots(A)$$

$$I_2 = b_{21}V_1 - b_{22}I_1 \dots\dots\dots(B)$$

$$V_1 = 500 - 500I_1 \dots\dots\dots(C)$$
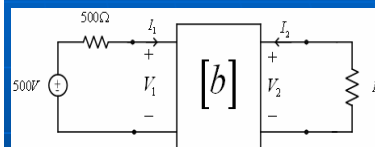
$$I_2 = -\frac{V_2}{R_L} \dots\dots\dots(D)$$



Substitute (C) and (D) into (A) and (B) to eliminate  $V_1$  and  $I_2$

$$V_2 - 13 \times 10^3 I_1 = -10^4 \dots\dots(E)$$

$$V_2 + 6 \times 10^3 I_1 = 5 \times 10^3 \dots\dots(F)$$

From (E) and (F), 
$$V_2 = \frac{5000}{19} = 263.16V$$




## 5.5 Interconnected Two-Port Circuits

Two-port circuits may be interconnected in five ways :

- (1) in series
- (2) in parallel
- (3) in series-parallel
- (4) in parallel-series
- (5) in cascade

## 5.5 Interconnected Two-Port Circuits

(1) Series connection

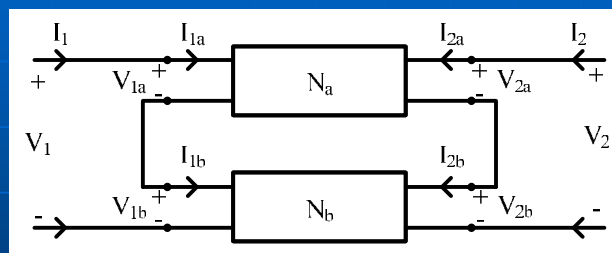


$$I_1 = I_{1a} = I_{1b} \quad V_1 = V_{1a} + V_{1b}$$

$$I_2 = I_{2a} = I_{2b} \quad V_2 = V_{2a} + V_{2b}$$

$$\therefore [Z] = [Z_a] + [Z_b]$$

## 5.5 Interconnected Two-Port Circuits

### (2) Parallel connection

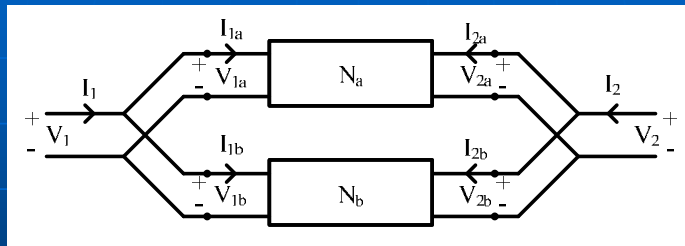


$$\begin{aligned} I_1 &= I_{1a} + I_{1b} & V_1 &= V_{1a} = V_{1b} \\ I_2 &= I_{2a} + I_{2b} & V_2 &= V_{2a} = V_{2b} \end{aligned}$$

$$\therefore [Y] = [Y_a] + [Y_b]$$

## 5.5 Interconnected Two-Port Circuits

### (3) Series-parallel connection

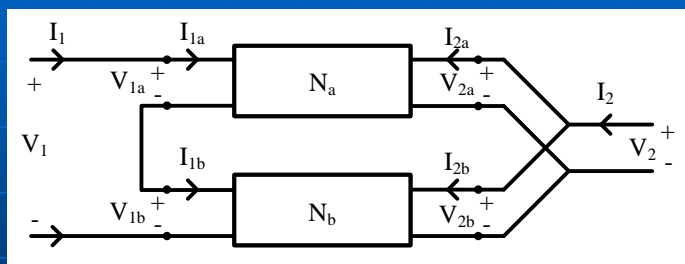


$$\begin{aligned} I_1 &= I_{1a} = I_{1b} & V_1 &= V_{1a} + V_{1b} \\ I_2 &= I_{2a} + I_{2b} & V_2 &= V_{2a} = V_{2b} \end{aligned}$$

$$\therefore [h] = [h_a] + [h_b]$$

## 5.5 Interconnected Two-Port Circuits

### (4) Parallel-series connection

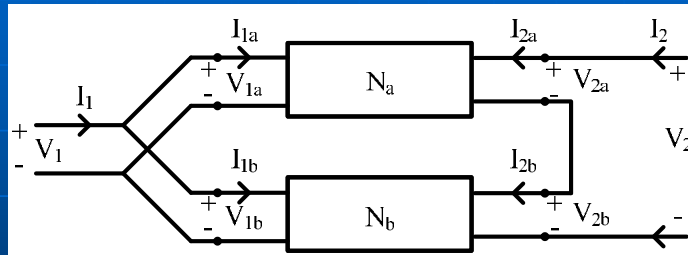

$$I_1 = I_{1a} + I_{1b}$$

$$V_1 = V_{1a} = V_{1b}$$


$$I_2 = I_{2a} = I_{2b}$$

$$V_2 = V_{2a} + V_{2b}$$

$$\therefore [g] = [g_a] + [g_b]$$

## 5.5 Interconnected Two-Port Circuits

### (5) Cascade connection

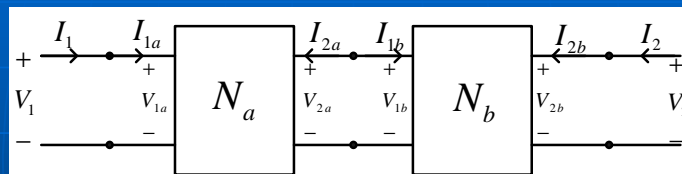

$$V_1 = V_{1a}$$

$$I_1 = I_{1a}$$

$$V_{2a} = V_{1b}$$

$$I_{1b} = -I_{2a}$$


$$V_2 = V_{2b}$$

$$I_2 = I_{2b}$$

$$\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} = \begin{bmatrix} a_{11}' & a_{12}' \\ a_{21}' & a_{22}' \end{bmatrix} + \begin{bmatrix} a_{11}'' & a_{12}'' \\ a_{21}'' & a_{22}'' \end{bmatrix}$$

## 5.5 Interconnected Two-Port Circuits

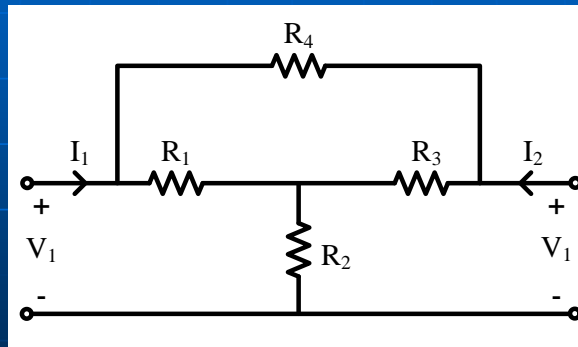
Example 11 : Find the  $[Z]$  and  $[Y]$  parameters of the following two port network.



## 5.5 Interconnected Two-Port Circuits

Example 11 : (cont.)

For  $[y]$  parameters :

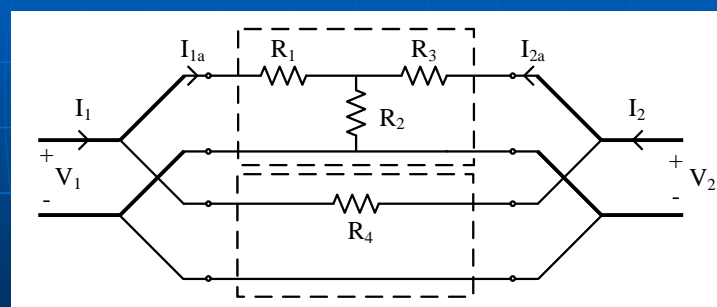


## 5.5 Interconnected Two-Port Circuits

Example 11 : (cont.)

$$\begin{bmatrix} I_{1a} \\ I_{2a} \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_{1a} \\ V_{2a} \end{bmatrix}$$


$$\begin{cases} \frac{1}{y_{11}} = R_1 + (R_2 \parallel R_3) = R_1 + \frac{R_2 R_3}{R_2 + R_3} \\ \frac{1}{y_{22}} = R_3 + (R_1 \parallel R_2) = R_3 + \frac{R_1 R_2}{R_1 + R_2} \end{cases}$$
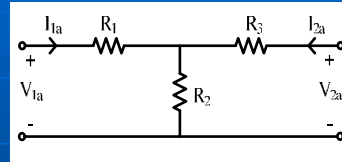
$$y_{12} = y_{21} = \frac{I_{1a}}{V_2} = -V_2 y_{22} \times \frac{R_2}{R_1 + R_2} \times \frac{1}{V_2} = -y_{22} \times \frac{R_2}{R_1 + R_2}$$



## 5.5 Interconnected Two-Port Circuits

Example 11 : (cont.)

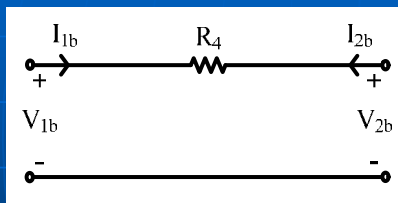

$$\begin{bmatrix} I_{1b} \\ I_{2b} \end{bmatrix} = \begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} \begin{bmatrix} V_{1b} \\ V_{2b} \end{bmatrix}$$


$$\begin{cases} y_{11} = \frac{1}{R_4} = y_{22} \\ y_{12} = y_{21} = \frac{I_1}{V_2} = -\frac{1}{R_4} \end{cases}$$

$$\therefore [y] = [y_a] + [y_b]$$

## 5.5 Interconnected Two-Port Circuits

Example 11 : (cont.)

For [z] parameters :

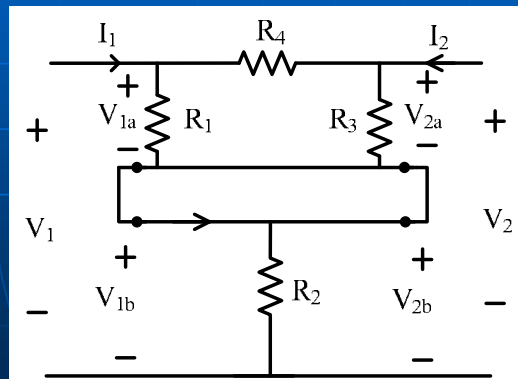


C.T. Pan

75

## 5.5 Interconnected Two-Port Circuits


Example 11 : (cont.)

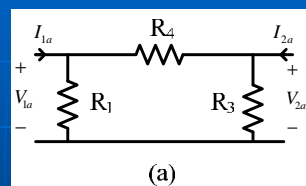

$$Z_{11} = R_1 \parallel (R_3 + R_4)$$

$$Z_{22} = R_3 \parallel (R_1 + R_4)$$
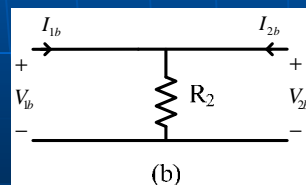
$$Z_{12} = Z_{21} = Z_{22} \times \frac{R_1}{R_1 + R_4}$$



$$Z_{11} = Z_{22} = R_2$$

$$Z_{12} = Z_{21} = R_2$$


$$\therefore [Z] = [Z_a] + [Z_b]$$

C.T. Pan

76

## 5.5 Interconnected Two-Port Circuits

Example 12 : Find the a parameters.

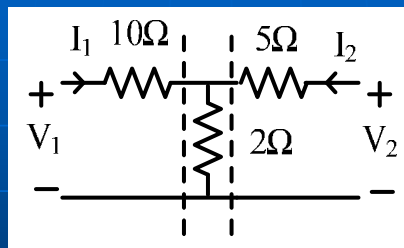


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & 10 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ \frac{1}{2} & 1 \end{bmatrix} \begin{bmatrix} 1 & 5 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

$$= \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

## 5.5 Interconnected Two-Port Circuits

Example 13 : A common emitter circuit

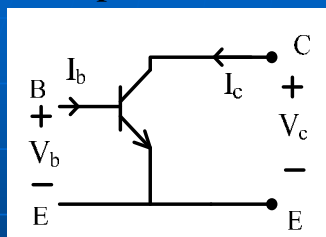


$$\begin{bmatrix} V_b \\ I_c \end{bmatrix} = \begin{bmatrix} h_{ie} & h_{re} \\ h_{fe} & h_{oe} \end{bmatrix} \begin{bmatrix} I_b \\ V_c \end{bmatrix}$$

$h_{ie}$ : base input impedance

$h_{re}$ : reverse voltage gain

$h_{fe}$ : forward current gain

$h_{oe}$ : output admittance

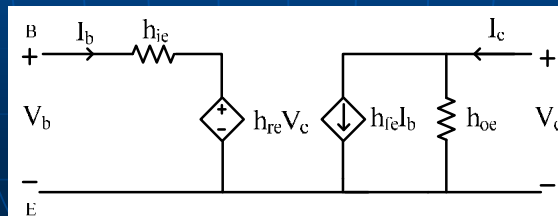

## Summary

- n Objective 1 : Understand the definition of 6 sets of two port parameters.
- n Objective 2 : Be able to find any set of two-port parameters.
- n Objective 3 : Be able to analyze a terminated two-port circuit.

## Summary

- n Objective 4 : Understand the reciprocal theorem for two-port circuits.
- n Objective 5 : Know how to analyze an interconnected two-port circuits.



## Summary

n Problem : 18.4

18.8

18.11

18.18

18.37

18.38

n Due within one week.