

Lecture 05

Per unit (PU value)

P.U. (Per Unit value)

$$P.U. = \frac{\text{real value}}{\text{base value}}$$

Example: A given impedance is 0.050 per-unit on bases of $V_b=138\text{kV}$ and $S_3 \varphi b=200\text{MVA}$. Calculate Z in per-unit if base values for V_b and $S_3 \varphi b$ are, respectively,

- a) 138 kV, 100 MVA
- b) 132 kV, 200 MVA
- c) 132 kV, 100 MVA

Ans:

$$Z_{pu} = \frac{Z_r}{Z_b} \Rightarrow 0.050 = \frac{Z_r}{\frac{(138KV)^2}{200MVA}} \Rightarrow Z_r = 4.761(\Omega)$$

$$(a). Z_{pu} = \frac{Z_r}{Z_b} = \frac{4.761}{\frac{(138KV)^2}{100MVA}} = 0.025(pu)$$

$$(b). Z_{pu} = \frac{Z_r}{Z_b} = \frac{4.761}{\frac{(132KV)^2}{200MVA}} = 0.05465(pu)$$

$$(c). Z_{pu} = \frac{Z_r}{Z_b} = \frac{4.761}{\frac{(132KV)^2}{100MVA}} = 0.02732(pu)$$

How to chose the base value?(S?, V?, I?, or Z?)

1. For a single phase system:

a. Chose S_b & V_b (phase voltage)

b. Calculate

$$I_b = \frac{S_b}{V_b}, Z_b = \frac{V_b}{I_b} = \frac{V_b^2}{S_b}$$

2. For a three phases system:

a. Chose S_b & V_b (line voltage)

b. Calculate

$$I_b = \frac{S_b}{\sqrt{3}V_b}, Z_b = \frac{\sqrt{3}V_b}{I_b} = \frac{V_b^2}{S_b}$$

in which S_b can be transformer capacity or 100MVA, 1000KVA
(easy to calculate)

Example: — 3φ 12KV, 30MVA 發電機, 實際發電量 18MVA, 10.8KV, 求三相之容量與電壓標么值.

三相模式

$$S_b = 30 \text{MVA}$$

$$V_b = 12 \text{KV}$$

$$S_{pu} = \frac{18}{30} = 0.6(pu)$$

$$V_{pu} = \frac{10.8}{12} = 0.9(pu)$$

單相模式

$$S_b = \frac{30}{\sqrt{3}} \text{MVA}$$


$$V_b = \frac{12}{\sqrt{3}} \text{KV}$$

$$S_{pu} = \frac{\frac{18}{\sqrt{3}}}{\frac{30}{\sqrt{3}}} = 0.6(pu)$$

$$V_{pu} = \frac{\frac{10.8}{\sqrt{3}}}{\frac{12}{\sqrt{3}}} = 0.9(pu)$$

不論採用單相或三相模式標么值均相同

example

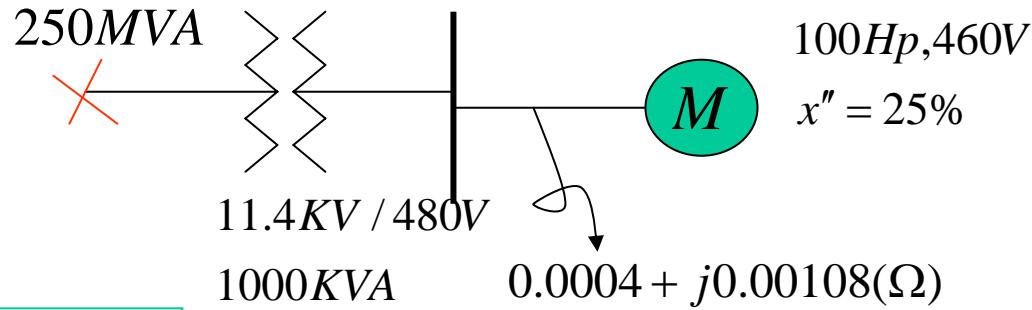

$$X_{tr}(pu) \quad x = 10\%$$

Step 1: find base value

$$S_b = 1000 \text{ KVA}$$

$$V_b = 480V$$

$$Z_b = \frac{V_b^2}{S_b} = \frac{480^2}{1000} = 0.2304$$

Step 2: find $Z_l(pu)$

$$R_{l(pu)} = \frac{0.0004}{Z_b} = 0.001736$$

$$X_{l(pu)} = \frac{0.00108}{Z_b} = 0.0046875$$

Step 2: find $X_M(pu)$

$$X_{M(pu)} = 0.25 \left(\frac{460}{480} \right)^2 \frac{1MVA}{0.1MVA} = 2.2952$$



Step 1: find base value

$$S_b = 10\text{MVA}, V_{Ab} = 13.8\text{KV}, V_{Bb} = 138\text{KV}, V_{Cb} = 69\text{KV}$$

$$Z_b = \frac{V_b^2}{S_b} \Rightarrow Z_{Ab} = \frac{(138K)^2}{10M} = 1900\Omega, Z_{Ab} = \frac{(13.8K)^2}{10M} = 19\Omega, Z_{Ab} = \frac{(69K)^2}{10M} = 476\Omega$$

Step 2: find Real Z

$$Z_C = 300\Omega, Z_B = 300\Omega \times 2^2 = 1200\Omega, Z_A = 1200\Omega \times 0.1^2 = 12\Omega$$

Step 3: find Z pu


$$Z_{A(pu)} = \frac{12}{19} = 0.63$$

$$Z_{B(pu)} = \frac{1200}{1900} = 0.63$$

$$Z_{C(pu)} = \frac{300}{476} = 0.63$$


阻抗換算至各個子系統均不相同
但其標么值卻相同

上例之標么阻抗圖如下：

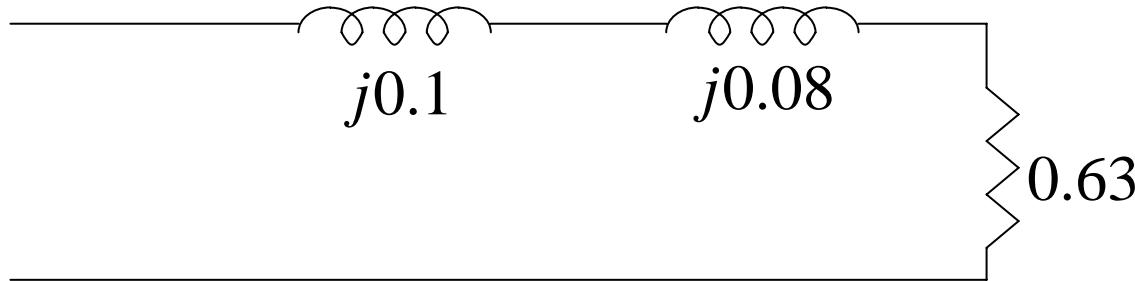

不需要考慮變壓器電壓比變換問題

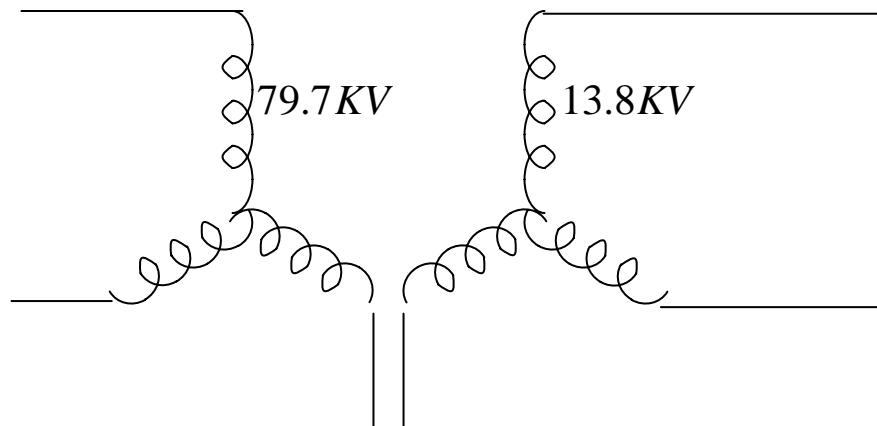Example: 三台 1φ 20/3MVA 79.7KV/13.8KV變壓器, 電抗0.2pu, 試求變壓器(a) 單相單獨使用 (b) Y-Y接線 (c) Δ-Y 接線 ;一次側及二次側等效之電抗實際值及標么值.



(a) 單相單獨使用

$$S_b = \frac{2}{3} MVA, V_{1b} = 79.7 KV, V_{2b} = 13.8 KV$$

$$\Rightarrow Z_{1b} = \frac{(V_{1b})^2}{S_b} = \frac{(79.7 K)^2}{\frac{2}{3} M} = 952.8 \Omega$$

$$\Rightarrow Z_{2b} = \frac{(V_{2b})^2}{S_b} = \frac{(13.8 K)^2}{\frac{2}{3} M} = 28.57 \Omega$$

一次側及二次側等效電抗: $Z_{1eq} = 0.2 \times 952.8 = 190.4 \Omega / phase$

$$Z_{2eq} = 0.2 \times 28.57 = 5.72 \Omega / phase$$

一次側及二次側等效電抗標么值均為: 0.2pu

(b) Y-Y 接線

$$S_b = 20 MVA, V_{1b} = 79.7 \sqrt{3} KV = 138 KV, V_{2b} = 13.8 \sqrt{3} = 23.9 KV$$

$$\Rightarrow Z_{1b} = \frac{(V_{1b})^2}{S_b} = \frac{(138 K)^2}{20 M} = 952.8 \Omega$$

$$\Rightarrow Z_{2b} = \frac{(V_{2b})^2}{S_b} = \frac{(23.9 K)^2}{20 M} = 28.57 \Omega$$

一次側及二次側等效電抗: $Z_{1eq} = 0.2 \times 952.8 = 190.4\Omega / phase$

$$Z_{2eq} = 0.2 \times 28.57 = 5.72\Omega / phase$$

一次側及二次側等效電抗標么值:

$$Z_{1pu} = 190.4 / 952.8 = 0.2$$

$$Z_{2pu} = 5.72 / 28.57 = 0.2$$

(b) Δ -Y 接線 $S_b = 20MVA, V_{1b} = 79.7KV, V_{2b} = 13.8\sqrt{3} = 23.9KV$

$$\Rightarrow Z_{1b} = \frac{(V_{1b})^2}{S_b} = \frac{(79.7K)^2}{20M} = 317.6\Omega$$

$$\Rightarrow Z_{2b} = \frac{(V_{2b})^2}{S_b} = \frac{(23.9K)^2}{20M} = 28.57\Omega$$

無論變壓器的接線情況標么值均相同

一次側及二次側等效電抗: $Z_{1Yeq} = 190.4 / 3 \Omega = 63.47\Omega (\Delta \rightarrow Y)$

$$Z_{2eq} = 0.2 \times 28.57 = 5.72\Omega / phase$$

一次側及二次側等效電抗標么值:

$$Z_{1pu} = 63.47 / 317.6 = 0.2$$

$$Z_{2pu} = 5.72 / 28.57 = 0.2$$

Example: A single-phase system similar to that shown in Fig. 2.10 has two transformers A-B and B-C connected by a line B feeding a load at the receiving end C. The ratings and parameter values of the components are:

Transformer A-B: 500V/1.5kV, 9.6kVA, leakage reactance = 5%

Transformer B-C: 1.2kV/120V, 7.2kVA, leakage reactance = 4%

Line B: series impedance = $(1.5+j3.0)$

Load C: 120V, 6kVA at 0.8 power-factor lagging

- Determine the value of the load impedance in ohms and the actual ohmic impedances of the two transformers referred to both their primary and secondary
- Choosing 1.2 kV as the voltage base for circuit B and 10 kVA as the systemwide kVA base, express all system impedances in per unit.



電力系統之短路容量(KVAs)

$$VAs = I_{Sy} \times V_b = \frac{V_b}{Z_s} \times V_b = \frac{V_b^2}{Z_s}$$

$$Z_s = \frac{(V_b)^2}{VA_s} \quad Z_b = \frac{(V_b)^2}{VA_b}$$

$$Z_{spu} = \frac{Z_s}{Z_b} = \frac{KVA_b}{KVA_s}$$

台電:

11.4KV供電	250MVA
22.8KV供電	500MVA
69KV供電	1500MVA