

Unit 8

Combinational Circuit Design and Simulation Using Gates



Outline

- Review of combinational circuit design
- Design of circuits with limited gate fan-in
- Gate delay and timing diagrams
- Hazards in combinational logic
- Simulation and testing of logic circuits



Review of Combinational Circuit Design


- Design of a combinational switching circuit
 - Setup a truth table which specifies the output(s) as a function of the input variables
 - Derive simplified algebraic expressions for the output functions using K-Maps, the Q-M method, or other similar procedures.
- Multi-level & Multi-output circuit
- Minimum SOP's starting point
 - Minimum two-level AND-OR 、 NAND-NAND 、 OR-NAND 、 NOR-OR
- Minimum POS's starting point
 - Minimum two-level OR-AND 、 NOR-NOR 、 AND-NOR 、 NAND-AND

Circuit with Limited Gate Fan-In (1/3)

- Ex 1

Realize $f(a, b, c, d) = \sum m(0, 3, 4, 5, 8, 9, 10, 14, 15)$ using 3-input NOR gates

cd \ ab	ab			
	00	01	11	10
00	1	1	0	1
01	0	1	0	1
11	1	0	1	0
10	0	0	1	1

 

$$\begin{aligned}
 f' &= a'b'c'd + ab'cd + abc' + a'bc + a'cd' \\
 &= b'd(a'c' + ac) + a'c(b + d') + abc'
 \end{aligned}$$

Circuit with Limited Gate Fan-In (2/3)



- Ex 2
Only using 2-input NAND gates and inverters

bc \ a	0	1
00	1	1
01		1
11	1	
10	1	

$$f_1 = \sum m(0, 2, 3, 4, 5)$$

bc \ a	0	1
00	1	1
01		
11	1	1
10	1	

$$f_2 = \sum m(0, 2, 3, 4, 7)$$

bc \ a	0	1
00		
01	1	
11		1
10	1	1

$$f_3 = \sum m(1, 2, 6, 7)$$

$$f_1 = b'c' + ab' + a'b$$

$$f_2 = b'c' + bc + a'b$$

$$f_3 = a'b'c + ab + bc'$$


Circuit with Limited Gate Fan-In (3/3)




$$f_1 = b'(a + c') + a'b$$

$$f_2 = b(a' + c) + b'c' \quad \text{or} \quad f_2 = (b' + c)(b + c') + a'b$$

$$f_3 = a'b'c + b(a + c')$$

 


(a)





 


(b)

Gate Delay and Timing Diagrams (1/2)

 

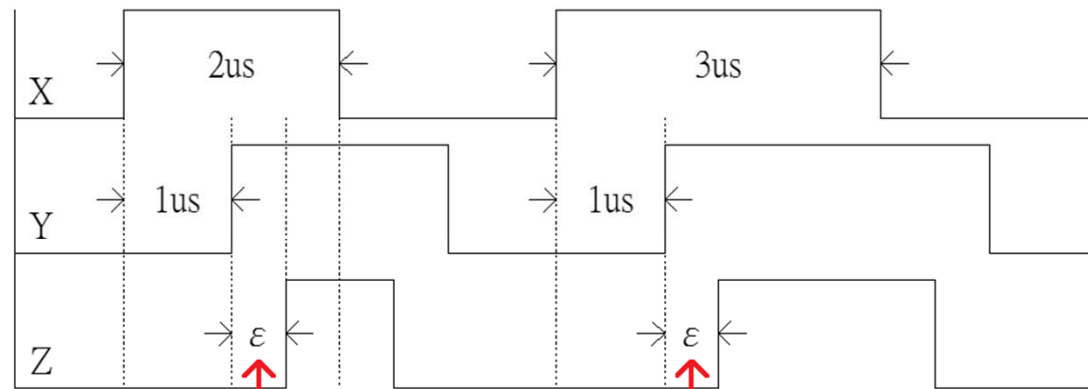 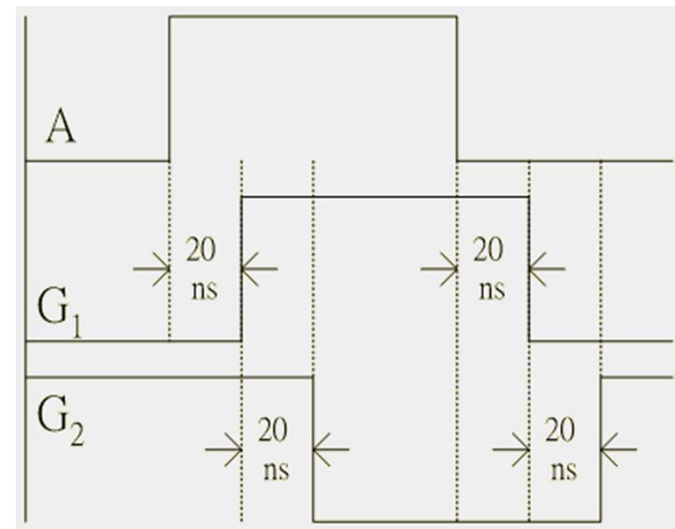  ϵ_1, ϵ_2 may be very small but still exist





propagation delay in AND

Gate Delay and Timing Diagrams (2/2)




AND = 2ns
NOR = 3ns

  


If x signal is complemented, what happen to z ?

Hazard in Combinational Logic (1/5)

 
- What is hazard?
 - **Unwanted** switching transients appearing in the output while the input to a combinational circuit changes
- Types of hazards



(a) Static 1-hazard

 

(b) Static 0-hazard

 


(c) Dynamic hazards


- In K-Map,
 - If any two adjacent 1's are not covered by the same loop, a 1-hazard exists for the transition between the two 1's.

Hazard in Combinational Logic (2/5)

- Let $A=1$ and $C=1$ (Static 1-hazard)

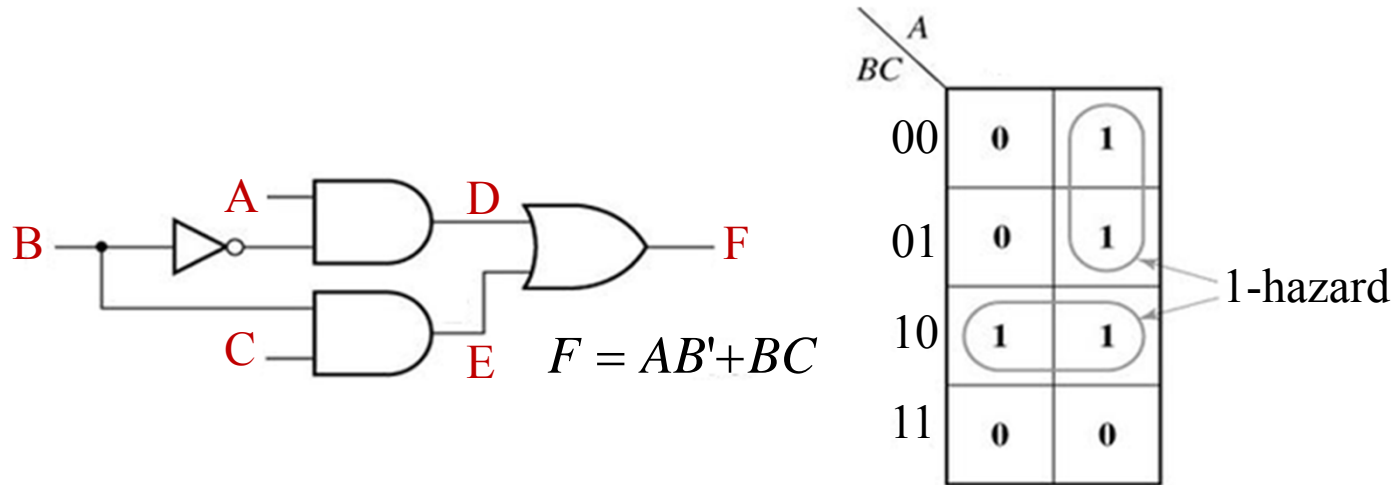

(a) Circuit with a static 1-hazard

 


(b) Timing chart

Hazard in Combinational Logic (3/5)



Circuit with hazard removed



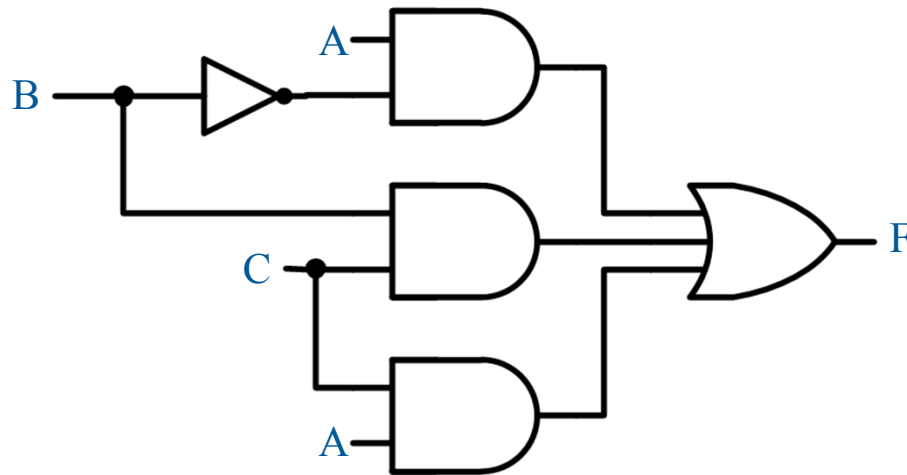


$$F = AB' + BC + AC$$

A \ BC	00	01	11	10
0	0	1	1	0
1	0	1	1	0

Hazard in Combinational Logic (4/5)

  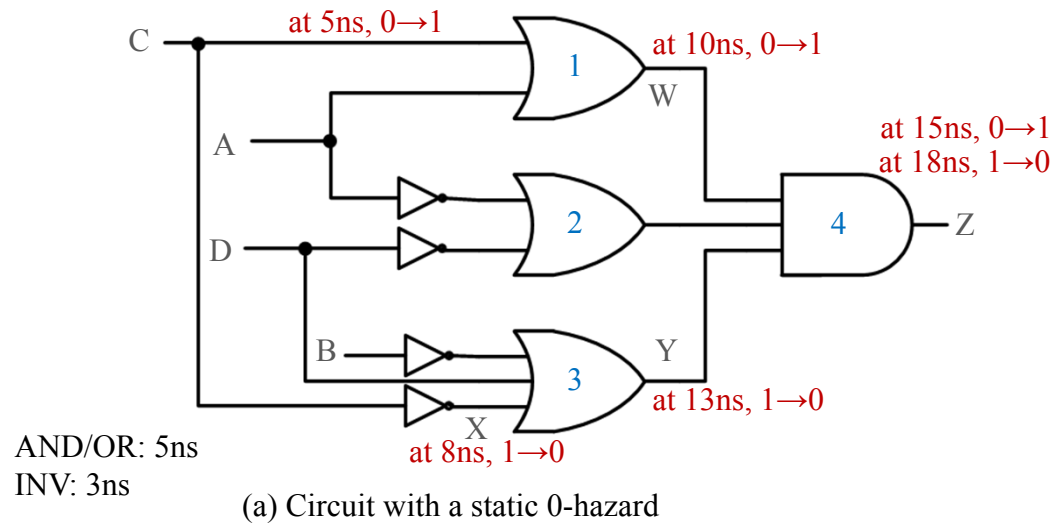- Let $A=0$, $B=1$, and $D=0$ (Static 0-hazard)




Hazard in Combinational Logic (5/5)



Circuit with hazard removed


$$F = (A + C)(A' + D')(B' + C' + D)$$

 


$$F = (A + C)(A' + D')(B' + C' + D)(C + D')(A + B' + D)(A' + B' + C')$$

Simulation and Testing of Logic Circuits (1/4)

 - For simulating logic circuits
 - Specify the circuit components and connections
 - Determine the circuit inputs
 - Observe the circuit outputs
- 4-valued logic simulator
 - 0 (low) 、 1 (high) 、 X (unknown) 、 Z (high impedance)



(a) Simulation screen showing switches

 

(b) Simulation screen with missing gate input

Simulation and Testing of Logic Circuits (2/4)



AND & OR function for 4-valued simulation

•	0	1	X	Z
0	0	0	0	0
1	0	1	X	X
X	0	X	X	X
Z	0	X	X	X

+	0	1	X	Z
0	0	1	X	X
1	1	1	1	1
X	X	1	X	X
Z	X	1	X	X

Simulation and Testing of Logic Circuits (3/4)



- In the logic circuit, a wrong output may be due to
 - Verification
 - Incorrect design
 - Gates connected wrong
 - Wrong input signals to the circuit
 - Testing
 - Defective gates
 - Defective connecting wires

Simulation and Testing of Logic Circuits (4/4)



- Logic circuit with incorrect output
 - $A = B = C = D = 1, F = 0$

