

Unit 9




Multiplexers, Decoders, and Programmable Logic Devices




Outline

- Multiplexers
- Three state buffers
- Decoders
- Encoders
- Read Only Memories (ROMs)
- Programmable logic devices
- Field Programmable Gate Arrays (FPGAs)

Multiplexers (1/5)

   

Unit 9 n control inputs

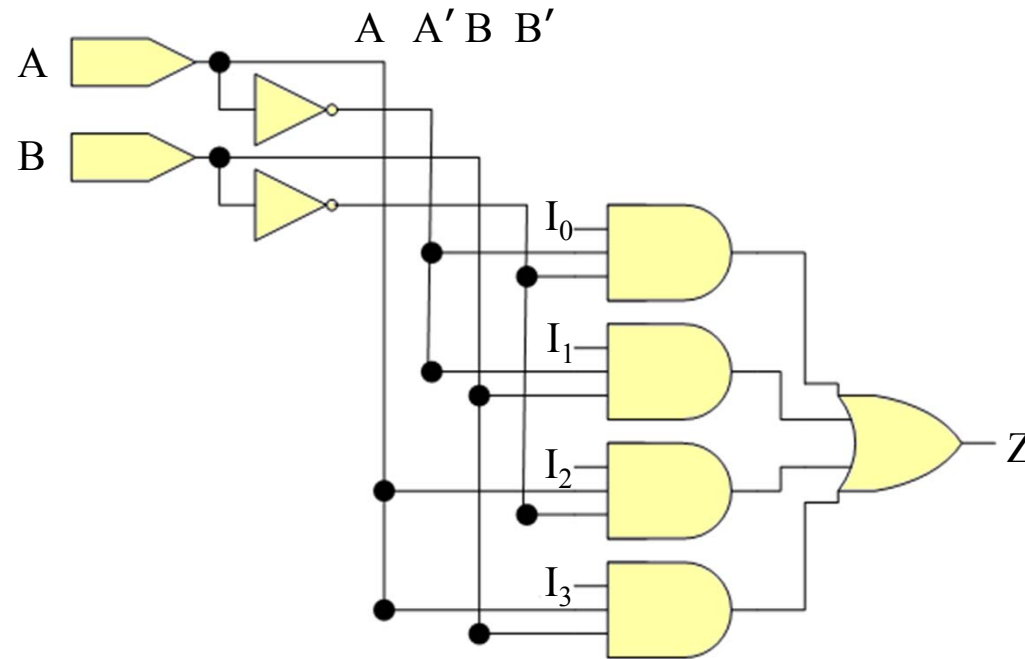

$$4-1: Z = A'B'I_0 + A'BI_1 + AB'I_2 + ABI_3$$


$$8-1: Z = A'B'C'I_0 + A'B'CI_1 + A'BC'I_2 + A'BCI_3$$

$$+ AB'C'I_4 + AB'CI_5 + ABC'I_6 + ABCI_7$$

$$2^n - 1: Z = \sum_{k=0}^{2^n-1} m_k I_k$$

Multiplexers (2/5)

Quad multiplexer to select data

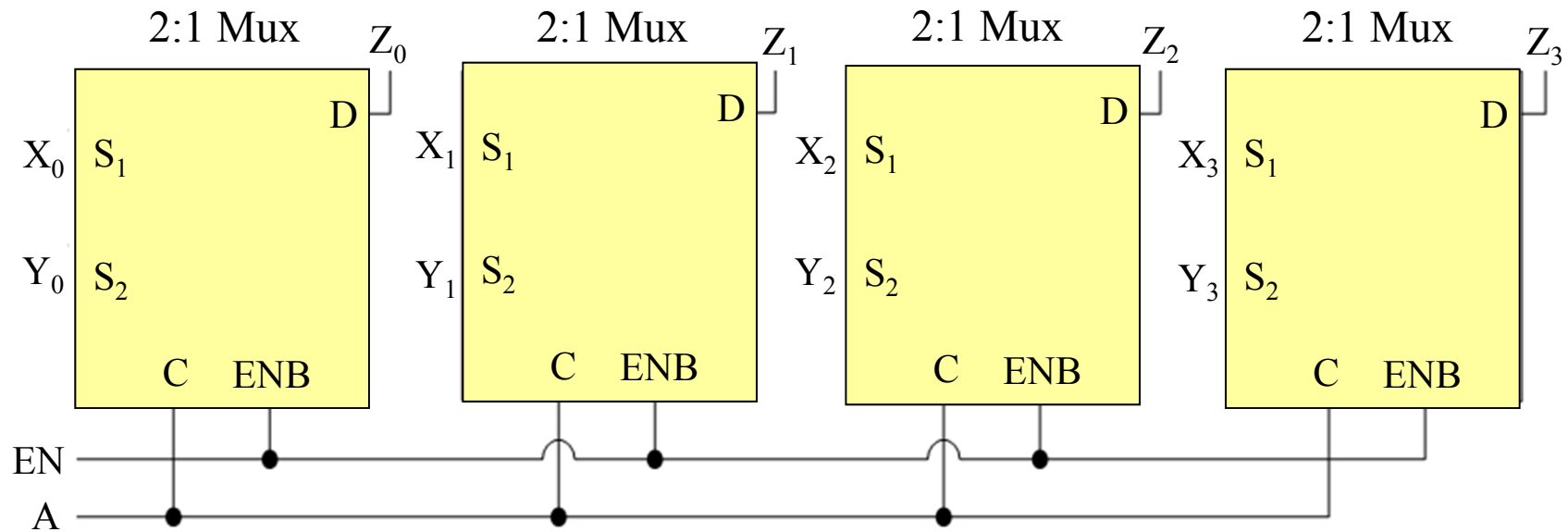


Multiplexers (3/5)

4-to-1 MUX to realize 3-variable function

Ex :
 
$$\begin{aligned}
 F(A, B, C) &= A'B' + AC \\
 &= A'B' + AC(B + B') \\
 &= A'B' \cdot 1 + AB'C + ABC
 \end{aligned}$$




Multiplexers (4/5)


8-to-1 MUX to realize 4-variable function

$$F = A'B'C' + A'BC + ABD' + AC'D' + B'CD$$
 
$$= A'B'C'(D+D') + A'BC(D+D') + AB(C+C')D' + A(B+B')C'D' + (A+A')B'CD$$



 $A'B'C' = 1$
$A'BC = D$
$A'BC' = 0$
$A'BC = 1$
$AB'C' = D'$
$AB'C = D$
$ABC' = D'$
$ABC = D'$



Multiplexers (5/5)

	A	B	C	D	F	
I_0	0	0	0	0	1	1
	0	0	0	1	1	
I_1	0	0	1	0	0	D
	0	0	1	1	1	
I_2	0	1	0	0	0	0
	0	1	0	1	0	
I_3	0	1	1	0	1	1
	0	1	1	1	1	
I_4	1	0	0	0	1	\overline{D}
	1	0	0	1	0	
I_5	1	0	1	0	0	D
	1	0	1	1	1	
I_6	1	1	0	0	1	\overline{D}
	1	1	0	1	0	
I_7	1	1	1	0	1	\overline{D}
	1	1	1	1	0	

$$F = A'B'C'(D+D') + A'BC(D+D') + AB(C+C')D' + A(B+B')C'D' + (A+A')B'CD$$


V_1	V_2	...	V_n	F			
0	0	...	0	0	0	1	1
0	0	...	1	0	1	0	1
				↓	↓	↓	↓
				0	V_n	$\overline{V_n}$	1

$$F = A'B'C' + A'B'CD + A'BC + AB'C'D' + AB'CD + ABC'D' + ABCD'$$


$$= A'B'C' + A'BC + ABD' + AC'D' + B'CD$$

Three-State Buffers (1/4)

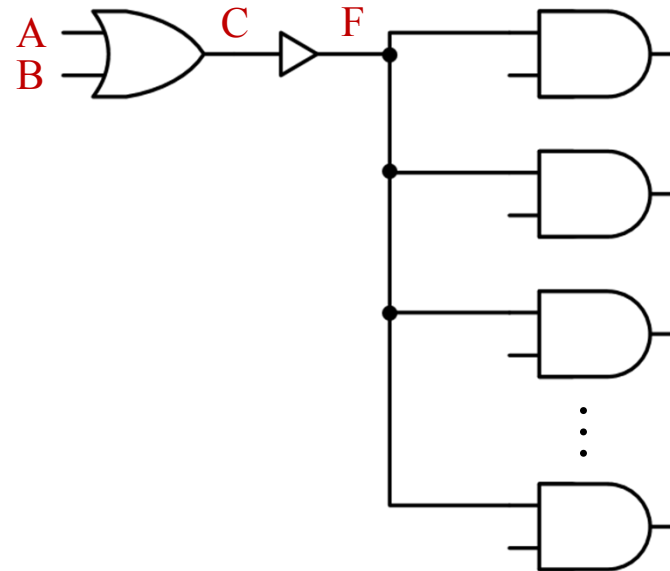Buffers: to increase the driving capability of a gate output



 Tri-state (three-state) Buffers: permits gate outputs to be connected together







Three-State Buffers (2/4)


Truth table

<i>B</i>	<i>A</i>	<i>C</i>
0	0	Z
0	1	Z
1	0	0
1	1	1

Truth Table

    


Data selection using three-state buffers

 

Three-State Buffers (3/4)

Circuits with two three-state buffers

 


S1	S2			
	X	0	1	Z
X	X	X	X	X
0	X	0	X	0
1	X	X	1	1
Z	X	0	1	Z


Three State Buffers (4/4)

Applications

1. Bus

 

2. Chip I/O



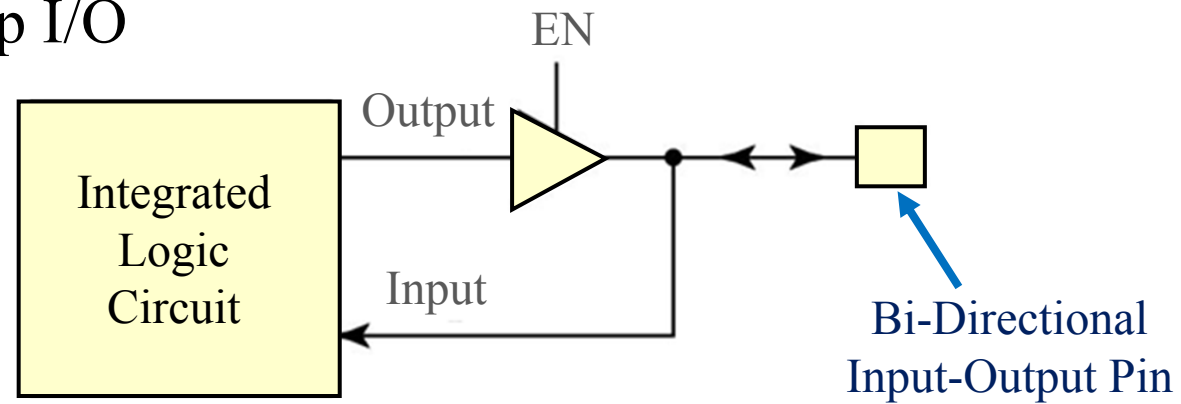


Decoders (1/4)


Generate all of the minterms of inputs

				a	b	c	Y ₀	Y ₁	Y ₂	Y ₃	Y ₄	Y ₅	Y ₆	Y ₇
a	m ₀	y ₀ = a'b'c'	m ₀	0	0	0	1	0	0
	m ₁	y ₁ = a'b'c	m ₁	0	0	1	0	1						:
	m ₂	:	:	0	1	0	:		1					:
b	m ₃	:	:	0	1	1	:			1				:
	m ₄	:	:	1	0	0	:				1			:
	m ₅	:	:	1	0	1	:					1		:
c	m ₆	:	:	1	1	0	:						1	0
	m ₇	y ₇ = abc	m ₇	1	1	1	0	0	1


Decoders (2/4)

   

Decoders (3/4)

 

Outputs

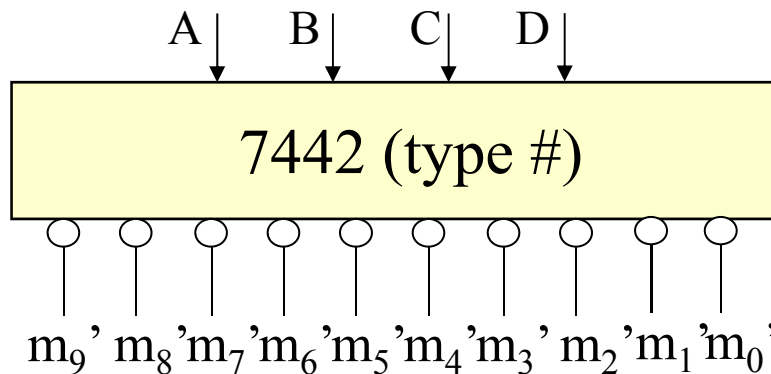


Unit 9

BCD input				Decimal output									
A	B	C	D	0	1	2	3	4	5	6	7	8	9
0	0	0	0	0	1	1	1	1	1	1	1	1	1
0	0	0	1	1	0	1	1	1	1	1	1	1	1
0	0	1	0	1	1	0	1	1	1	1	1	1	1
0	0	1	1	1	1	1	0	1	1	1	1	1	1
0	1	0	0	1	1	1	1	0	1	1	1	1	1
0	1	0	1	1	1	1	1	1	0	1	1	1	1
0	1	1	0	1	1	1	1	1	1	0	1	1	1
0	1	1	1	1	1	1	1	1	1	1	0	1	1
1	0	0	0	1	1	1	1	1	1	1	1	0	1
1	0	0	1	1	1	1	1	1	1	1	1	1	0
1	0	1	0	1	1	1	1	1	1	1	1	1	1
1	0	1	1	1	1	1	1	1	1	1	1	1	1
1	1	0	0	1	1	1	1	1	1	1	1	1	1
1	1	0	1	1	1	1	1	1	1	1	1	1	1
1	1	1	0	1	1	1	1	1	1	1	1	1	1
1	1	1	1	1	1	1	1	1	1	1	1	1	1


Decoders (4/4)

Realization of a multiple output circuit using a decoder
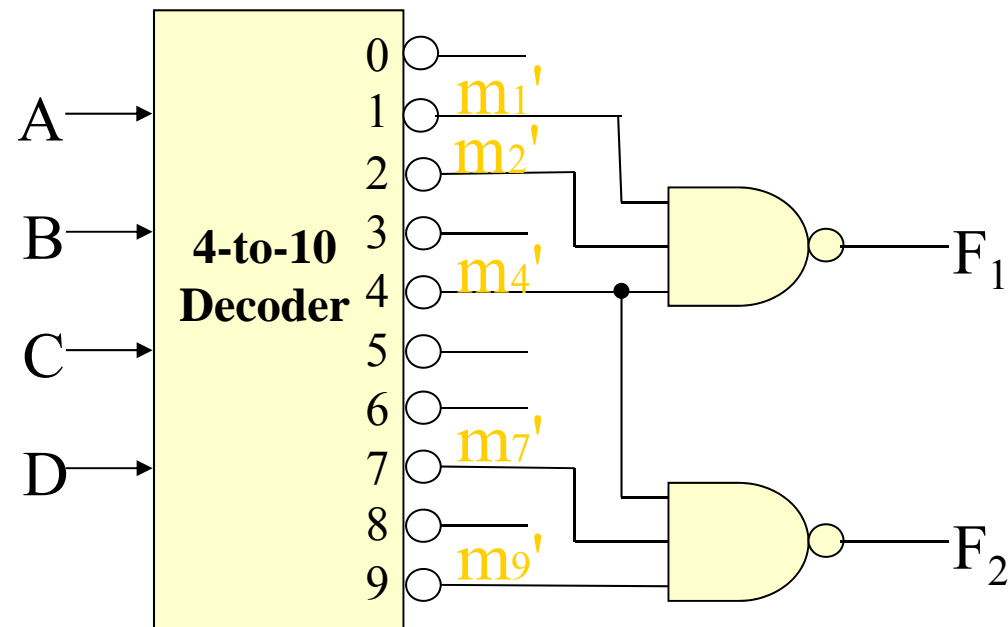
$$F_1 = m_1 + m_2 + m_4 \quad F_2 = m_4 + m_7 + m_9$$



Encoders

 


y0	y1	y2	y3	y4	y5	y6	y7	a	b	c	d
0	0	0	0	0	0	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0	0	0	1
X	1	0	0	0	0	0	0	0	0	1	1
X	X	1	0	0	0	0	0	0	1	0	1
X	X	X	1	0	0	0	0	0	1	1	1
X	X	X	X	1	0	0	0	1	0	0	1
X	X	X	X	X	1	0	0	1	0	1	1
X	X	X	X	X	X	1	0	1	1	0	1
X	X	X	X	X	X	X	1	1	1	1	1

Read Only Memories (1/5)

An LSI circuit to realize multiple output Boolean function(s)

Inputs

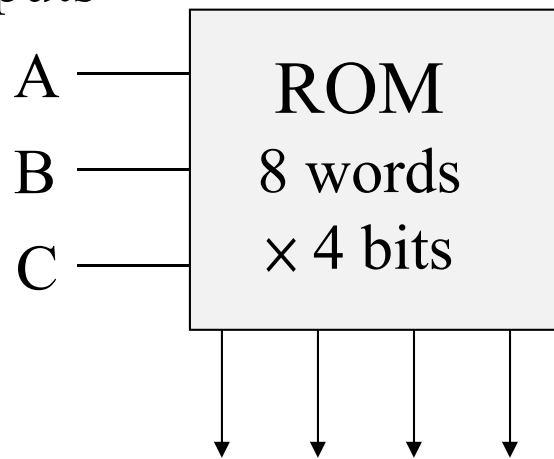

F_0 F_1 F_2 F_3

Outputs

A	B	C	F_0	F_1	F_2	F_3
0	0	0	1	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	0	0
0	1	1	0	1	1	0
1	0	0	0	1	1	0
1	0	1	1	1	1	0
1	1	0	0	0	1	1
1	1	1	1	1	1	1

Stored
in ROM
(2^3 words of
4 bits each)

$$F_0 = m_0 + m_1 + m_5 + m_7$$


$$F_1 = m_2 + m_3 + m_4 + m_5 + m_7$$

$$F_2 = m_0 + m_1 + m_3 + m_4 + m_5 + m_6 + m_7$$

$$F_3 = m_6 + m_7$$

Read Only Memories (2/5)




General Form

 

n inputs	m outputs
	$F_0 \quad \dots \quad \dots \quad \dots \quad F_{m-1}$
$0 \quad \dots \quad 0 \quad 0$	$0 \quad 0 \quad \dots \quad 1 \quad 0$
$0 \quad \dots \quad 0 \quad 1$	$\vdots \quad \quad \quad \quad \quad \quad \vdots$
$\vdots \quad \quad \quad \quad \quad \quad \vdots$	$\vdots \quad \quad \quad \quad \quad \quad \vdots$
$\vdots \quad \quad \quad \quad \quad \quad \vdots$	$\vdots \quad \quad \quad \quad \quad \quad \vdots$
$\vdots \quad \quad \quad \quad \quad \quad \vdots$	$\vdots \quad \quad \quad \quad \quad \quad \vdots$
$\vdots \quad \quad \quad \quad \quad \quad \vdots$	$\vdots \quad \quad \quad \quad \quad \quad \vdots$
$1 \quad \dots \quad 1 \quad 1$	$1 \quad 0 \quad \dots \quad 1 \quad 0$

} 2^n words




Read Only Memories (3/5)

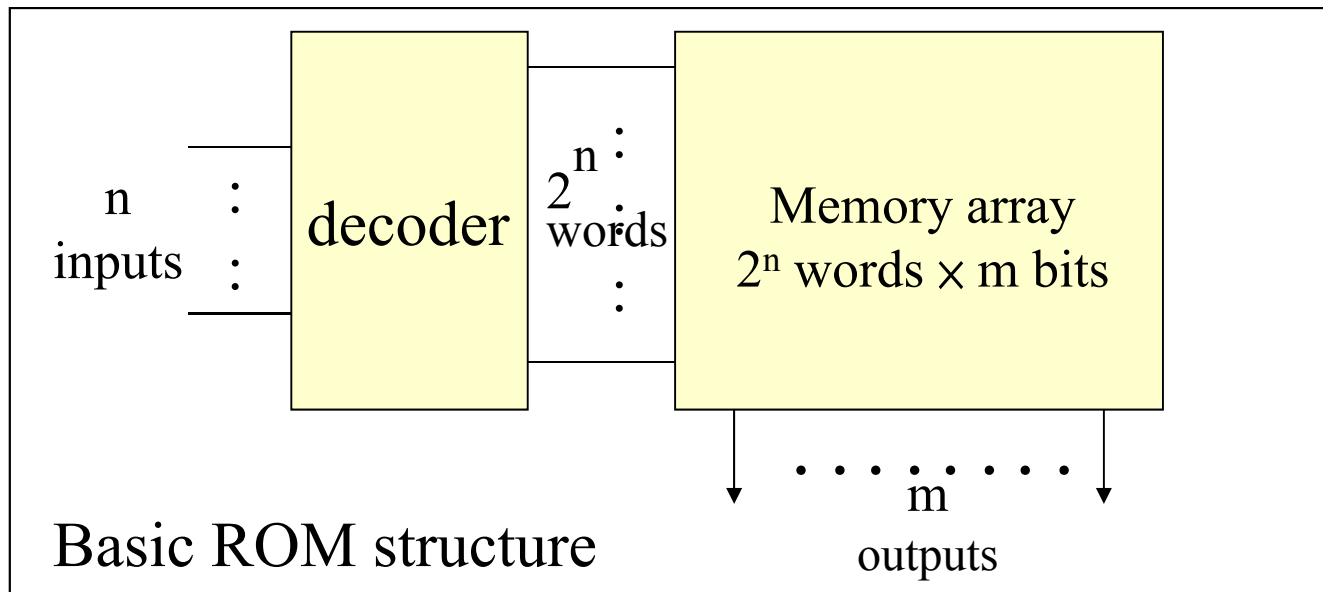  

Read Only Memories (4/5)

ROM as logic devices (use decoder and diodes)

A	B	C	F_0	F_1	F_2	F_3
0	0	0	1	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	1	1
0	1	1	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	1	0	1	1	1	1
1	1	1	0	1	0	1

   


$$F_0 = m_0 + m_1 + m_4 + m_6$$

Read Only Memories (5/5)

$$F_0 = \sum m(0,1,4,6) \quad F_1 = \sum m(2,3,4,6,7)$$
 
$$F_2 = \sum m(0,1,2,6) \quad F_3 = \sum m(2,3,5,6,7)$$






- (1) Use “mask” to program ROM
- (2) EPROM (Erasable Programmable) UV light
- (3) EEPROM (Electrically Erasable)

Programmable Logic Devices (1/7)

Various kinds: PLA , PAL

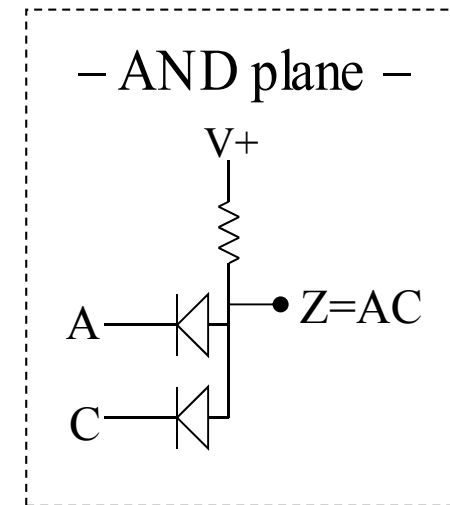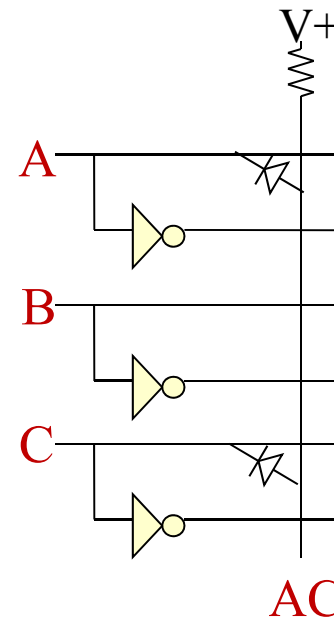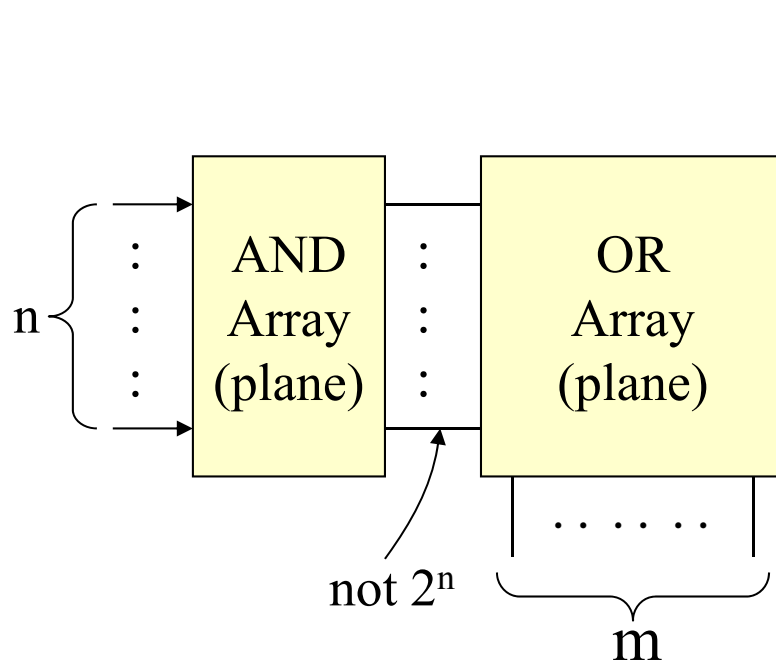PLAs: $n \times m$ realizes m functions with n inputs



2-level SOP implementation

ROM directly implements truth table

If any of A, C is not activated,



$A = \text{GND}$ or $C = \text{GND}$

i.e., $A = 0$ or $C = 0$

$Z=0$


Programmable Logic Devices (2/7)

	A	B	C	F ₀	F ₁	F ₂	F ₃
A'B'	0	0	-	1	0	1	0
AC'	1	-	0	1	1	0	0
B	-	1	-	0	1	0	1
BC'	-	1	0	0	0	1	0
AC	1	-	1	0	0	0	1

  

Programmable Logic Devices (3/7)

Equivalent AND - OR Array

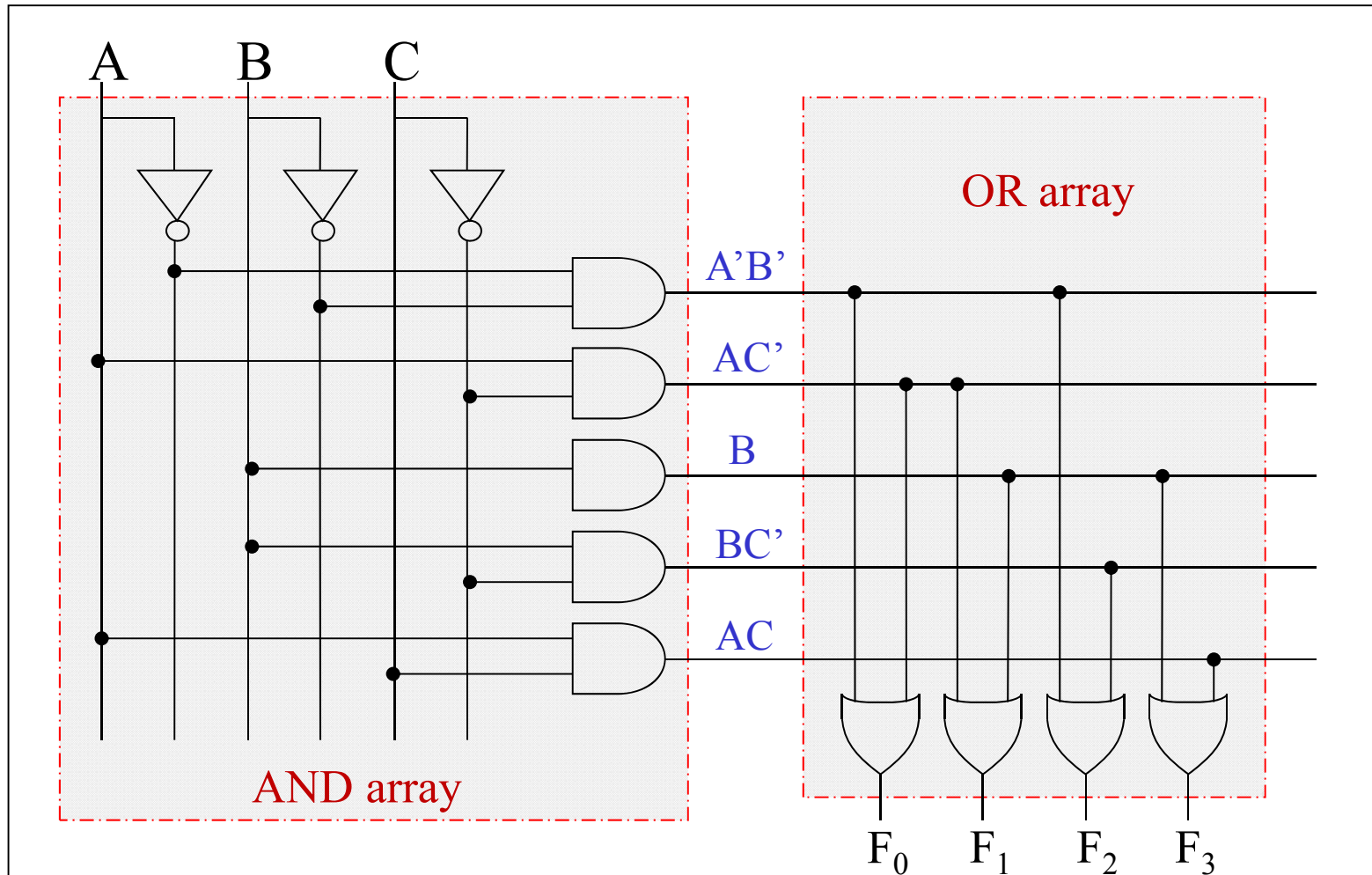

Programmable Logic Devices (4/7)

Example

$$F_1 = \sum m(2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$$

$$F_2 = \sum m(2, 3, 5, 6, 7, 10, 11, 14, 15)$$

$$F_3 = \sum m(6, 7, 8, 9, 13, 14, 15)$$

Minimized multiple output expressions (using K-Map)

$$F_1 = a'bd + abd + ab'c' + b'c$$


$$F_2 = c + a'bd$$

$$F_3 = bc + ab'c' + abd$$

	a	b	c	d	F ₁	F ₂	F ₃
	0	1	–	1	1	1	0
	1	1	–	1	1	0	1
<i>PLA table</i>	1	0	0	–	1	0	1
	–	0	1	–	1	0	0
	–	–	1	–	0	1	0
	–	1	1	–	0	0	1

Programmable Logic Devices (5/7)

a	b	c	d	F ₁	F ₂	F ₃
0	1	–	1	1	1	0
1	1	–	1	1	0	1
1	0	0	–	1	0	1
–	0	1	–	1	0	0
–	–	1	–	0	1	0
–	1	1	–	0	0	1

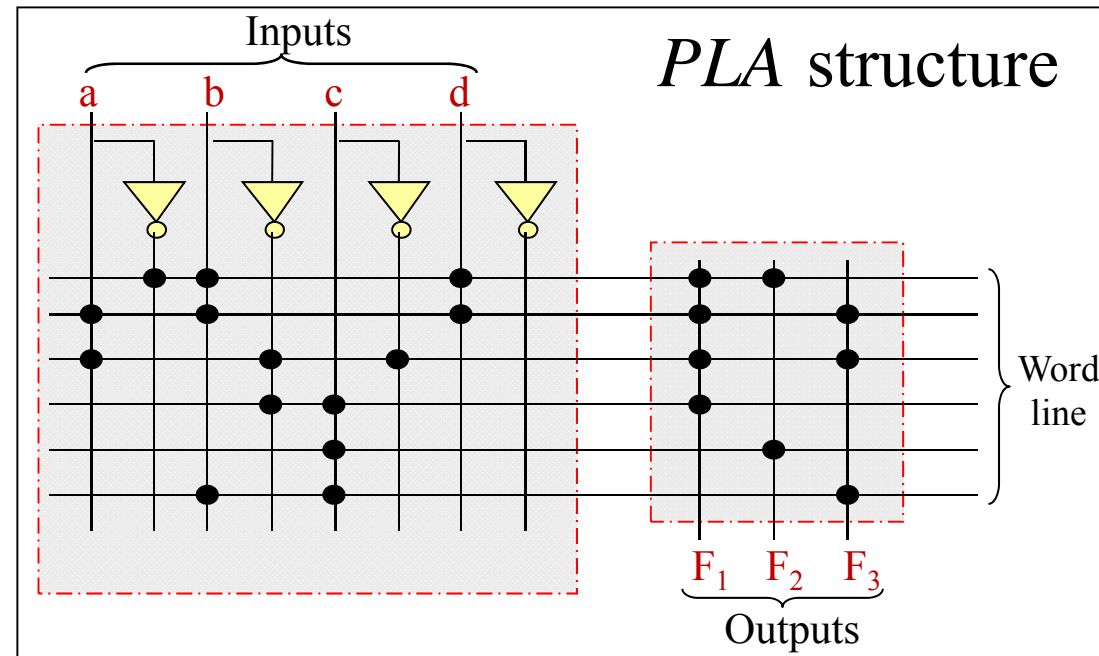

a b c d = 0 1 1 1

row 1,5,6 selected, $\Rightarrow F_1 = 1(1\text{st}) + 0(5\text{th}) + 0(6\text{th}) = 1$

$$F_2 = 1 + 1 + 0 = 1$$

$$F_3 = 0 + 0 + 1 = 1$$

= 0 0 0 1

no rows selected, $\Rightarrow F_1F_2F_3 = 000$

= 1 0 0 1

row 3 selected, $\Rightarrow F_1F_2F_3 = 101$



© Mask programmable PLA

© Field programmable PLA

Programmable Logic Devices (6/7)

PALs: $n \times m$ realizes m functions with n inputs

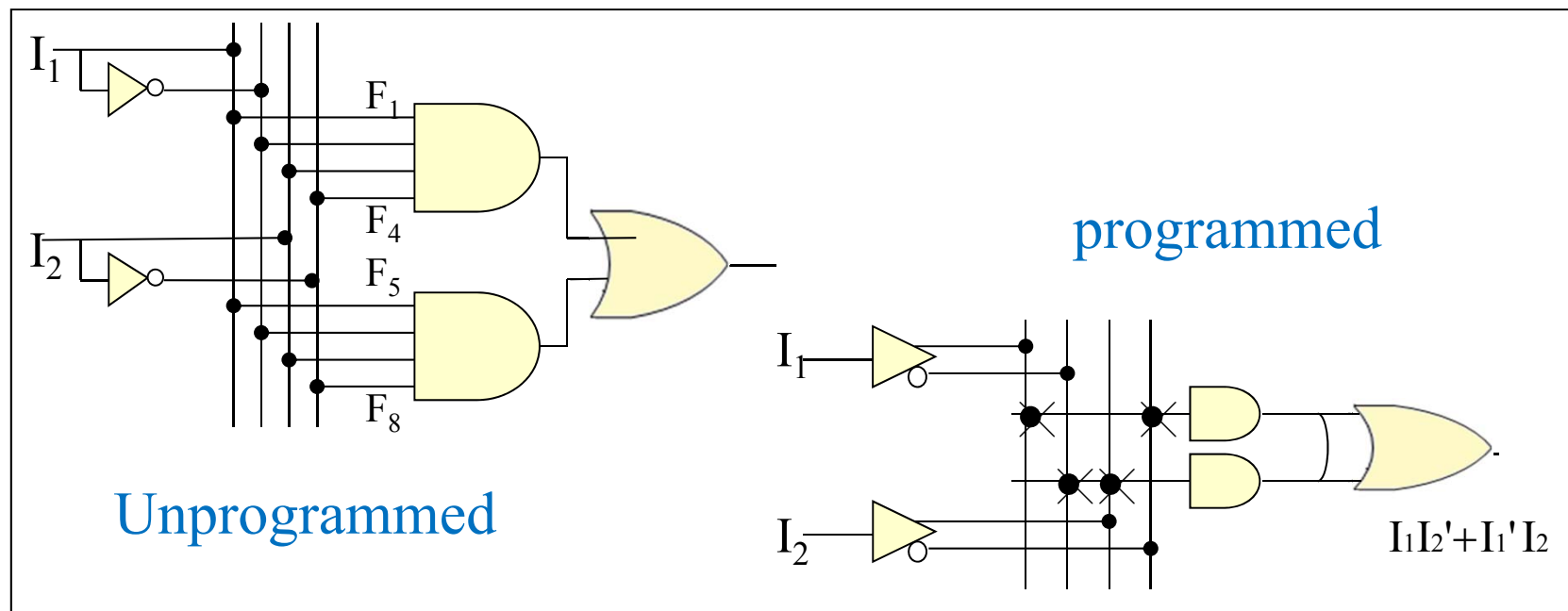 A special case of PLA: $\left(\begin{array}{l} \text{AND array programmable} \\ \text{OR array NOT programmable} \end{array} \right)$



Programmable Logic Devices (7/7)




PLD Summary

	AND Array	OR Array
PLA	Programmable	Programmable
PAL	Programmable	Fixed
ROM	Fixed	Programmable
Not Programmable	Fixed	Fixed

Field Programmable Gate Arrays (1/4)

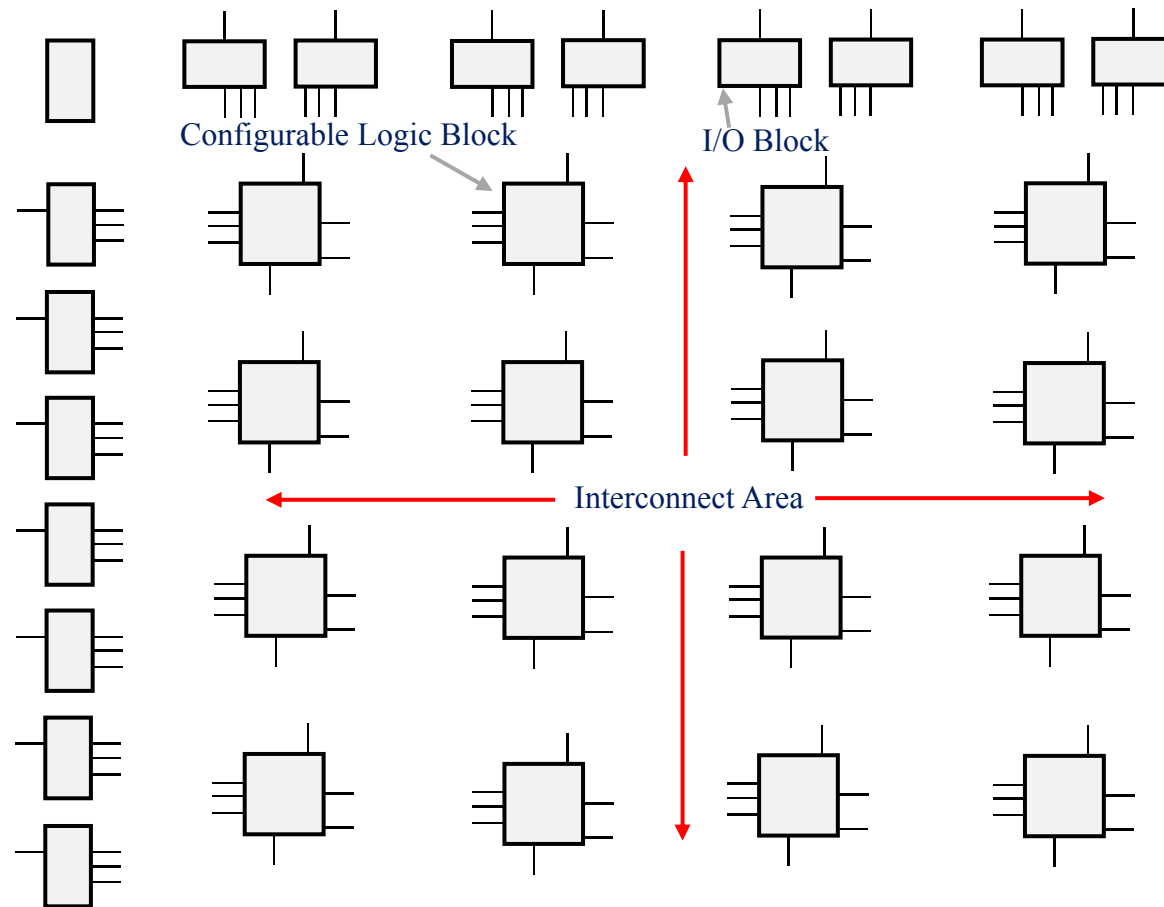
An IC that contains an array of identical logic cells with programmable interconnections



Layout of a typical FPGA

Field Programmable Gate Arrays (2/4)

CLB: configurable logic block

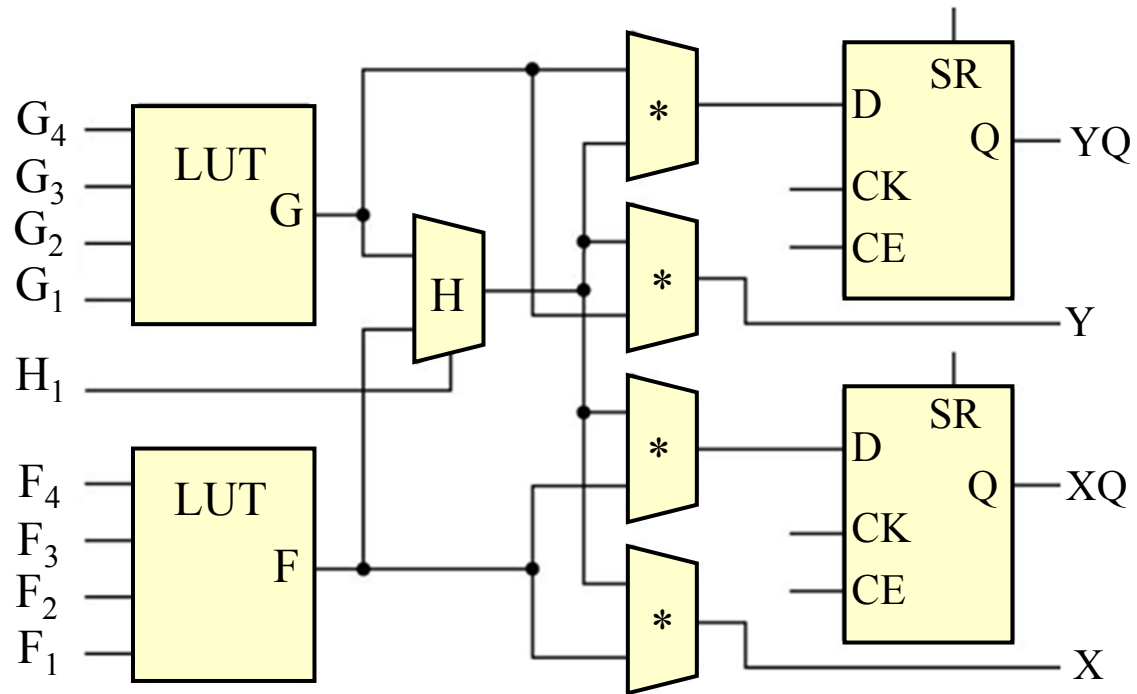

* = Programmable MUX

Field Programmable Gate Arrays (3/4)

Decomposition of switching functions

Shannon's expansion theorem

$$F(x_1, x_2, \dots, x_{i-1}, x_i, x_{i+1}, \dots) \\ = x_i' F_0 + x_i F_1$$

		ab			
		00	01	11	10
cd	00	1	1	1	1
	01			1	1
	11	1	1	1	
	10	1			


F

		a=0		a=1	
		00	01	11	10
cd	00	1	1	1	1
	01			1	1
	11	1	1	1	
	10	1			


F_0
 F_1

Field Programmable Gate Arrays (4/4)

 Realization of 5- and 6-variable functions with 4-variable function generators (FG)



(a) 5-variable function

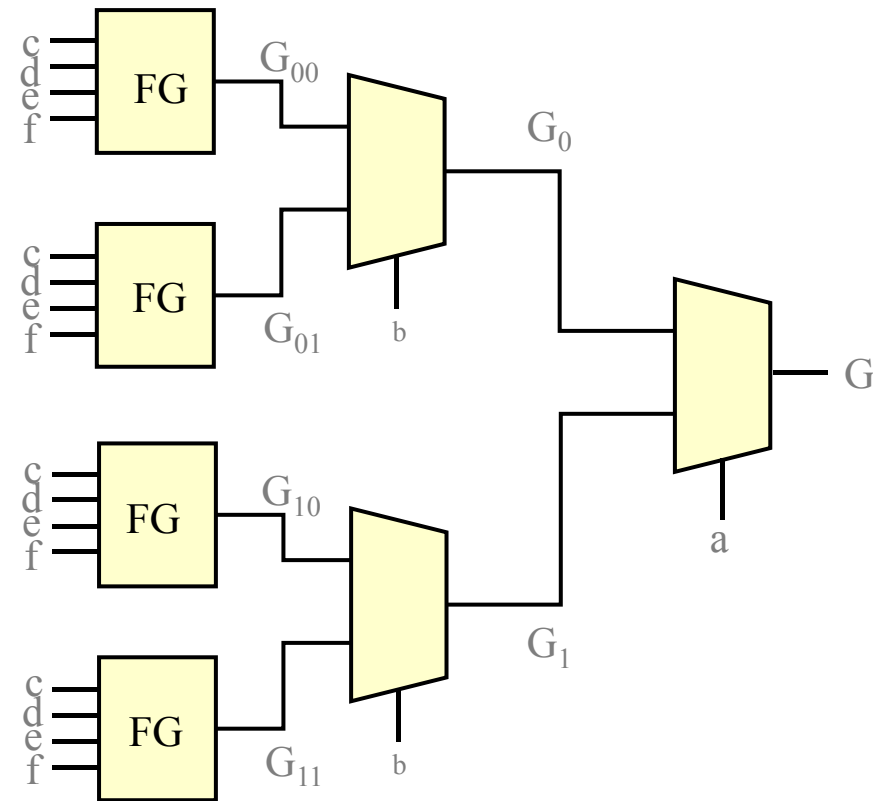

(b) 6-variable function