

# Introduction to Verilog HDL

---

# Hardware Description Language (HDL)

---



- High-Level Programming Language
- Special constructs to model microelectronic circuits
  - Describe the operation of a circuit at various levels of abstraction
    - Behavioral
    - Functional (Register Transfer Level)
    - Structural
  - Express the concurrency of circuit operation
  - Serve as input to synthesis



# Major HDLs

---

- Verilog HDL
  - Started by Gateway in 1984
  - Became open to public by Cadence in 1990
  - IEEE standard 1364 in 1995
  - Slightly better at gate/transistor level
  - Language style close to C/C++
  - Pre-defined data type, easy to use
- VHDL
  - Started by VHSIC project in 1980s
  - IEEE standard 1076 in 1987, IEEE 1164 in 1993
  - Slightly better at system level
  - Language style close to Ada/Pascal
  - User-defined data type, more flexible
- Equally effective, personal preference


# Why HDL

---



- Facilitate a top-down design methodology using synthesis
  - Design at a high implementation-independent level
  - Delay decision on implementation details
  - Easily explore design alternatives
  - Automatically map high-level description to a technology-specific implementation
- Provides greater flexibility
  - Reuse earlier design components
  - Move designs between multiple vendors and tools

# Typical Design Flow

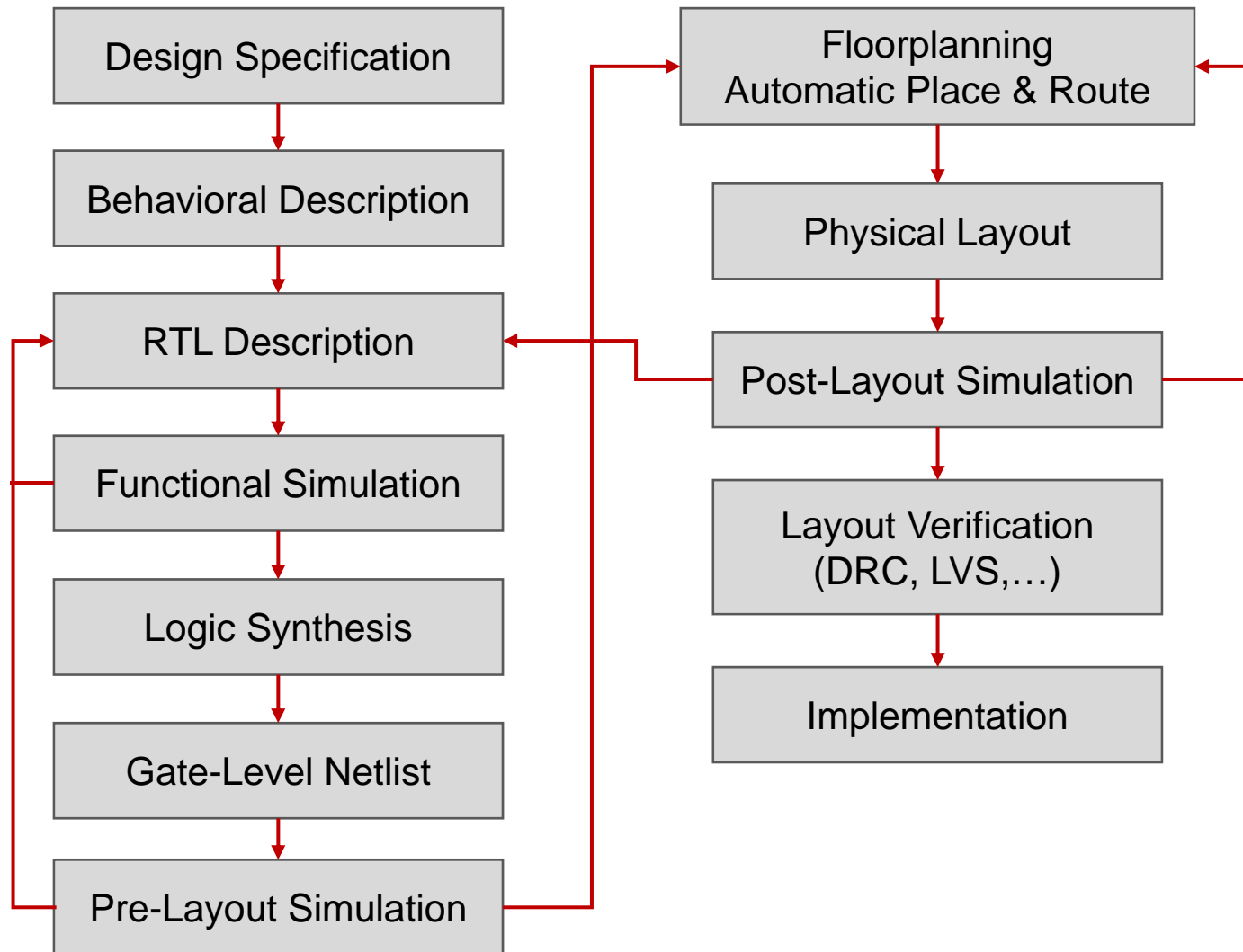


# Verilog-Supported Levels of Abstraction

---




- Behavioral
  - Describes a system by the flow of data between its functional blocks
  - Defines signal values when they change
- Functional or Register Transfer Level (RTL)
  - Describes a system by the flow of data and control signals between and within its functional blocks
  - Defines signal values with respect to a clock
- Structural
  - Describes a system by connecting predefined components
  - Uses technology-specific, low-level components when mapping from an RTL description to a gate-level netlist, such as during synthesis.

# Block Diagram & Schematic

 

block diagram

 

schematic

# Modules



- A module is the basic building block in Verilog
  - Every module starts with the keyword **module**, has a name, and ends with the keyword **endmodule**
- A module can be
  - A design block
  - A simulation block, i.e., a testbench

```
module add_1 (. . .);  
    . . .  
    . . .  
endmodule
```



# Module Ports




- Module ports describe the input and output terminals of a module
  - Listed in parentheses after the module name
  - Declared to be **input**, **output**, or **inout** (bi-directional)

```
module add_1 (sum, a, b, c_in, c_out);
output sum;
input a;
input b;
input c_in;
output c_out;

// output sum, c_out;
// input a, b, c_in;
. . .
. . .
endmodule
```

# Structural Level Description

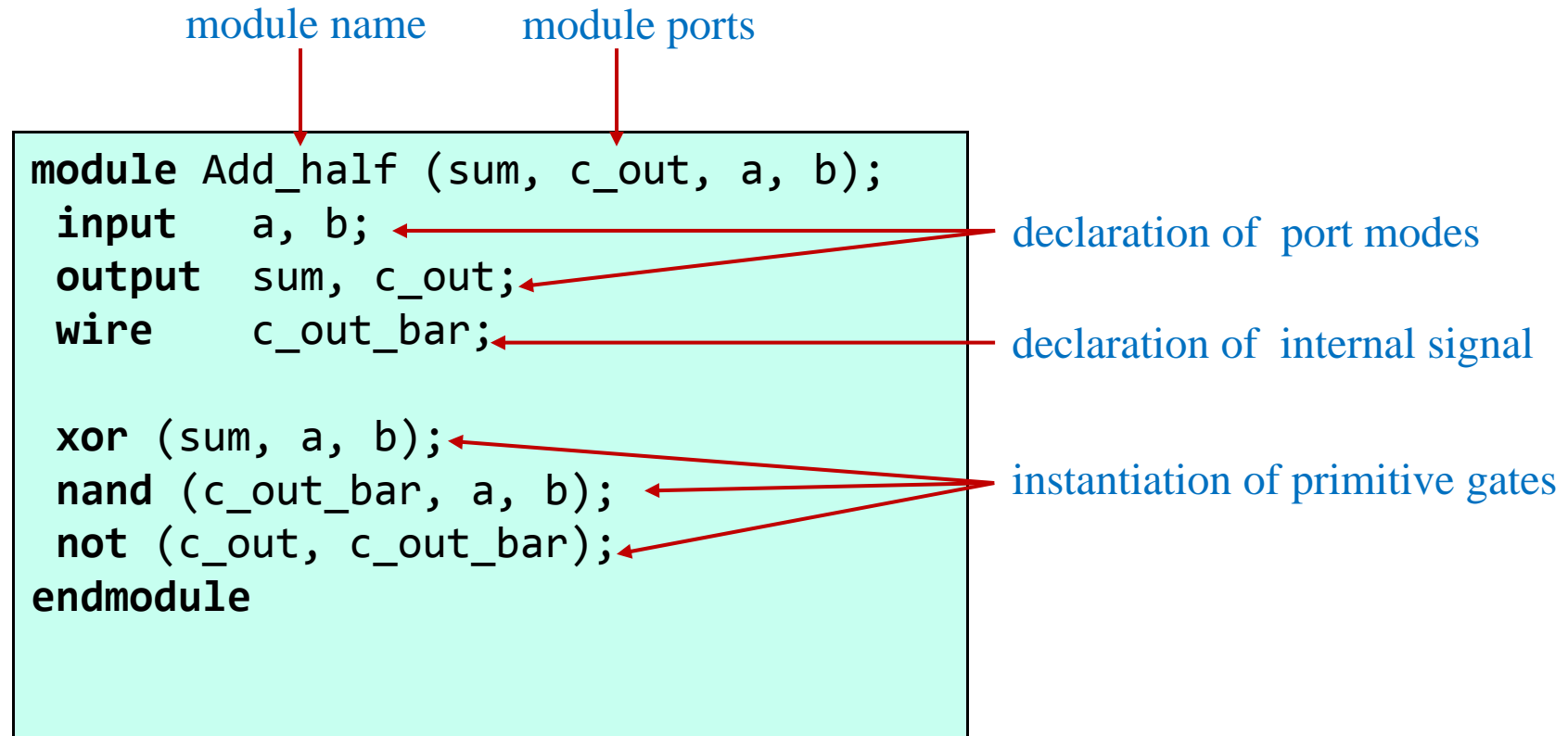

*Note: All bold-faced items are Verilog keywords*


# Predefined Primitives

---



- Combinational logic gates
  - **and, nand**
  - **or, nor**
  - **xor, xnor**
  - **buf, not**


# Full Adder

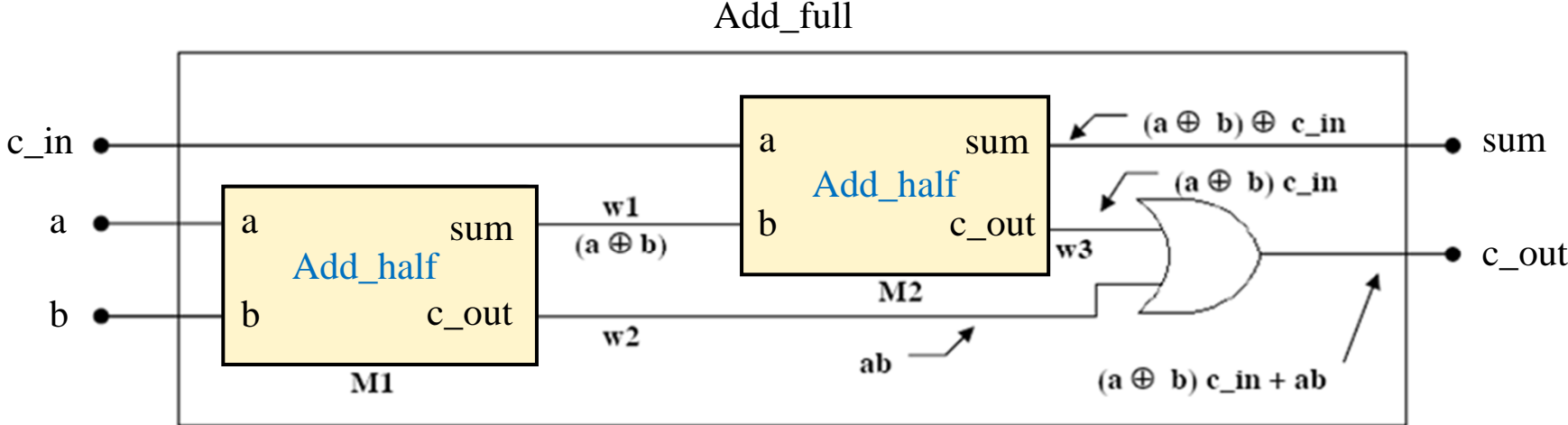

```

module Add_full (sum, c_out, a, b, c_in); //parent module
  input a, b, c_in;
  output c_out, sum;
  wire w1, w2, w3;
  module instance name
  Add_half M1 (w1, w2, a, b); //child module
  Add_half M2 (sum, w3, w1, c_in); //child module
  or (c_out, w2, w3); //primitive instantiation
endmodule
  
```

# Hierarchical Description

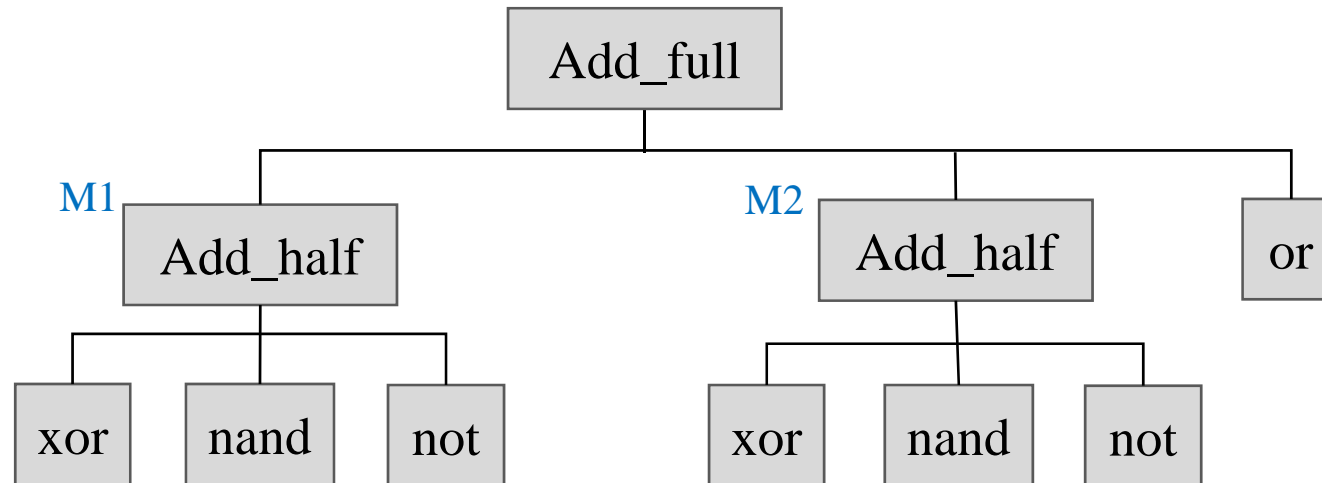

*Nested module instantiation is the mechanism for hierarchical decomposition of a design*

# RTL Level Description

---



- An RTL model provides sufficient architectural details that a synthesis tool can construct the circuit

```
module add_1 (sum, a, b, c_in, c_out);  
output sum, c_out;  
input  a, b, c_in;  
  
    assign {c_out, sum} = a + b + c_in;  
  
endmodule
```

# The Behavioral Level

---



- Describes the behavior of a design without implying any specific internal architecture
  - High level constructs, such as @, **case**, **if**, **repeat**, **wait**, **while**, etc
  - Testbench
  - Limited support by synthesis tools
- The difference between a behavioral model and an RTL model and an RTL model is not always clear
  - whether synthesizable or not

# Behavioral Level Description




```
module Add_half (sum, c_out, a, b);  
input a, b;  
output sum, c_out;  
reg sum, c_out;  
  
always@(a or b)  
begin  
    sum = a ^ b; //exclusive or  
    c_out = a & b; //and  
end  
endmodule
```

procedural statements



# Behavioral Description of D F/F

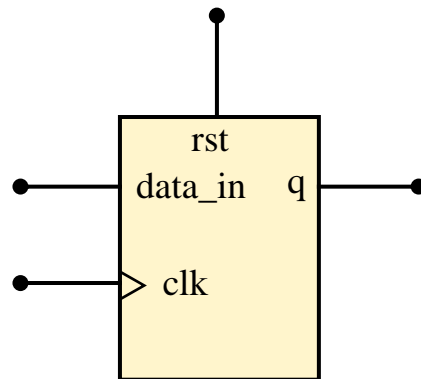

block  
diagram

```
module Flip_flop (q, data_in, clk, rst);  
  input  data_in, clk, rst;  
  output q;  
  reg q;  
  
  always @ (posedge clk) ← declaration of  
    begin                                     synchronous  
      if(rst == 1) q=0;                       behavior  
      else q = data_in;  
    end  
endmodule
```

# Variables

---



- Nets “wire”: structural connectivity
- Registers “reg”: abstraction of storage (may or may not be physical storage)
- Both nets and registers are informally called signals, and may be either scalar or vector

# Logic Values

---




- Verilog signal values
  - 0: logical 0, or a FALSE condition
  - 1: logical 1, or a TRUE condition
  - x: an unknown value
  - z: a high impedance condition
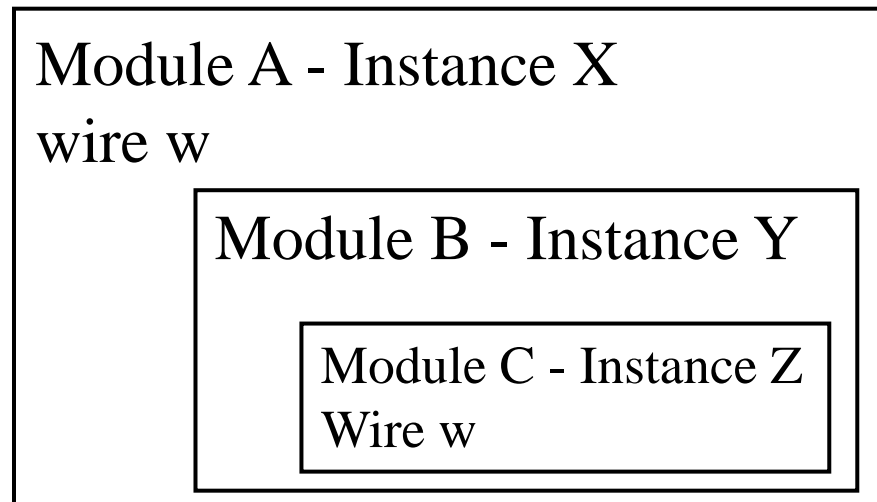
# Hierarchical De-Referencing



- To reference a variable defined inside an instantiated module
- Supported by a variable's hierarchical path name
  - X.w
  - X.Y.Z.w



# if...else



- **else** is paired with nearest **if** when ambiguous (use **begin...end** in nesting to clarify)

```
(a) if (a < b) c = d + 1;      (d) if (a < b)
                                sum = sum + 1;
(b) if (a < b);
                                else
(c) if (k == 1)
                                sum = sum + 2;
    begin : A_block
        sum_out = sum_reg;
        c_out = c_reg;
    end
```

# Example



```
module mux4_PCA (a, b, c, d, select, y_out);
    input          a, b, c, d;
    input [1:0]    select;
    output         y_out;
    reg           y_out;

    always @ (select or a or b or c or d)
        if (select == 0) y_out = a; else
        if (select == 1) y_out = b; else
        if (select == 2) y_out = c; else
        if (select == 3) y_out = d; else
        y_out = 1'bx;
endmodule
```

# case



- Require complete bitwise match
- Example:

```
...
  always @ (a or b or c or d or
select)
  begin
    case (select)
      0: y = a;
      1: y = b;
      2: y = c;
      3: y = d;
      default: y = 1'bx;
    endcase
  end
```

# Netlist of Primitives




```
module or_nand_1 (enable, x1,
x2, x3, x4, y);


input enable, x1, x2, x3, x4;
output y;
wire w1, w2, w3;

or (w1, x1, x2);
or (w2, x3, x4);
or (w3, x3, x4); // redundant
nand (y, w1, w2, w3, enable);

endmodule
```

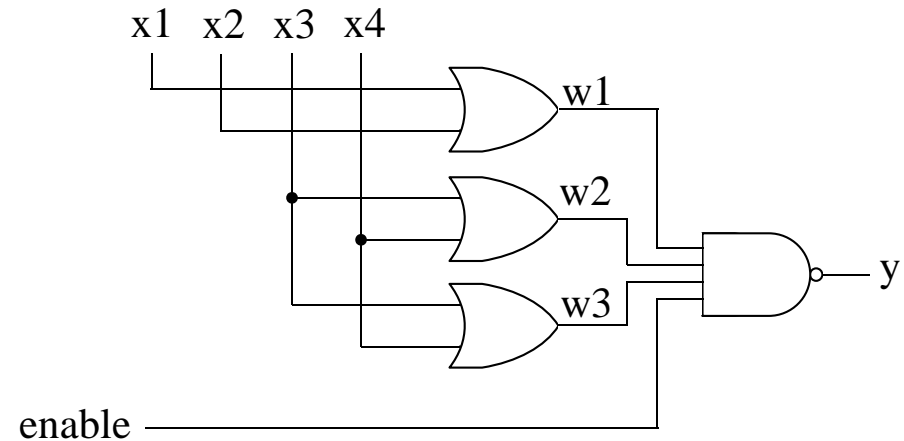

(a) Pre-optimized circuit

 



(b) Circuit synthesized from the circuit in (a)



# Continuous Assignment



```
module or_nand_2 (enable, x1, x2, x3, x4, y);  
input  enable, x1, x2, x3, x4;  
output y;  
  
assign y = ~(enable & (x1 | x2) & (x3 | x4));  
endmodule
```

  


Synthesis result

# Behavioral Description



```
module or_nand_3 (enable, x1, x2, x3, x4, y);
  input          enable, x1, x2, x3, x4;
  output        y;
  reg           y;

  always @ (enable or x1 or x2 or x3 or x4)
    begin
      y = ~(enable & (x1 | x2) & (x3 | x4));
    end
endmodule
```

 

Circuit synthesized from a behavioral description



# Avoid Latch Inference (1/2)

- When if or case statements are used without specifying outputs in all possible conditions, a latch will be created

```
always@(enable or data)
  if(enable)
    q = data;
```

```
always@(enable or data)
begin
  if(enable)
    q = data;
  else
    q = 0;
end
```

Specify all output values

 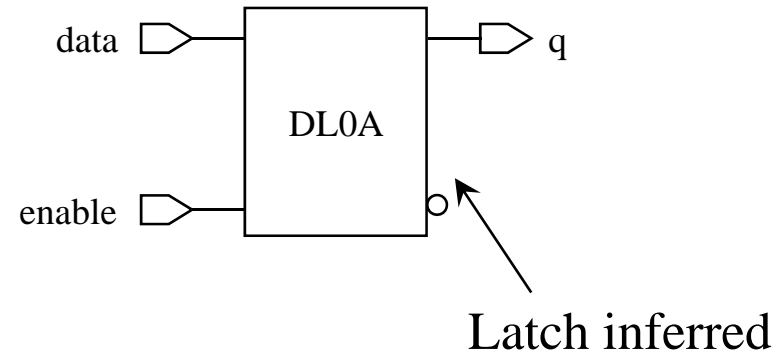


## Avoid Latch Inference (2/2)



```
always@(a or b or c)
case(a)
  2'b11 : e = b;
  2'b10 : e = ~c;
endcase
```

No latch

 

```
always@(a or b or c)
case(a)
  2'b11 : e = b;
  2'b10 : e = ~c;
  default : e = 0;
endcase
```

Add a default  
statement

result in a latch

# Code Converter (1/3)



- A code converter transforms one representation of data to another
- Ex: A BCD to excess-3 code converter
  - BCD: Binary Coded Decimal
  - Excess-3 code: the decimal digit plus 3

Truth Table for Code Converter Example

Input BCD				Output Excess-3			
A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	1	1
0	0	0	1	0	1	0	0
0	0	1	0	0	1	0	1
0	0	1	1	0	1	1	0
0	1	0	0	0	1	1	1
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0

# Code Converter (2/3)




- Equations: (share terms to minimize cost)

$$W = A + BC + BD = A + B(C + D)$$


$$X = \bar{B}C + \bar{B}D + B\bar{C}\bar{D} = \bar{B}(C + D) + B\bar{C}\bar{D}$$

$$Y = CD + \bar{C}\bar{D} = \overline{C \oplus D}$$

$$Z = \bar{D}$$

 

$$W = A + BC + BD$$

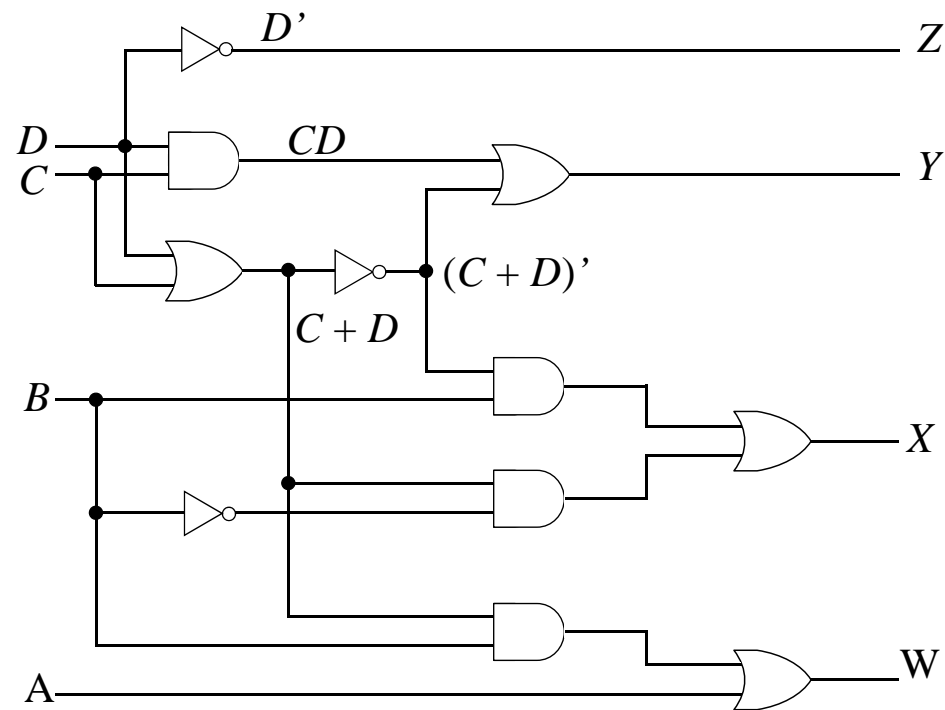

# Code Converter (3/3)



- **RTL style**

```
assign W = A|(B&(C|D));  
assign X = ~B&(C|D)|(B&~C&~D);  
assign Y = ~(C^D);  
assign Z = ~D;
```

- **Behavior style**


```
assign ROM_in = {A, B, C, D};  
assign {W, X, Y, Z} = ROM_out;  
always @(ROM_in) begin  
    case (ROM_in)  
        4'b0000: ROM_out = 4'b0011;  
        4'b0001: ROM_out = 4'b0100;  
        ...  
        4'b1001: ROM_out = 4'b1100;  
        default: ROM_out = 4'b0000;  
    endcase  
end
```

# Decoder (1/2)



- A decoder is to generate the  $2^n$  (or fewer) minterms of  $n$  input variables
- Ex: a 3-to-8 line decoder

Inputs			Outputs							
x	y	z	$D_0$	$D_1$	$D_2$	$D_3$	$D_4$	$D_5$	$D_6$	$D_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

 



## Decoder (2/2)



- **Behavior style 1**


```
input x, y, z;
output [7:0] D;
reg [7:0] D;
always @(x or y or z) begin
    case ({x, y, z})
        3'b000: D = 8'b00000001;
        3'b001: D = 8'b00000010;
        ...
        3'b111: D = 8'b10000000;
        default: D = 8'b0;
    endcase
end
```

- **Behavior style 2**

```
input x, y, z;
output [7:0] D;
wire [2:0] addr;
reg [7:0] D;
assign addr = {x, y, z};
always @(addr) begin
    D = 8'b0;
    D[addr] = 1;
end
```
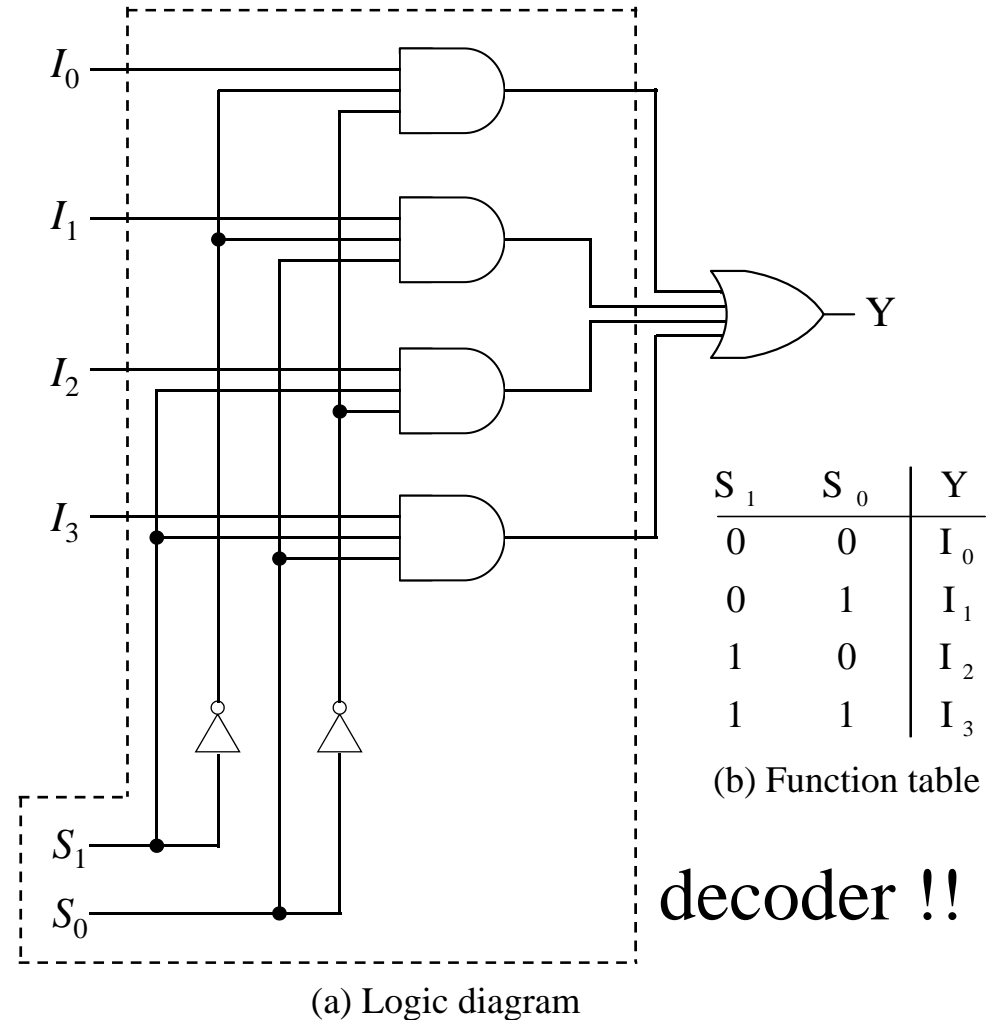
# Multiplexer (1/2)

- A multiplexer uses  $n$  selection bits to choose binary info. from a maximum of  $2^n$  unique input lines



## Multiplexer (2/2)

- **Behavior style 1**

```
input [1:0] S;  
input [3:0] I;  
output Y;  
reg Y;  
always @(S or I) begin  
    case (S)  
        2'b00: Y = I[0];  
        2'b01: Y = I[1];  
        2'b10: Y = I[2];  
        2'b11: Y = I[3];  
        default: Y = 0;  
    endcase  
end
```


- **Behavior style 2**

```
input [1:0] S;  
input [3:0] I;  
output Y;  
reg Y;  
always @(S or I)  
    begin  
        Y = I[S];  
    end
```

# BCD Adder (1/2)

C detects whether the binary sum is greater than 9 (1001)

$$C = K + Z_8Z_4 + Z_8Z_2$$

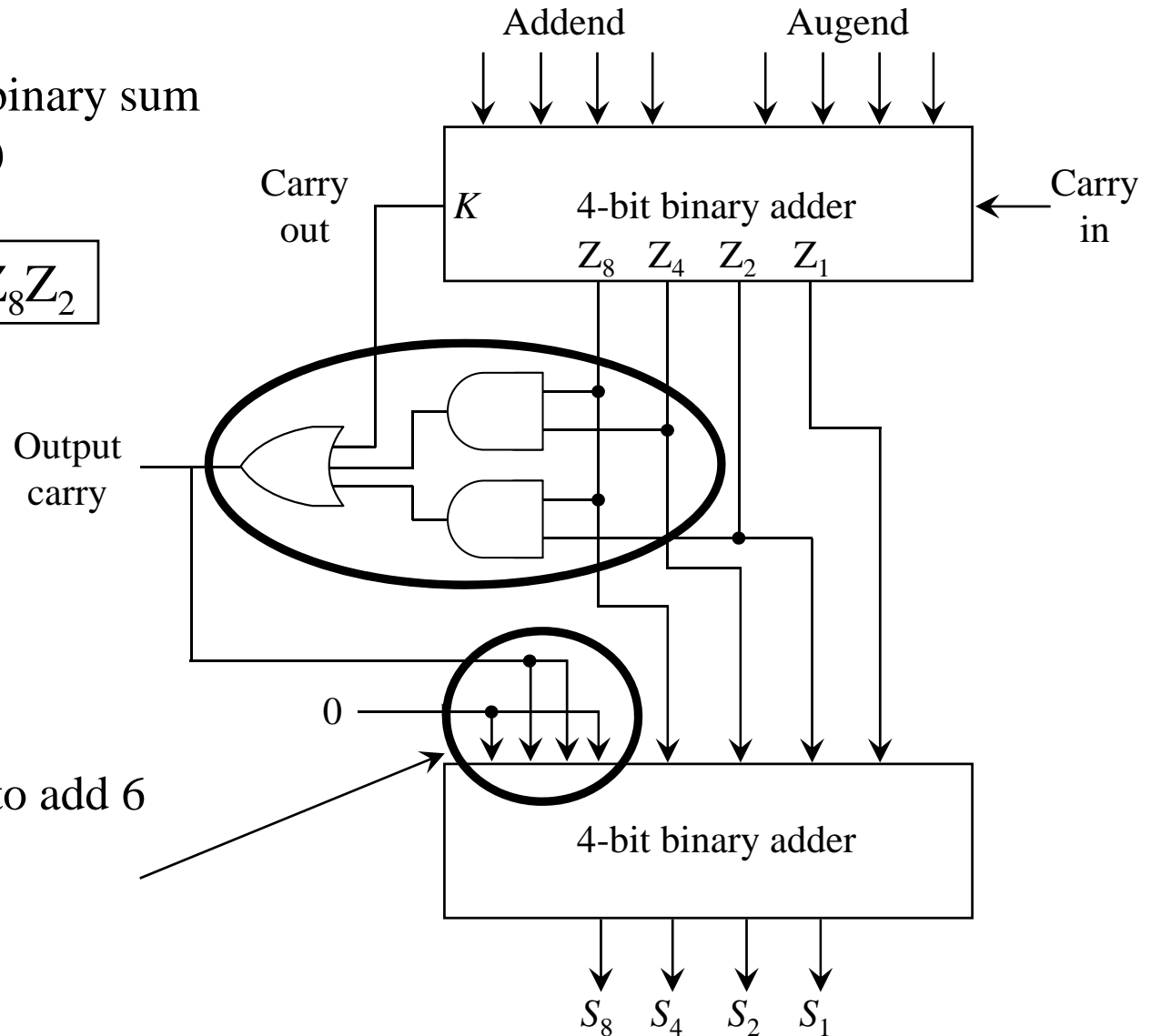

If C=1, it is necessary to add 6 (0110) to binary sum



## BCD Adder (2/2)

---

```
module bcd_add (S, Cout, A, B, Cin);
    input [3:0] A, B;
    input Cin;
    output [3:0] S;
    output Cout;
    reg [3:0] S;
    reg Cout;

    always @(A or B or Cin) begin
        {Cout, S} = A + B + Cin;
        if (Cout != 0 || S > 9) begin
            S = S + 6;
            Cout = 1;
        end
    end
end
endmodule
```



# Latch Inference

---

- **Incompletely specified wire in the synchronous section**
- **D latch**

```
always @(enable or data)
    if (enable)
        q = data;
```

# More Latches




- **D latch with gated enable**

```
always @(enable or d or gate)
```

```
  if (enable & gate)
```

```
    q = d;
```

 

- **D latch with asynchronous reset**

```
always @(reset or data or enable)
```

```
  if (reset)
```

```
    q = 1'b0;
```

```
  else if (enable)
```

```
    q = data;
```



# Flip-Flop Inference

- **Wire (port) assigned in the synchronous section**

```

module FF_PN (Clock, X1, X2, Y1, Y2);
    input Clock;
    input X1, X2;
    output Y1, Y2;
    reg Y1, Y2;
    always @(posedge Clock)
        Y1 = X1;
    always @(negedge Clock)
        Y2 = X2;
endmodule

```

  





# Modeling Reset

## Synchronous reset


```
always@(posedge clk)
  if(!reset) q=1'b0;
  else q=data;
```
 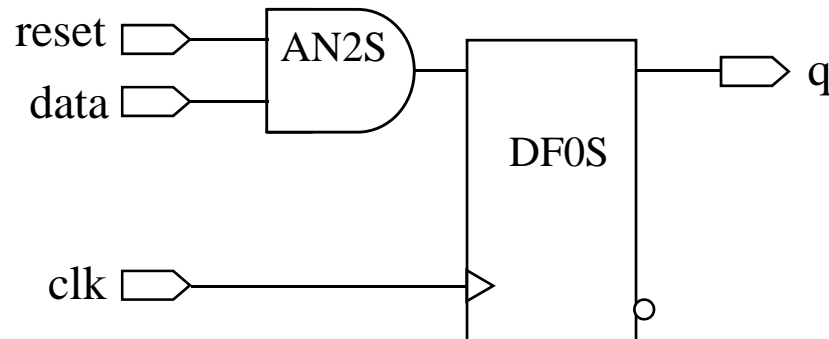
## Asynchronous reset


```
always@(posedge clk or negedge reset)
  if(!reset) q=1'b0;
  else q=data;
```



# The Simplest Shift Register

 

4-Bit Shift Register

 

Symbol

# Procedural Assignment

---



- Assign value to registers
- Blocking procedural assignment
  - Use “=”
  - An assignment is completed before the next assignment starts
- Non-blocking procedural assignment
  - Use “<=”
  - Assignments are executed in parallel

# Examples



```
a = 1;  
b = 0;  
...  
a <= b;      // use b=0  
b <= a;      // use a=1
```

```
a = 1;  
b = 0;  
...  
a = b;      // use b=0  
b = a;      // use a=0
```

```
a = 1;  
b = 0;  
...  
b <= a;      // use a=1  
a <= b;      // use b=0
```

```
a = 1;  
b = 0;  
...  
b = a;      // use a=1  
a = b;      // use b=1
```

# HDL Modeling for Shift Reg.



- **Blocking assignment**

```
assign S0 = D;
always @(posedge CLK) begin
  if (reset) begin
    A=0; B=0; C=0; D=0;
  end
  else if (shift) begin
    D = C;
    C = B;
    B = A;
    A = SI;
  end
end
end
```

↑  
order dependent

- **Non-blocking assignment**

```
assign S0 = D;
always @(posedge CLK)begin
  if (reset) begin
    A<=0; B<=0; C<=0; D<=0;
  end
  else if (shift) begin
    A <= SI;
    C <= B;
    D <= C;
    B <= A;
  end
end
end
```


↑  
can be any order

# Non-Blocking Assignment

```
always@(posedge clk)
begin
    outa<=in;
    outb<=outa;
    outc<=outb;
end
```

=
 
```
always@(posedge clk)
    outa=in;
always@(posedge clk)
    outb=outa;
always@(posedge clk)
    outc=outb;
```



# References

---



- T.-C. Wang, course slides of “HDL and Synthesis”, Dept. of CS, NTHU.
- C.-N. Liu, course slides of “Digital System Design”, Dept. of EE. NCU.