

# Unit 7

---

## Multi-Level Gate Circuits / NAND and NOR Gates





# Outline

---

- Multi-level gate circuits
- NAND and NOR gates
- 2-level NAND and NOR circuits
- Multi-level NAND and NOR circuits
- Multi-output circuit realization

# Multi-Level Gate Circuits (1/2)

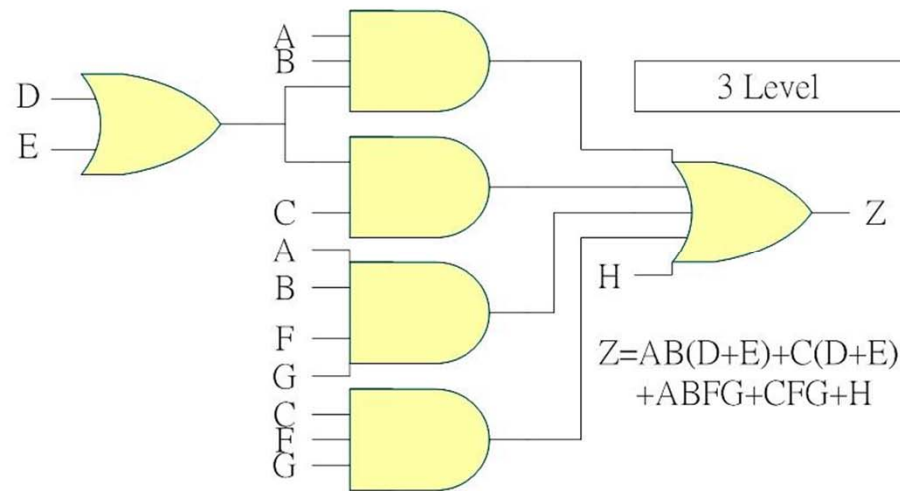 


AND – OR: 2 – level SOP  
 OR – AND: 2 – level POS  
 OR – AND – OR: 3 – level  
 circuit of AND and OR  
 ⇒ no particular ordering

1. Gate input number & delay determine level
2. Factoring to accomplish different level
 
## Multi-Level Gate Circuits (2/2)

$$f(a, b, c, d) = \sum m(1, 5, 6, 10, 13, 14)$$



Using K-Map Method:

$$f = a'c'd + bc'd + bcd' + acd' \dots\dots(1)$$

2-level AND-OR gate network

$\Rightarrow$  2 levels, 5 gates, 16 gate inputs

Factoring:

$$f = c'd(a' + b) + cd'(a + b) \dots\dots(2)$$

$\Rightarrow$  3 levels, 5 gates, 12 gate inputs

or use POS:

$$f = (c+d)(a'+b+c)(c'+d')(a+b+c') \dots(3)$$

$\Rightarrow$  2 levels, 5 gates, 14 gate inputs

or  $f = [c+d(a'+b)][c'+d'(a+b)] \dots(4)$

$\Rightarrow$  4 levels, 7 gates, 14 gate inputs



or  $f = [c+(a'd+bd)][c'+(ad'+bd')] \dots(5)$

$\Rightarrow$  3 levels, 7 gates, 16 gate inputs


# NAND & NOR Gates (1/5)

NAND :


$$F=(ABC)'=A'+B'+C'$$

  


A	B	AB	$\overline{AB}$
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

 


NOR :

 

$$F=(A+B+C)'=A'B'C'$$

 

A	B	A+B	$\overline{A+B}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

 


## NAND & NOR Gates (2/5)

**Functionally Complete Sets of Gates:** A set of logic operations is Functionally Complete, if any Boolean function can be expressed in terms of this set of operations.

{AND, OR, NOT}

{AND, NOT}  $\because \text{OR} = X + Y = (X'Y)'$


can be formed by AND, NOT

 

{OR, NOT}

A functionally complete set of operations must contain NOT


NOT: Realized by NAND or NOR

 


# NAND & NOR Gates (3/5)



## Majority Gate

 

## Minority Gate

 

Odd number of inputs


a	b	c	$F_M$	$F_m$
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

# NAND & NOR Gates (4/5)

3-input minority gates can realize any switching function

$F = B'C' + A'B' + A'C'$

A \ BC	00	01	10	11
0	1	1	1	0
1	0	0	0	0

 

B	C	$F_m$
0	0	1
0	0	1
0	1	1
0	1	0
-----		
1	0	1
1	0	0
1	1	0
1	1	0


  

$\left. \begin{matrix} 0 \\ 0 \\ 1 \end{matrix} \right\}$	$\left. \begin{matrix} 1 \\ 1 \\ 0 \end{matrix} \right\}$	$\left. \begin{matrix} 1 \\ 1 \\ 0 \end{matrix} \right\}$	$\left. \begin{matrix} 0 \\ B \\ C \end{matrix} \right\}$		$(BC)'$
-----					
$\left. \begin{matrix} 1 \\ 1 \\ 1 \end{matrix} \right\}$	$\left. \begin{matrix} 0 \\ 0 \\ 0 \end{matrix} \right\}$	$\left. \begin{matrix} 1 \\ 0 \\ 0 \end{matrix} \right\}$	$\left. \begin{matrix} 1 \\ B \\ C \end{matrix} \right\}$		$(B+C)'$




# NAND & NOR Gates (5/5)



1. Inverter : Let  $C=B=A$

 

3. OR :  $B+C = [ (B+C)' ]'$

 

  2. AND : Let  $A=1$  then  $F_m = B'C'$   
Must invert B & C in advance




# 2-level NAND & NOR Circuits (1/3)




*NAND* & *NOR* : Readily available in IC form

## *DeMorgan's Law*

 


$$(A+B)' = A' B'$$

 


$$(A \cdot B)' = A'+B'$$

or

 


$$(A+B) = (A' B')'$$

 


$$A \cdot B = (A'+ B')'$$

## 2-level NAND & NOR Circuits (2/3)

*Ex1 : AND / OR  $\Rightarrow$  NAND/NAND*

 


*Ex2 : AND / OR  $\Rightarrow$  NOR/NOR*

 


## 2-level NAND & NOR Circuits (3/3)




Ex1: *OR / AND*  $\Rightarrow$  NOR/NOR

 


 
Ex2: *OR / AND*  $\Rightarrow$  NAND/NAND



# Multi-level NAND & NOR Circuits (1/2)

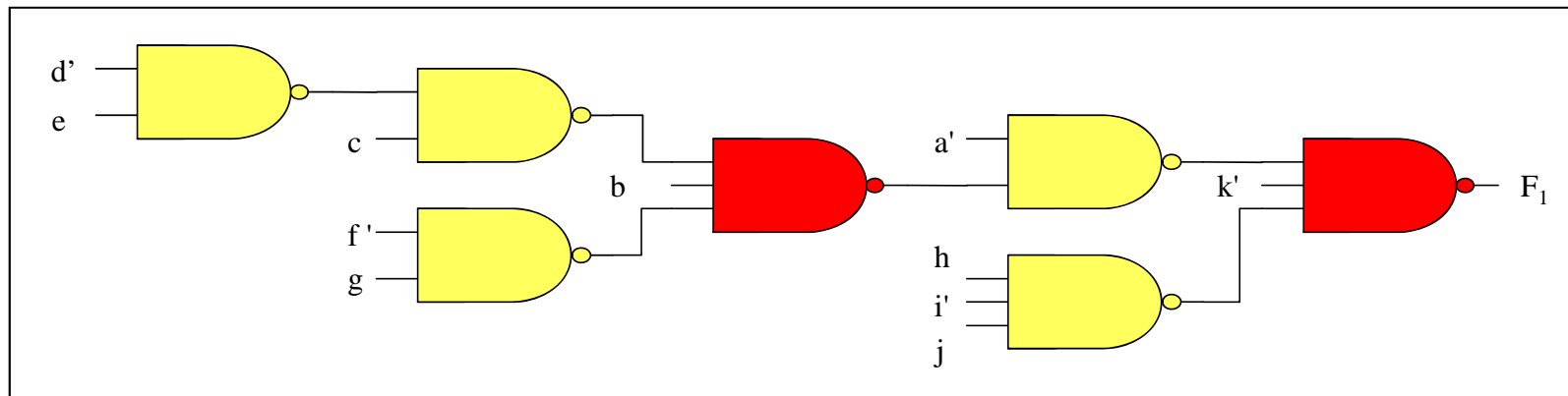  

# Multi-level NAND & NOR Circuits (2/2)

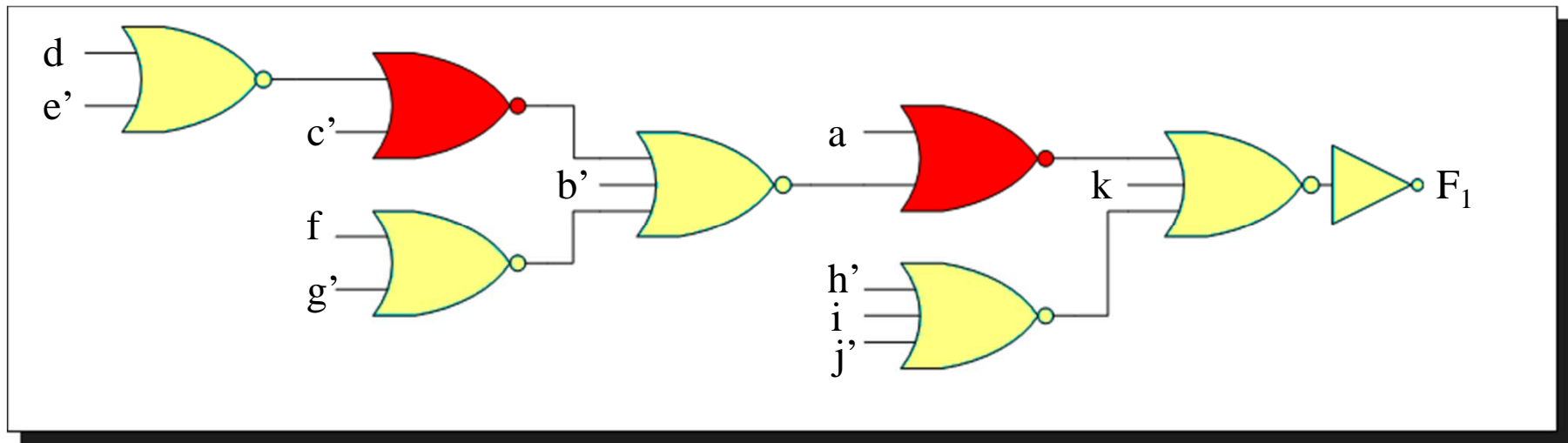 

# Multi-output Circuit Realization (1/11)


$$\begin{aligned}
 \text{Ex: } F_1(A, B, C, D) &= \sum m(11, 12, 13, 14, 15) \\
 F_2(A, B, C, D) &= \sum m(3, 7, 11, 12, 13, 15) \\
 F_3(A, B, C, D) &= \sum m(3, 7, 12, 13, 14, 15)
 \end{aligned}$$

From K-Map


$$F_1 = AB + ACD$$

$$F_2 = ABC' + CD$$


$$F_3 = A'CD + AB$$

 
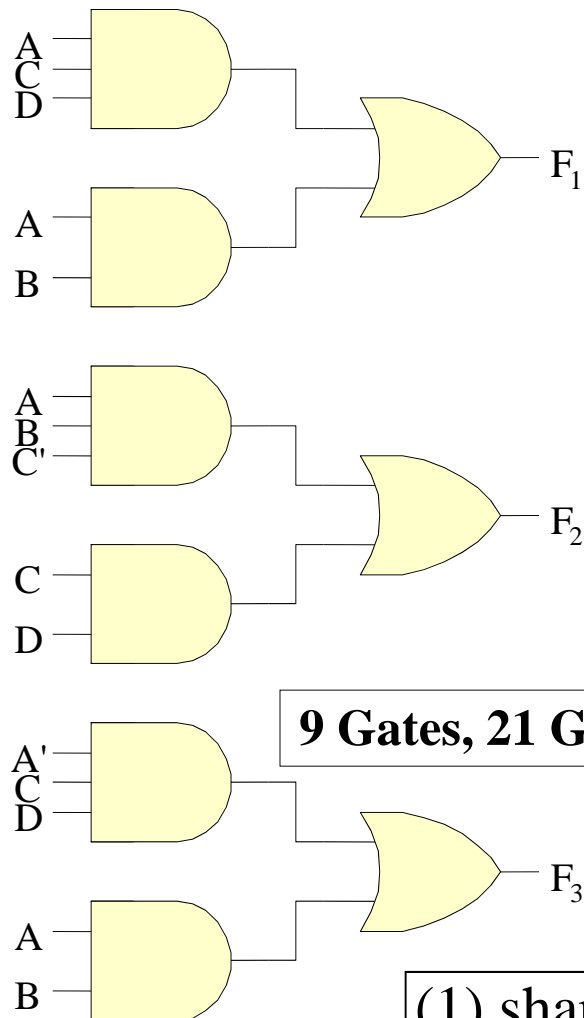
# Multi-output Circuit Realization (2/11)



**9 Gates, 21 Gate inputs**

 

**7 Gates, 18 Gate inputs**

- (1) share AB
- (2)  $A'CD + ACD = CD$ , CD covers  $A'CD$  and  $ACD$






# Multi-output Circuit Realization (3/11)

$$f_1 = \sum m(2, 3, 5, 7, 8, 9, 10, 11, 13, 15) \quad f_1 = {}_1bd + {}_2b'c + {}_3ab'$$

$$f_2 = \sum m(2, 3, 5, 6, 7, 10, 11, 14, 15) \quad f_2 = {}_4a'bd + c$$

$$f_3 = \sum m(6, 7, 8, 9, 13, 14, 15) \quad f_3 = {}_5bc + {}_6ab'c' + \begin{cases} {}_7ac'd \\ {}_7abd \end{cases}$$

10 Gates, 25 Gate inputs

   


# Multi-output Circuit Realization (4/11)

$$f_1 = {}_1a'bd + {}_2abd + {}_3ab'c' + {}_4b'c$$





$$f_2 = {}_1a'bd + {}_4b'c + {}_5bc$$

8 Gates, 23 Gate inputs

$$f_3 = {}_3ab'c' + {}_2abd + {}_5bc$$

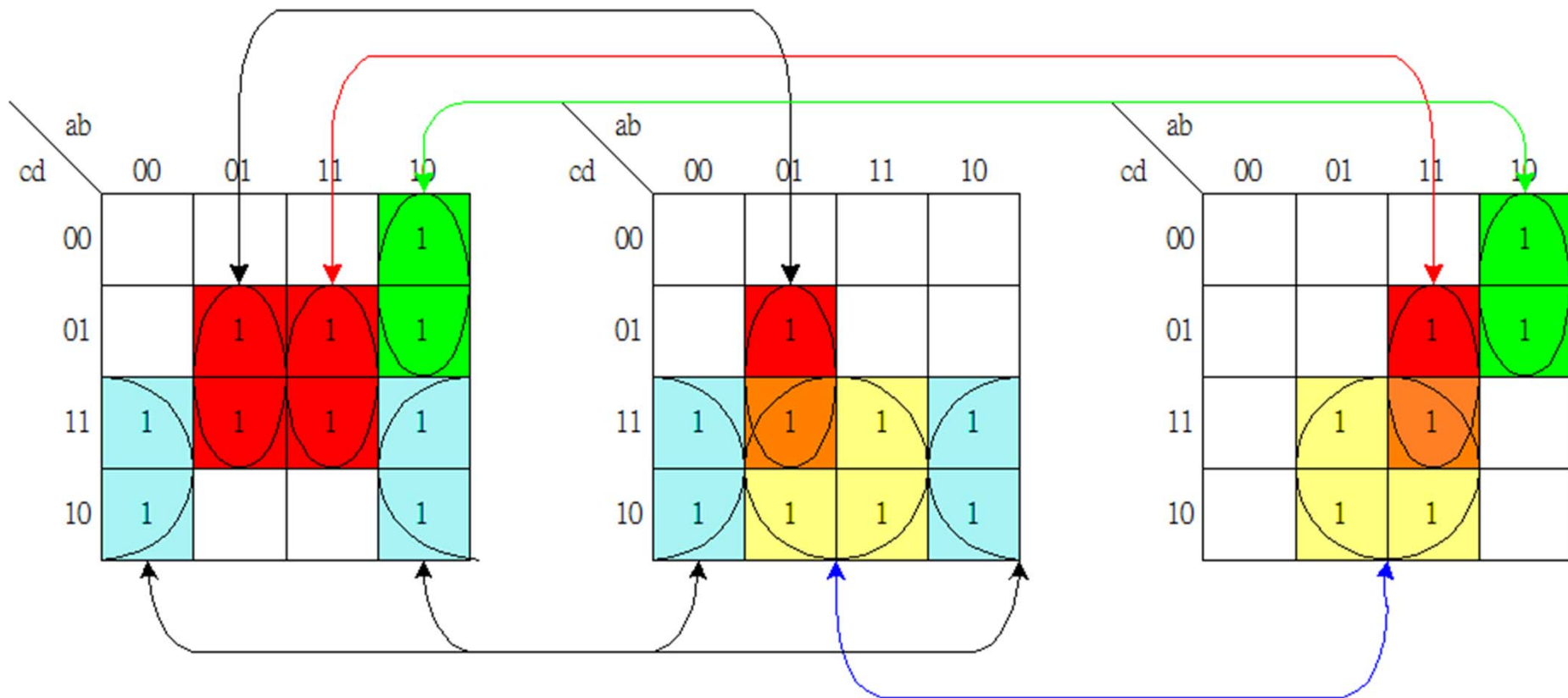
  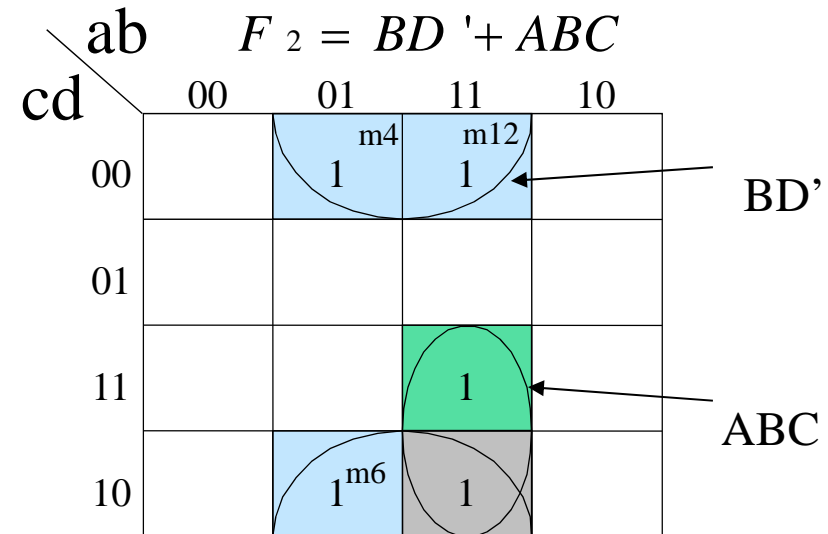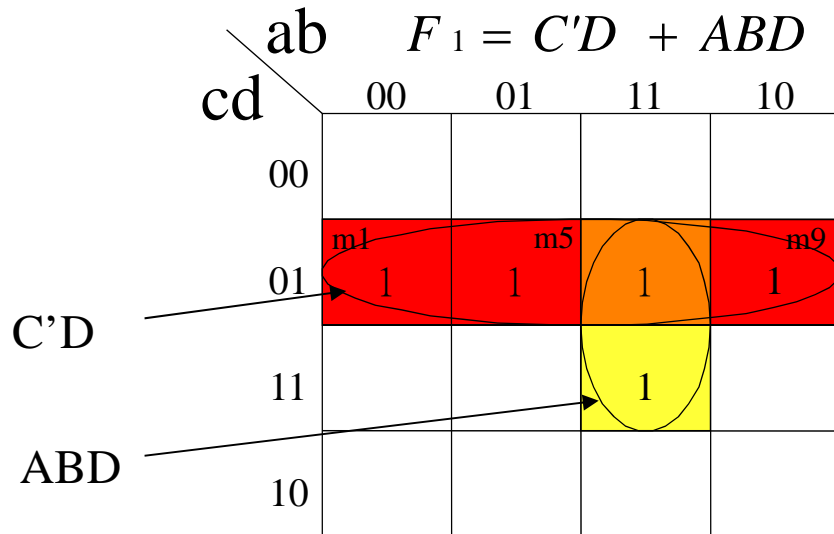
# Multi-output Circuit Realization (5/11)





# Multi-output Circuit Realization (6/11)



$$F_1 = a'c'd' + a'bc' + a'cd' + bcd'$$

$$F_2 = a'c'd' + bc'd' + a'b'c' + bcd'$$

  



8 Gates, 26 Gate inputs

# Multi-output Circuit Realization (7/11)



$$F_1 = a'd' + a'bc' + bcd'$$

$$F_2 = a'b'c' + bd'$$

  

7 Gates, 18 Gate inputs

## Multi-output Circuit Realization (8/11)

---



Determine *essential prime implicants* for multiple output function

On (5/11),  $c'd$  ( $m_1, m_5, m_9$ ),  $bd'$  ( $m_4, m_6, m_{12}$ ) are essential,  
 $abd$ ,  $abc$  are not essential.


$\because m_{15}$  is in  $abd$  of  $F_1$ , and in  $abc$  of  $F_2$ .

On (7/11),  $a'd'$  ( $m_2$ ),  $a'bc'$  ( $m_5$ ),  $a'b'c'$  ( $m_1$ ),  $bd'$  ( $m_{12}$ ) are essential.

Generally, do not split essential terms for sharing

# Multi-output Circuit Realization (9/11)

## 8-4-2-1 BCD to Excess-3 Code

 

$$w = a + bc + bd$$

$$x = bc'd' + b'd + b'c$$

$$y = c'd' + cd$$

$$z = d'$$

<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>w</i>	<i>x</i>	<i>y</i>	<i>z</i>	
0	0	0	0	0	0	1	1	0
0	0	0	1	0	1	0	0	1
0	0	1	0	0	1	0	1	2
0	0	1	1	0	1	1	0	3
0	1	0	0	0	1	1	1	4
0	1	0	1	1	0	0	0	5
0	1	1	0	1	0	0	1	6
0	1	1	1	1	0	1	0	7
1	0	0	0	1	0	1	1	8
1	0	0	1	1	1	0	0	9
1	0	1	0	X	X	X	X	
1	0	1	1	X	X	X	X	
1	1	0	0	X	X	X	X	
1	1	0	1	X	X	X	X	
1	1	1	0	X	X	X	X	
1	1	1	1	X	X	X	X	

# Multi-output Circuit Realization (10/11)

		W			
		ab	00	01	11
cd	00	0	0	X	1
	01	0	1	X	1
	11	0	1	X	X
	10	0	1	X	X

		X			
		ab	00	01	11
cd	00	0	1	X	0
	01	1	0	X	1
	11	1	0	X	X
	10	1	0	X	X

$$w = a + bc + bd$$

$$x = bc'd' + b'd + b'c$$

$$y = c'd' + cd$$

$$z = d'$$

## 3-Level Network

9 Gates

## 2-Level Network

10 Gates

		y			
		ab	00	01	11
cd	00	1	1	X	1
	01	0	0	X	0
	11	1	1	X	X
	10	0	0	X	X

		Z			
		ab	00	01	11
cd	00	1	1	X	1
	01	0	0	X	0
	11	0	0	X	X
	10	1	1	X	X

$$w = a + b(c + d)$$

$$x = bc'd' + b'(c + d)$$

$$y = c'd' + cd$$

$$z = d'$$



# Multi-output Circuit Realization (11/11)

