

Unit 11

Flip-Flops



Outline

- Introduction
- Set-Reset latch
- Gated D latch
- Edge-triggered D Flip-Flop
- Set-Reset Flip-Flop
- J-K Flip-Flop
- T Flip-Flop
- Flip-Flop with additional inputs
- Summary

Introduction (1/3)

Combinational: Output is a function of **present inputs** only


Sequential : Output is a function of both **present and previous inputs**

Circuit “**remembers**” previous history using


→ Flip-Flop (F/F): with clock input (on clock **edge**)

→ Latch : with no clock input (or on clock **level**)

 
F/F: a memory device with 1 output,
or 2 complementary outputs







Introduction (2/3)

 

 ϵ_1, ϵ_2 may be very small but still exist.



Timing

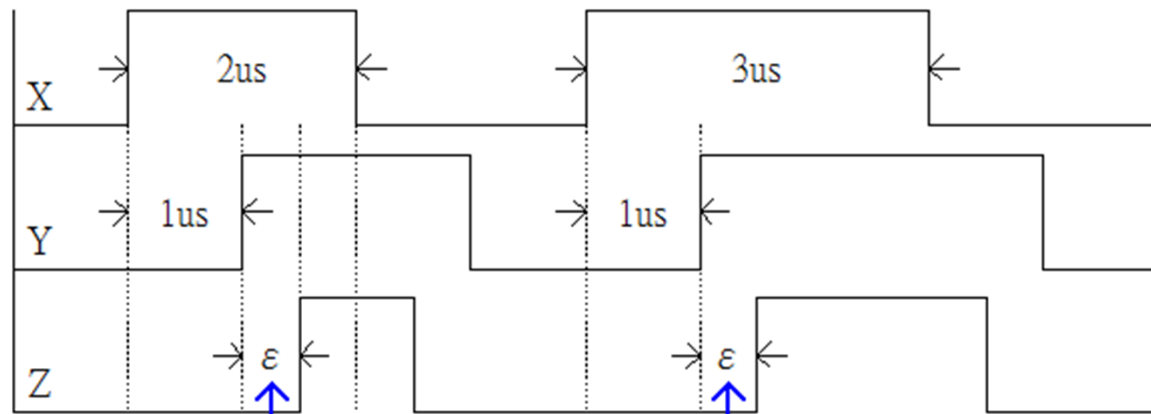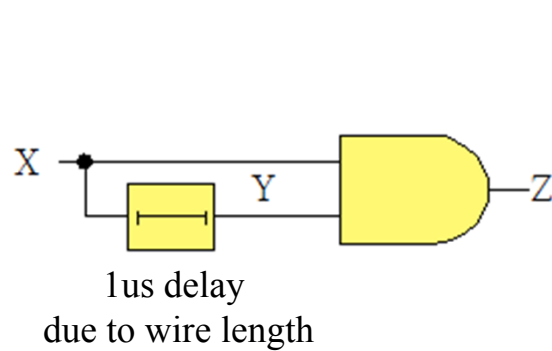  


propagation delay in AND

Introduction (3/3)

Timing in feedback network

One inversion (oscillatory)

 


(a) Inverter with feedback




(b) Oscillation at inverter output

Two inversions (stable)

 


(a)

 


(b)

Set-Reset Latch (SR Latch) (1/9)

 


$$S=R=0, Q^+=Q$$

 


$$P=Q'$$

Set-Reset Latch (SR Latch) (2/9)

 

$$S=1, R=0, Q=1, Q^+=1$$


$$P=Q'$$

 

$$S=1, R=0, Q=0, Q^+=1$$


Set: $S=1, R=0, \rightarrow Q^+=1$

Set-Reset Latch (SR Latch) (3/9)

 

$S=0, R=1, Q=0, Q^+=0$


$$P=Q'$$

 


$S=0, R=1, Q=1, Q^+=0$

Reset: $S=0, R=1, \rightarrow Q^+=0$


Set-Reset Latch (SR Latch) (4/9)

 

Original circuit


 


Restructured circuit

 


Symbol

Set-Reset Latch (SR Latch) (5/9)

 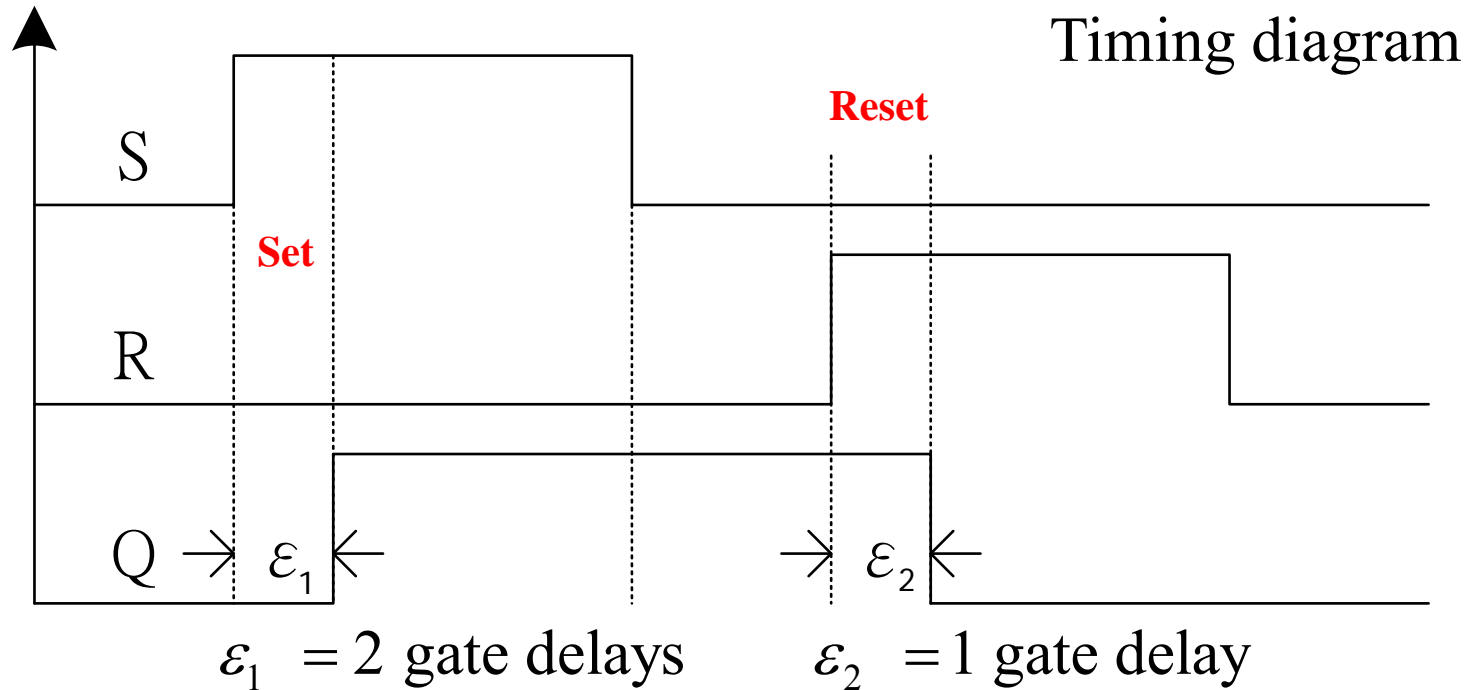

Set-Reset Latch (SR Latch) (6/9)

 

if $S = R = 1 \rightarrow 0$ at the same time,

$$\Rightarrow Q = P(Q')$$

$$= 0 \rightarrow 1 \rightarrow 0 \dots \text{ (not allowed)}$$

or $Q = 1$ first

$Q' = 1$ first (undetermined)

$S(t)$	$R(t)$	$Q(t)$	$Q(t + \varepsilon) (= Q^+(t))$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	—
1	1	1	—

} inputs not allowed

Set-Reset Latch (SR Latch) (7/9)

$$Q(t + \varepsilon) = S(t) + R'(t)Q(t) \text{ or}$$

$$\underbrace{Q^+ = S + R'Q}_{\text{characteristic equation}} \quad (\text{when } SR = 0 \text{ or } SR \neq 11)$$



		S(t)	
		0	1
Q(t)	R(t)		
	00	0	1
	01	1	1
	11	0	X
10	0	X	

S	R	Q_{n+1}
0	0	Q_n
0	1	0
1	0	1
1	1	—

Q_n : present state
 Q_{n+1} : next state

Set-Reset Latch (SR Latch) (8/9)

Alternative form using NAND gates

  

$\overline{S}(t)$	$\overline{R}(t)$	$Q(t)$	$Q(t+\varepsilon)$ ($= Q^+(t)$)
1	1	0	0
1	1	1	1
1	0	0	0
1	0	1	0
0	1	0	1
0	1	1	1
0	0	0	—
0	0	1	—

} inputs not allowed



\overline{S}	\overline{R}	Q_{n+1}
1	1	Q_n
1	0	0
0	1	1
0	0	—

Q_n : present state
 Q_{n+1} : next state

Set-Reset Latch (SR Latch) (9/9)


Usage of SR latch

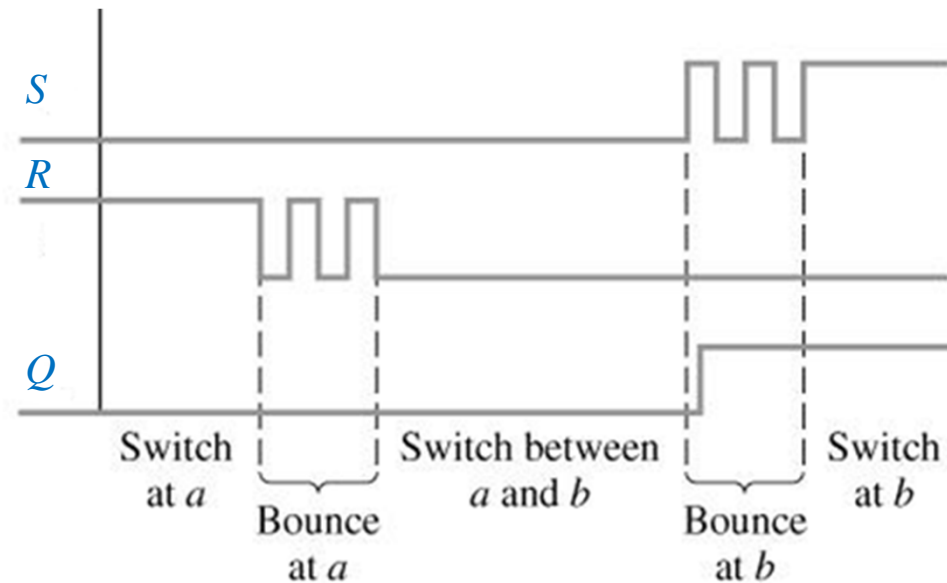 1. As a component in more complex latches and F/Fs
2. For debouncing switches




Gated D Latch


Transparent latch since $G=1, Q = D$

 

(a)

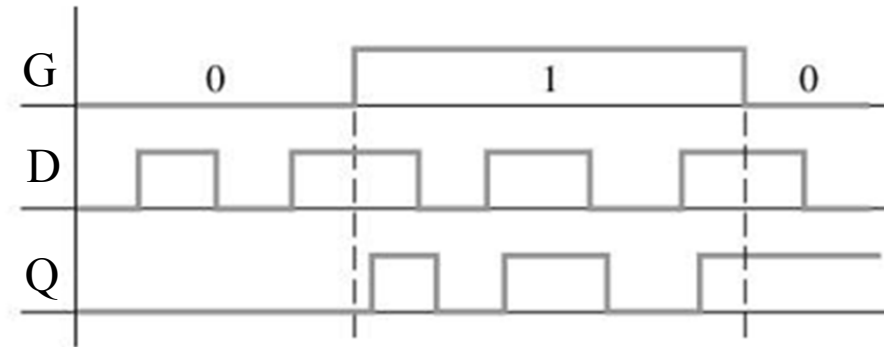

(b)

 


G	D	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1

GD		Q			
		00	01	11	10
Q	0	0	0	1	0
	1	1	1	1	0


$$Q^+ = G'Q + GD$$

Edge-Triggered D Flip-Flop (1/5)

 Similar to D latch, but changes only to *clock edge*



(a) Rising-edge trigger

 


(b) Falling-edge trigger

D	Q_n	Q_{n+1}	D	Q_n^+
0	0	0	0	0
0	1	0	1	1
1	0	1		
1	1	1	$Q^+ = D$	


Edge-Triggered D Flip-Flop (2/5)

 Timing diagram of *falling edge* triggered D F/F




Edge-Triggered D Flip-Flop (3/5)

 Timing diagram of *rising edge* triggered D F/F



 (a) Construction from two gated D latches




(b) Time analysis


Edge-Triggered D Flip-Flop (4/5)

- Determine the minimum clock period
 - Minimum clock period
= (total delay of gates) + (total delay of F/F)
- Example: suppose that
 - Propagation delay of the inverter = $2ns$,
 - Propagation delay of the D F/F = $5ns$,
 - Setup time of the D F/F = $3ns$,
 - Determine the minimum clock period of the circuit


Edge-Triggered D Flip-Flop (5/5)

 


(a) Simple flip-flop circuit

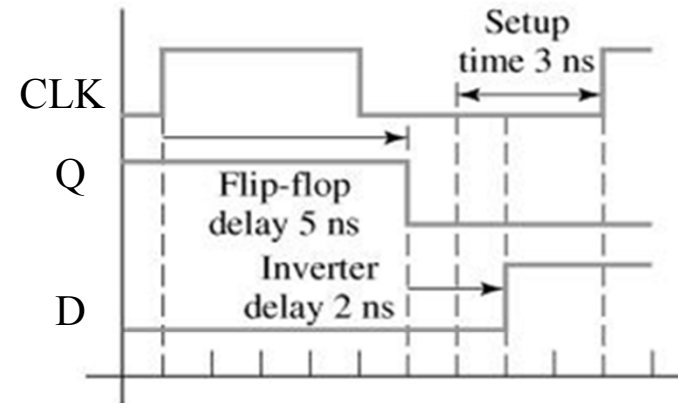

(b) Setup time not satisfied

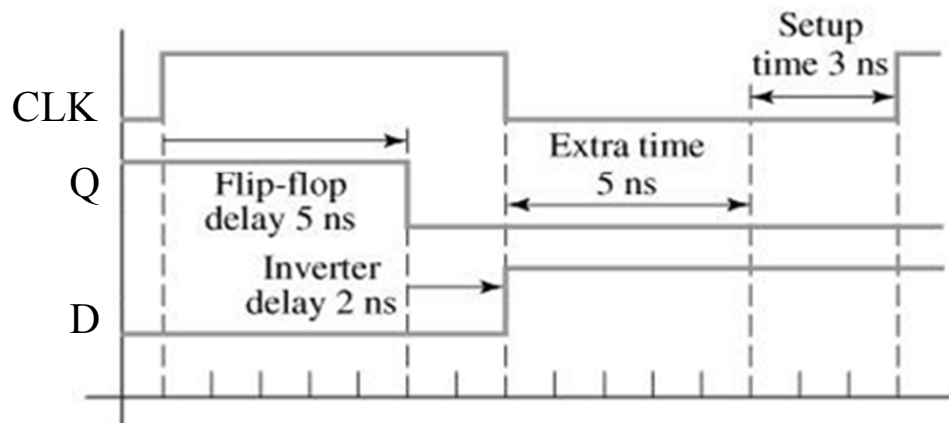


(c) Setup time satisfied

 

 (d) Minimum clock period

S-R Flip-Flop (1/2)

Similar to SR latch, but has *an extra clock input* and changes only at *clock edge*



Operation summary:

$S=R=0$ no state change

$S=1, R=0$ set Q to 1 (after active Ck edge)

$S=0, R=1$ reset Q to 0 (after active Ck edge)

$S=R=1$ not allowed

S	R	Q	Q ⁺
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	-
1	1	1	-


inputs NOT allowed

RQ \ S		0	1
		00	0
01	1	1	
11	0	X	
10	0	X	


$$Q^+ = S + R'Q$$

S-R Flip-Flop (2/2)

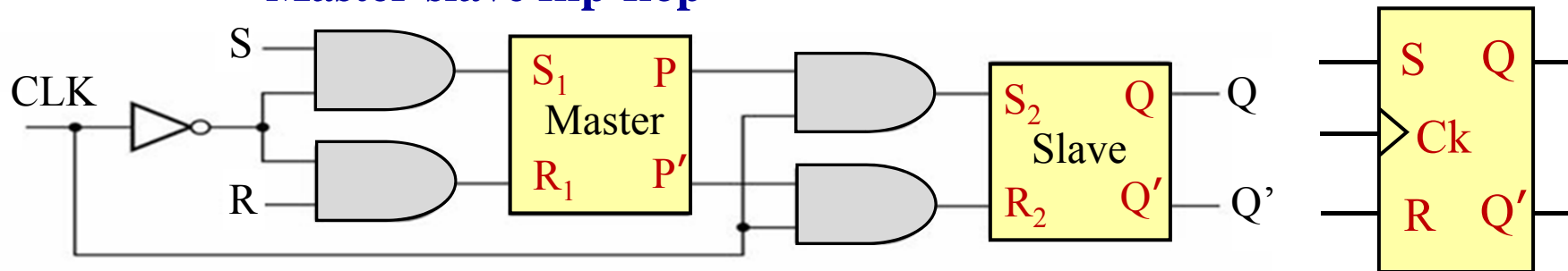- **Implementation of S-R Flip-Flop**
 - **Constructed from two S-R latches and gates**
 - **Master-slave flip-flop**



(a) Implementation with two latches

 



(b) Timing analysis

At t_5 , $S=R=0$,
the state of Q
should not change


We can solve this
problem if we only
allow the S and R
inputs to change
while the clock is
high

J-K Flip-Flop (1/3)

- Implementation of J-K Flip-Flop

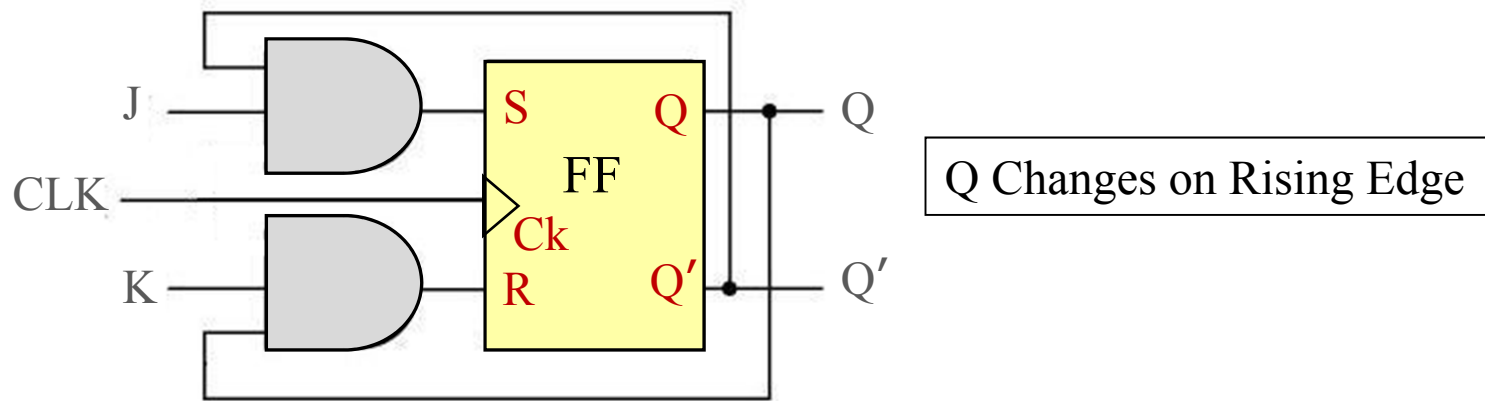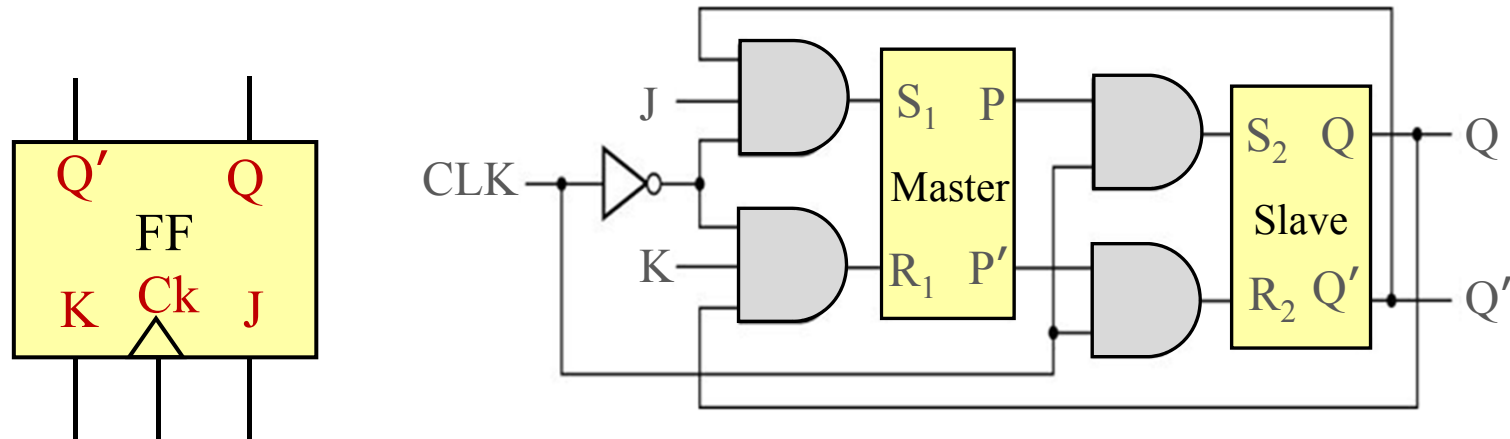

J-K Flip-Flop (2/3)

 

J	K	Q	Q^+
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

$$Q^+ = Q$$

$$Q^+ = 0$$


$$Q^+ = 1$$

$$Q^+ = Q'$$

$$Q^+ = JQ' + K'Q$$

	JK			
Q	00	01	11	10
0	0	0	1	1
1	1	0	0	1


J-K Flip-Flop (3/3)

 

J-K flip-flop timing


T Flip-Flop (1/3)

- Implementation of T (Toggle) Flip-Flop

 

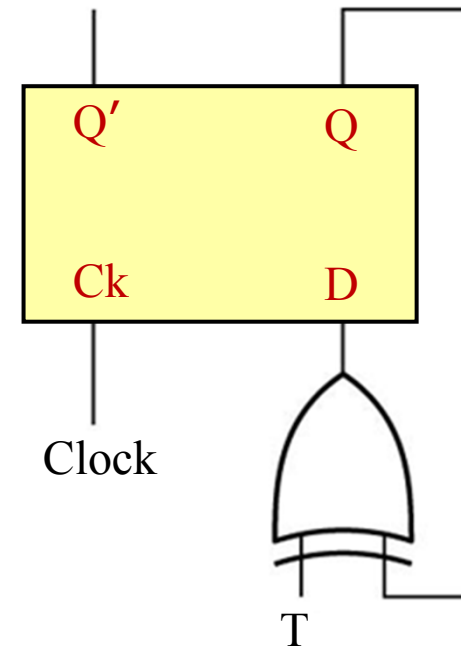(a) Conversion of J-K to T


$$\begin{aligned}
 Q^+ &= JQ' + K'Q = TQ' + T'Q \\
 &= Q \oplus T
 \end{aligned}$$



(b) Conversion of D to T

$$\begin{aligned}
 Q^+ &= Q \oplus T \\
 &= TQ' + T'Q
 \end{aligned}$$

T Flip-Flop (2/3)

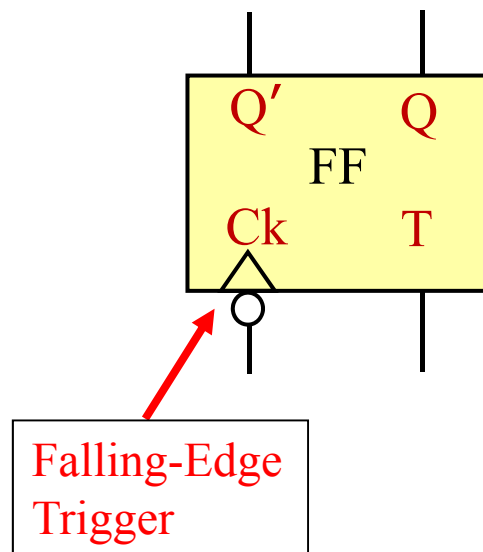


T	Q	Q^+
0	0	0
0	1	1
1	0	1
1	1	0

$$Q^+ = T'Q + TQ' = T \oplus Q$$

T Flip-Flop (3/3)


- Timing diagram for T Flip-Flop

 

Falling-Edge Trigger

Flip-Flops with Additional Inputs (1/4)


- Flip-Flop with Clear and Preset Inputs

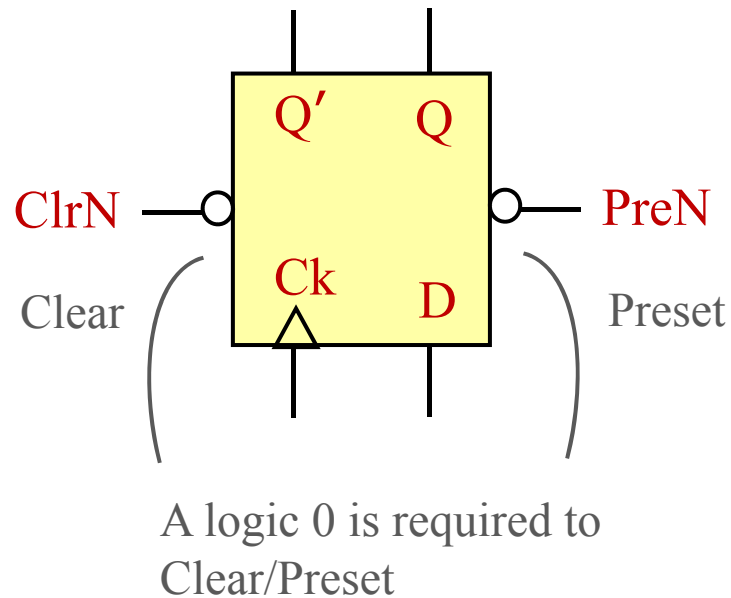

Ck	D	$PreN$	$ClrN$	Q^+
×	×	0	0	(not allowed)
×	×	0	1	1
×	×	1	0	0
↑	0	1	1	0
↑	1	1	1	1
0,1,↓	×	1	1	Q (no change)


Flip-Flops with Additional Inputs (2/4)

 - Timing diagram for rising-edge trigger D Flip-Flop with Clear and Preset



Flip-Flops with Additional Inputs (3/4)


- Gating the Clock
 - Holding existing data even though the data input to the Flip-Flop is changing
 - Two potential problems:
 - Gate delays may cause the clock to arrive at some Flip-Flops at different times than at other Flip-Flops, resulting in loss of synchronization
 - If En changes at the wrong time, the Flip-Flop may trigger due to the change in En instead of due to the change in the clock, resulting in loss of synchronization

 

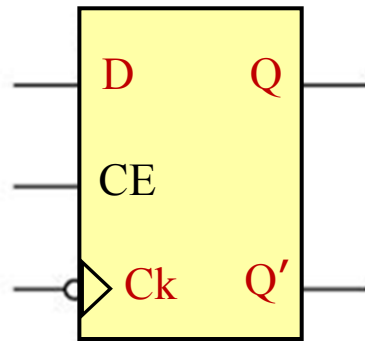
(a) Gating the clock

Flip-Flops with Additional Inputs (4/4)

- D Flip-Flop with Clock Enable (D-CE Flip-Flop)



(b) D-CE symbol

 

(c) Implementation

- $CE=0$, clock is disabled, $Q^+=Q$
- $CE=1$, the F/F acts like a normal D F/F, $Q^+=D$
- $Q^+=Q \cdot CE' + D \cdot CE$



Summary (1/3)

- The characteristic (next-state) equations for latches and F/Fs

$$Q^+ = S + R'Q \quad (SR = 0) \quad (\text{S-R Latch or Flip-Flop})$$

$$Q^+ = GD + G'Q \quad (\text{Gated D Latch})$$

$$Q^+ = D \quad (\text{D Flip-Flop})$$

$$Q^+ = D \cdot CE + Q \cdot CE' \quad (\text{D-CE Flip-Flop})$$

$$Q^+ = JQ' + K'Q \quad (\text{J-K Flip-Flop})$$

$$Q^+ = T \oplus Q = TQ' + T'Q \quad (\text{T Flip-Flop})$$

Summary (2/3)

- Q represents an initial or **present state** of the Flip-Flop, and Q^+ represents the final or **next state**
 - The interpretation of Q^+
 - For latch
 Q^+ represents the state of the latch a **short time after one of the inputs changes**
 - For Flip-Flop
 Q^+ represents the state of the Flip-Flop a **short time after the active clock edge**

Summary (3/3)

- Flip-Flops constructed from S-R Flip-Flop

