



Relationship of the Units

- Basic unit, latch and F/F (unit 11)
- **Simple** sequential circuits (unit 12)
 - Registers
 - Counters
- **Complex** sequential circuits : FSM (finite state machine)
 - Simple one: analysis, Mealy & Moore (unit 13)
 - Complex one:
 - Derive state graph and tables (unit 14)
 - Reduce state graph and tables (unit 15)

Unit 14

Derivation of State Graph and Table



Outline

- Design of a sequence detector
- More complex design problems
- Guidelines for construction of state graphs
- Alphanumeric state graph notation




Sequential Circuit Design

- Given a problem statement, to design a sequential circuit
 - 1. Construct a **state table or state graph** (unit 14)
 - Further simplification (unit 15)
 - 2. Derive F/F input equations and output equations (unit 12)

Design of a Sequence Detector (1/11)

Given problem statement \Rightarrow state graph
state table

Mealy Machine

 

Z=1 when detects X=101,
otherwise Z=0

X	=	0	0	1	1	0	1	1	0	0	1	0	1	0	1	0	0	
Z	=	0	0	0	0	0	1	0	0	0	0	0	1	0	1	0	0	
(Time	:	0	1	2	3	4	5	6	7	8	9	10	11	12	13	14	15)

Design of a Sequence Detector (2/11)

Construction of state graph


Start with a reset state S_0



S_0 : receives a “0” \Rightarrow stays at S_0 , $Z = 0$



 
receives a “1” \Rightarrow a new state S_1 , $Z = 0$



Design of a Sequence Detector (3/11)


S_1 : receives "0" $\Rightarrow S_2$, $Z = 0$

010

 

receives "1" $\Rightarrow S_1$, $Z = 0$

011

 


③

S_2 : receives "1" $\Rightarrow Z = 0$

0101

and goes back to S_1

 
Go back to S_1 since it is also the first 1 in new sequence



receives "0" $\Rightarrow S_0$, $Z = 0$

0100

 Go back to S_0 since 00 is not a part of desired sequence



④


Design of a Sequence Detector (4/11)

State table

P.S.	N.S.		Output Z	
	X = 0	X = 1	X = 0	X = 1
S ₀	S ₀	S ₁	0	0
S ₁	S ₂	S ₁	0	0
S ₂	S ₀	S ₁	0	1

State assignment

 A F/F can encode 2 states
 \Rightarrow 3 states \rightarrow 2 F/Fs (A, B)



S₀ : AB = 00
 S₁ : AB = 01
 S₂ : AB = 10

AB	A ⁺ B ⁺		Z	
	X = 0	X = 1	X = 0	X = 1
00	00	01	0	0
01	10	01	0	0
10	00	01	0	1



Design of a Sequence Detector (5/11)

Choose F/F

Use D F/F

AB	A^+B^+		D_A		D_B	
	X = 0	X = 1	X = 0	X = 1	X = 0	X = 1
00	0	0	0	0	0	1
01	1	0	1	0	0	1
10	0	0	0	0	0	1

K-Map simplification

AB \ X	0	1
00	0	0
01	1	0
11	×	×
10	0	0

$$A^+ = D_A = X'B$$

AB \ X	0	1
00	0	1
01	0	1
11	×	×
10	0	1

$$B^+ = D_B = X$$


AB \ X	0	1
00	0	0
01	0	0
11	×	×
10	0	1

$$Z = XA$$

Design of a Sequence Detector (6/11)



Circuit realization

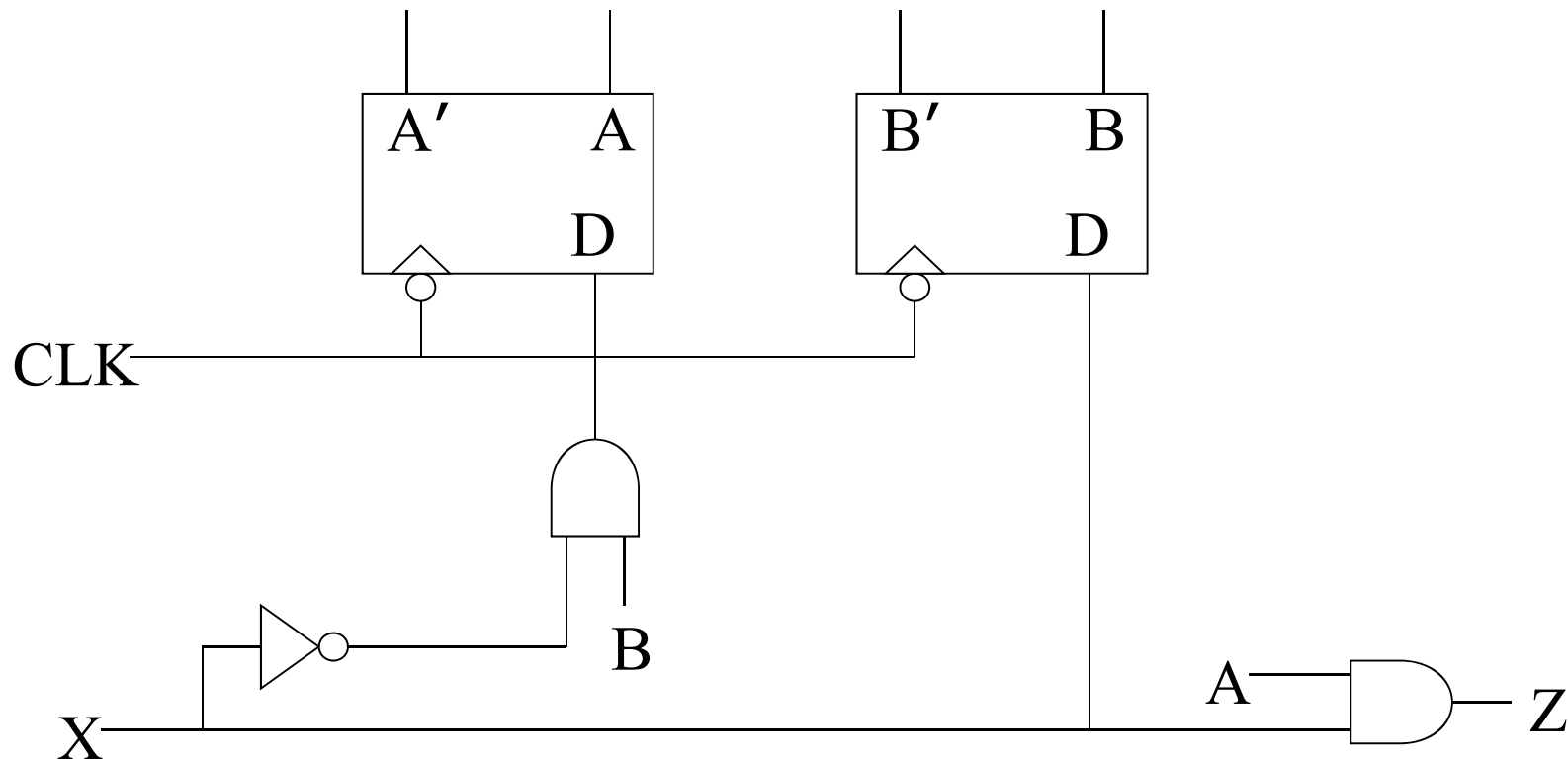

$$A^+ = D_A = X'B$$

$$B^+ = D_B = X$$


$$Z = XA$$

Design of a Sequence Detector (7/11)


Construction of state graph

Start with a reset state S_0


$S_0: Z = 0$

 

receives "0" $\Rightarrow S_0$

 

 receives "1" $\Rightarrow S_1$ ($S_1, Z = 0$)




①



Moore Machine

$S_0: Z = 0$

receives "1" $\Rightarrow S_1$

 

receives "0" $\Rightarrow S_2$ ($Z = 0$)

 
 


0110

②

010

Design of a Sequence Detector (8/11)

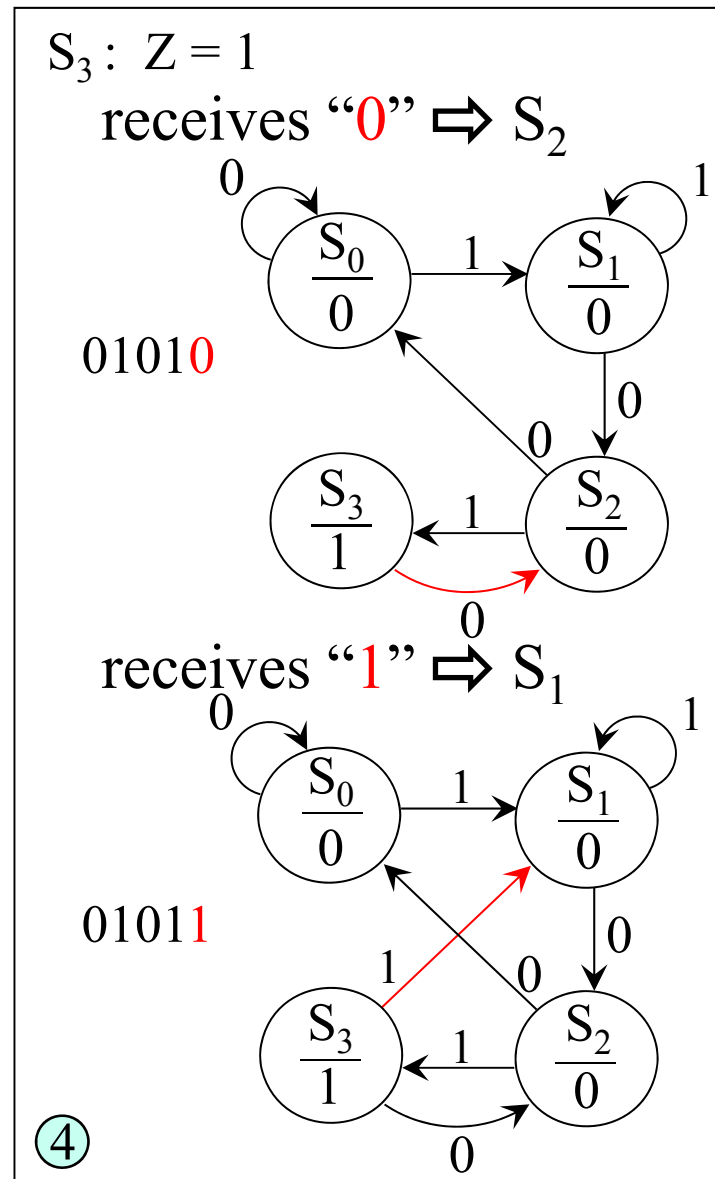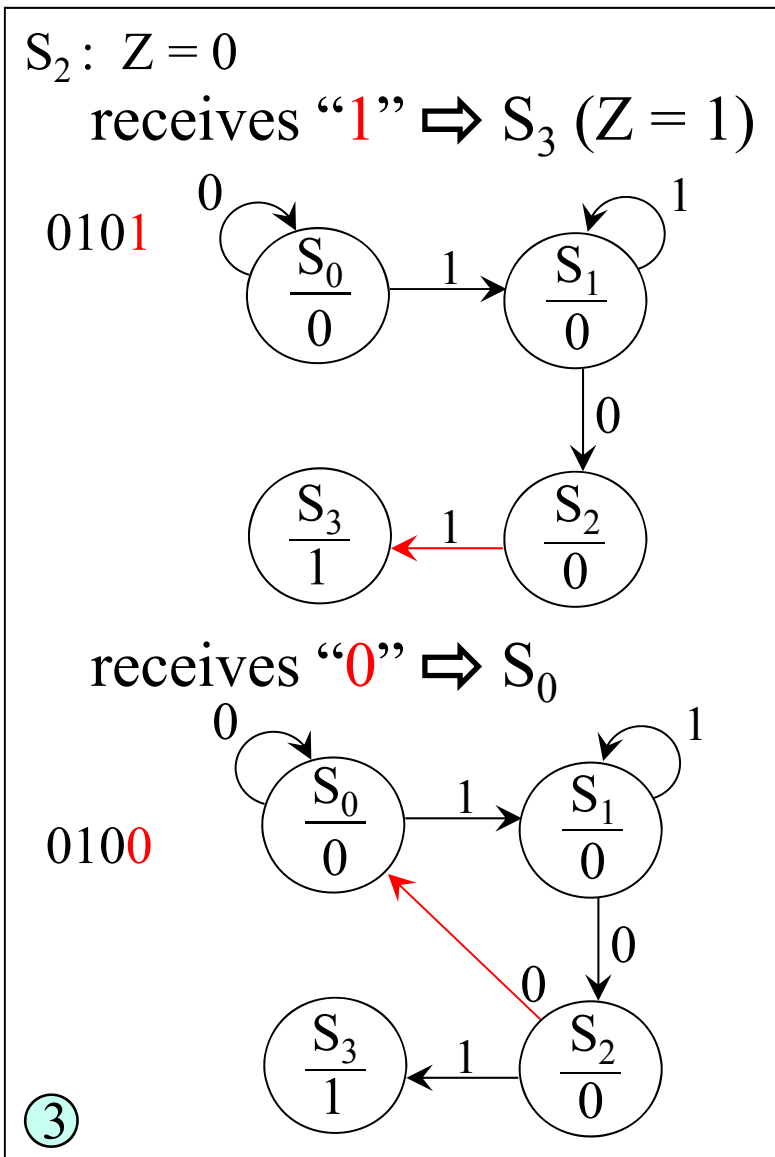


Design of a Sequence Detector (9/11)

State table

P.S.	N.S.		Present Output Z
	X = 0	X = 1	
S ₀	S ₀	S ₁	0
S ₁	S ₂	S ₁	0
S ₂	S ₀	S ₃	0
S ₃	S ₂	S ₁	1

State assignment

4 states \Rightarrow 2 F/Fs (A, B)

 

AB	A ⁺ B ⁺		Z
	X = 0	X = 1	
S ₀	00	01	0
S ₁	11	01	0
S ₂	00	10	0
S ₃	11	01	1



Design of a Sequence Detector (10/11)

Choose F/F

Use D F/F

AB	A^+B^+				D_A		D_B	
	X = 0	X = 1	X = 0	X = 1	X = 0	X = 1	X = 0	X = 1
00	0	0	0	1	0	0	0	1
01	1	1	0	1	1	0	1	1
11	0	0	1	0	0	1	0	0
10	1	1	0	1	1	0	1	1

K-Map simplification

		X	
		0	1
AB	00	0	0
	01	1	0
	11	0	1
	10	1	0

		X	
		0	1
AB	00	0	1
	01	1	1
	11	0	0
	10	1	1

		A	
		0	1
B	0	0	1
	1	0	0

$Z = AB'$

$$A^+ = D_A = X'A'B + XAB + X'AB'$$

$$B^+ = D_B = XA' + A'B + AB'$$

Design of a Sequence Detector (11/11)




Circuit realization

$$A^+ = X'A'B + XAB + X'AB'$$

$$B^+ = XA' + A'B + AB'$$

$$Z = AB'$$

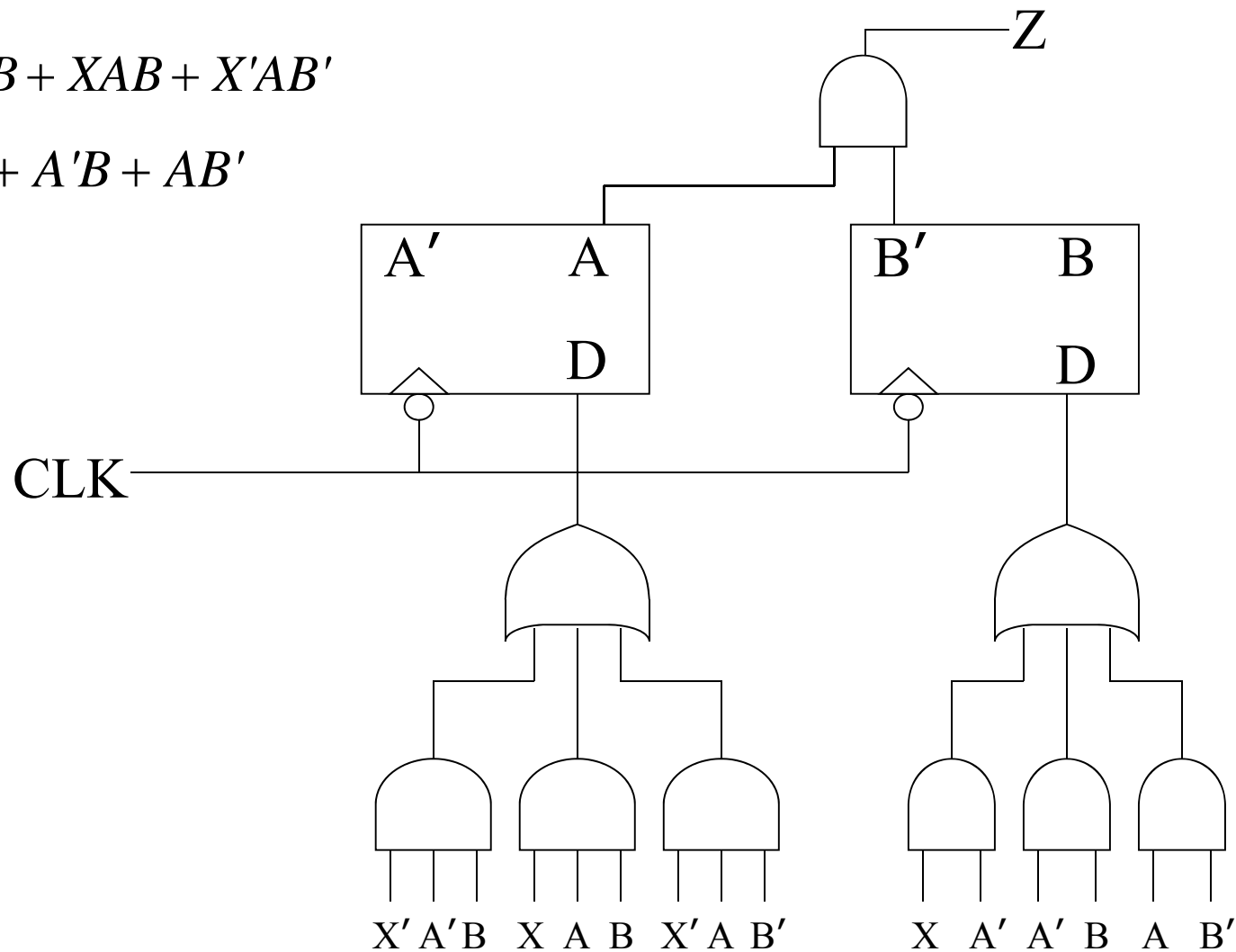


More complex Design Problems (1/11)



Mealy Machine

Sequence dectector

 


Z=1 when detects X=010 or 1001, otherwise Z=0

X	=	0	0	1	0	1	0	0	1	0	0	0	1	0	0	1	1	0
Z	=	0	0	0	1	0	1	0	1	1	0	0	0	1	0	1	0	0

More complex Design Problems (2/11)




Partial state graph construction for 010

 

<u>State</u>	<u>Sequence received</u>
S ₀	reset
S ₁	0
S ₂	01
S ₃	010

More complex Design Problems (3/11)

 Partial state graph construction for 1001




State	Sequence received
S_0	reset
S_1	0
S_2	01
S_3	010 or 10
S_4	1
S_5	100

More complex Design Problems (4/11)




Complete state graph

 

More complex Design Problems (5/11)




If state graph

 

More complex Design Problems (6/11)




Then $S_5 \rightarrow S_2$

 


More complex Design Problems (7/11)



Then $S_3 \rightarrow S_6$

 

More complex Design Problems (8/11)

 


S_3, S_5 have the same next states (S_2, S_6) and output 0 under the same input $\Rightarrow S_3 \equiv S_5$ (equivalent)


More complex Design Problems (9/11)





Moore Machine

 


 
$Z = 1$ if total number of “1” received is “odd” and at least 2 consecutive “0” received, otherwise, $Z = 0$



More complex Design Problems (10/11)

  

More complex Design Problems (11/11)

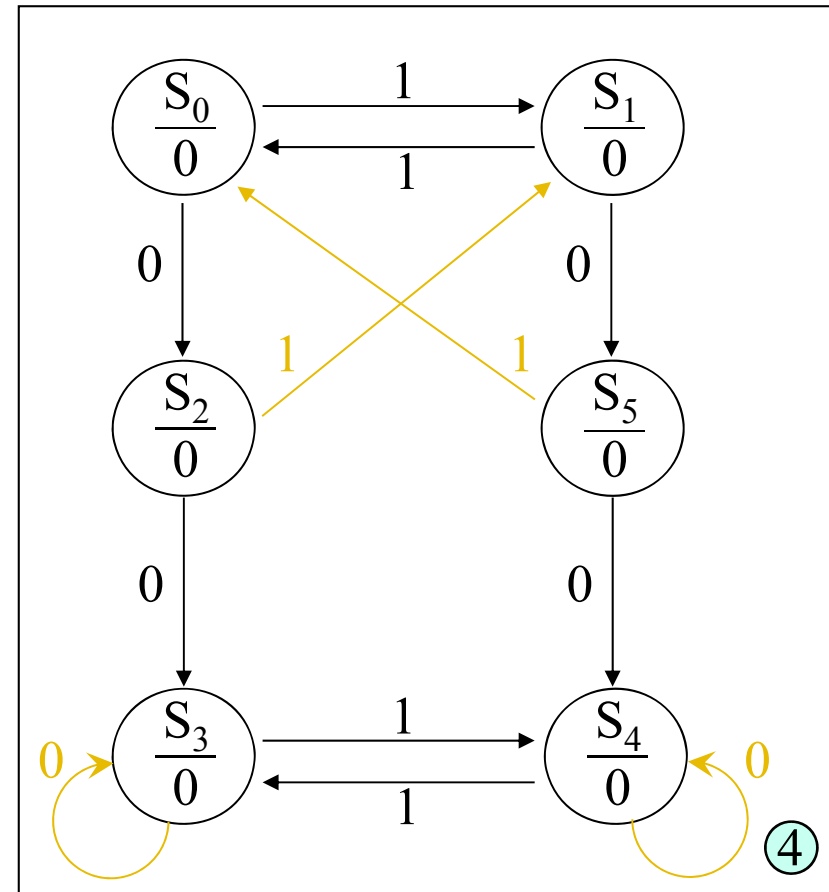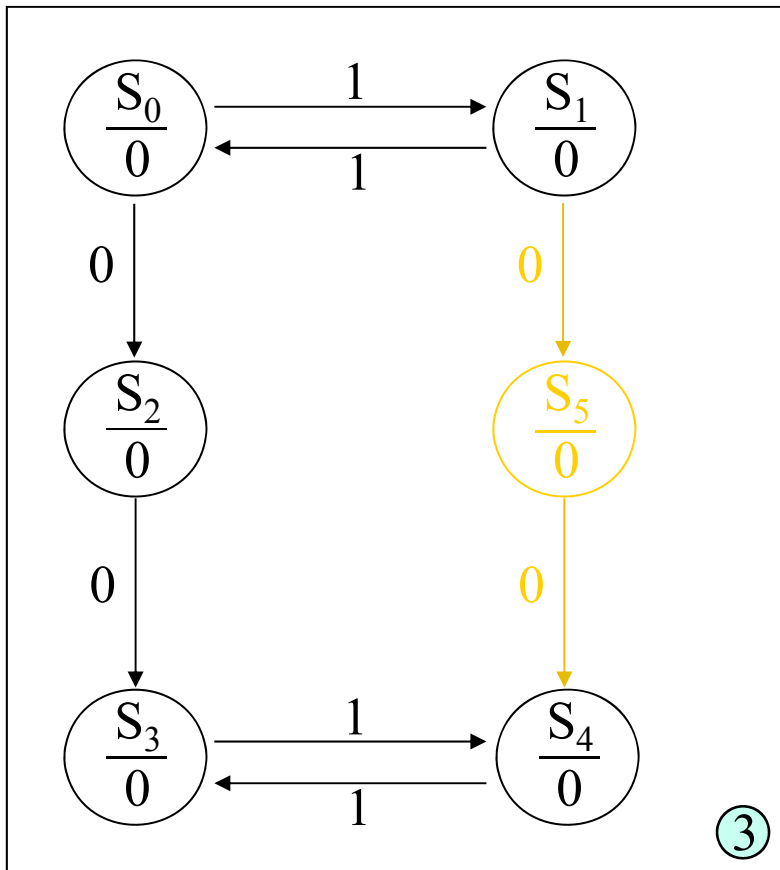

Guidelines for Construction of State Graphs (1/6)




1. Understand the problem by constructing sample sequences
2. Determine the reset state
3. Construct a partial graph to obtain “1” output
4. Construct remaining partial graphs to obtain “1” output
5. When setting up a new state, see whether it can go to an existing state
6. Complete the graph (check all input combinations !!)

Guidelines for Construction of State Graphs (2/6)



Mealy Machine

 


Check 4 consecutive inputs as a group, then reset
 $Z = 1$ when $X = 0101$ or 1001

X	=	0	1	0	1		0	0	1	0		1	0	0	1		0	1	0	0
Z	=	0	0	0	1		0	0	0	0		0	0	0	1		0	0	0	0

Hint: $Z=1$ if either 01 or 10 followed by 01

 
Guidelines for Construction of State Graphs (3/6)



Guidelines for Construction of State Graphs (4/6)




Mealy Machine

 


$Z_1=1$ if sequence **100** occurs & 010 has not occurred
 $Z_2=1$ if sequence 010 occurs,
 Note once a $Z_2 = 1$, then $Z_1 = 1$ will never occur

$X_1 =$	1	0	0	1	1	0	0	1	0	1	0	1	0	0	1	0	1	1	0	1	0	0	
$Z_1 =$	0	0	1	0	0	0	1	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0	0
$Z_2 =$	0	0	0	0	0	0	0	0	1	0	1	0	1	0	0	1	0	0	0	0	1	0	

 Guidelines for Construction of State Graphs (5/6)




(a)

 

(b)

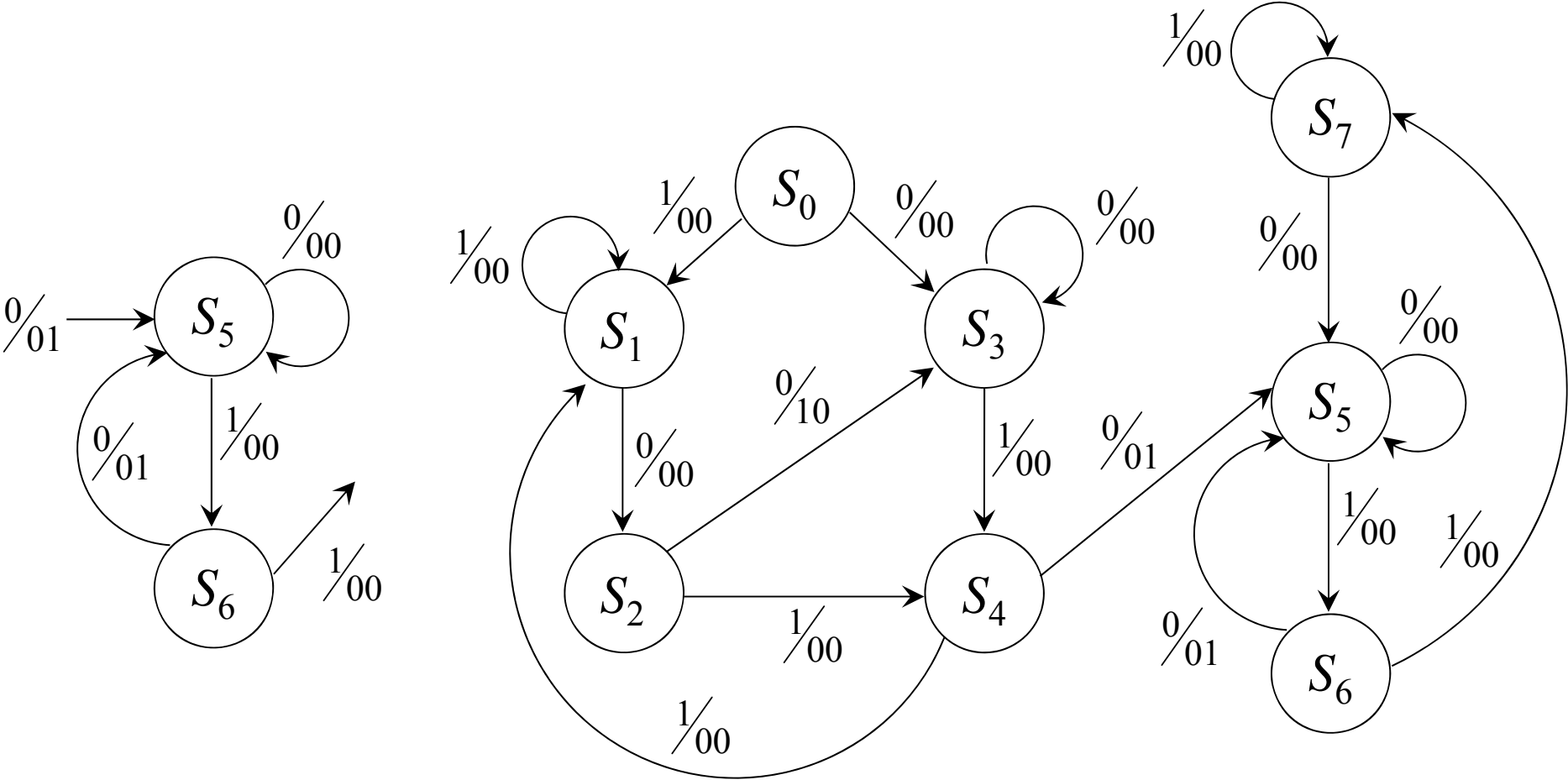Guidelines for Construction of State Graphs (6/6)




(a) Partial graph for 010

(b) Complete state graph


Alphanumeric State Graph Notation (1/2)

- When a sequential circuit has several inputs
 - Label the state graph arcs with alphanumeric input variable

F = forward **R = reverse**

 

(a)

 

(b)

↑
not complete

PS	NS				Output			
	FR =	00	01	10	11	Z ₁	Z ₂	Z ₃
S ₀		S ₀	S ₂	S ₁	S ₁	1	0	0
S ₁		S ₁	S ₀	S ₂	S ₂	0	1	0
S ₂		S ₂	S ₁	S ₀	S ₀	0	0	1

Alphanumeric State Graph Notation (2/2)


- **Property of the completely specified state graph**

- **OR** together all input labels on arcs emanating from a state, the result can be reduced to 1

$$F + F'R + F'R' = F + F' = 1$$

- **AND** together any pair of input labels on arcs emanating from a state, the result can be reduced to 0
 
$$F \cdot F'R = 0, \quad F \cdot F'R' = 0, \quad F'R \cdot F'R' = 0$$



- For large sequential circuits (4 inputs, 4 outputs)

- X_1X_4'/Z_2Z_3 1--0/0110

- $-/Z_1$ for any combination of input values,
the indicated state will occur and output $Z_1=1$