

Unit 4

Application of Boolean Algebra / Minterm and Maxterm Expansion




Outline

- Conversion of sentences to Boolean equations
- Truth table-based logic design
- Minterm and maxterm expansions
- Incompletely specified functions
- Binary adders and subtractors
- Speeding up integer additions
- Binary multiplication


Conversion of Sentences to Boolean Equations

*Ex : $\underbrace{\text{The alarm will ring}}_Z$ iff $\underbrace{\text{the power of alarm is on}}_A$ and
 $\underbrace{\text{the door is not closed}}_{B'}$ or $\underbrace{\text{it is after 6 p.m.}}_C$ and
 $\underbrace{\text{the window is not closed}}_{D'}$*

$$Z = AB' + CD'$$

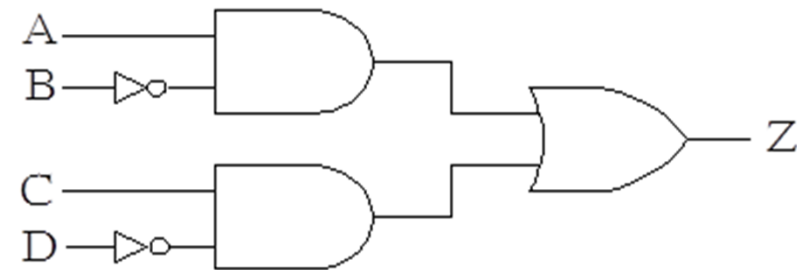

Truth Table-based Logic Design (1/2)

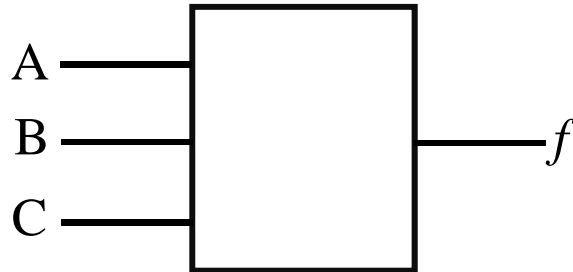

A	B	C	f	f'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0


① By “1's” function

$$f = A'BC + AB'C' + AB'C + ABC' + ABC$$

$$= A'BC + AB' + AB$$

$$= A'BC + A$$

$$= A + BC$$

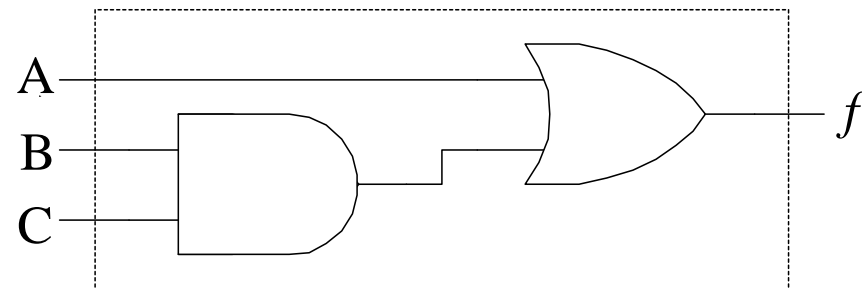

Truth Table-based Logic Design (2/2)



② By “0's” function

$$\begin{aligned} f &= (A + B + C)(A + B + C')(A + B' + C) \\ &= (A + B)(A + B' + C) = A + B(B' + C) \\ &= A + BC \end{aligned}$$

f is “0” ,

if $A = B = C = 0$

$$A = B = 0, C = 1$$

$$A = 0 = C, B = 1$$

A	B	C	f	f'
0	0	0	0	1
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	1	0
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

③ By f'

$$f' = A'B'C' + A'B'C + A'BC'$$

⇓

$$f = (A + B + C)(A + B + C')(A + B' + C)$$

Minterm & Maxterm Expansions (1/10)



Variables : $X, Y, Z \dots A, B, C \dots$

Literals : $X, X', Y, Y' \dots$

Example

$F = ABC' + A'B' + BC'$ 3 variables 7 literals

Row No.	A	B	C	Mintems			Maxterms			f	f'
0	0	0	0	$A'B'C'$	=	m_0	$A+B+C$	=	M_0	0	1
1	0	0	1	$A'B'C$	=	m_1	$A+B+C'$	=	M_1	0	1
2	0	1	0	$A'BC'$	=	m_2	$A+B'+C$	=	M_2	0	1
3	0	1	1	$A'BC$	=	m_3	$A+B'+C'$	=	M_3	1	0
4	1	0	0	$AB'C'$	=	m_4	$A'+B+C$	=	M_4	1	0
5	1	0	1	$AB'C$	=	m_5	$A'+B+C'$	=	M_5	1	0
6	1	1	0	ABC'	=	m_6	$A'+B'+C$	=	M_6	1	0
7	1	1	1	ABC	=	m_7	$A'+B'+C'$	=	M_7	1	0

Minterm & Maxterm Expansions (2/10)



$$m_i' = M_i$$

$$\begin{aligned}\Rightarrow f &= A'BC + AB'C' + AB'C + ABC' + ABC \\ &= m_3 + m_4 + m_5 + m_6 + m_7\end{aligned}$$

$$\text{or } f(A, B, C) = \sum m(3, 4, 5, 6, 7)$$

$$\text{min term} = 1 \Rightarrow f = 1$$

$$f = (A + B + C)(A + B + C')(A + B' + C) = M_0 M_1 M_2$$

$$f(A, B, C) = \prod M(0, 1, 2)$$

$$\text{maxterm} = 0 \Rightarrow f = 0$$

Minterm & Maxterm Expansions (3/10)



$$\begin{aligned} f(A, B, C) &= \sum m(3, 4, 5, 6, 7) \Rightarrow f'(A, B, C) = m_0 + m_1 + m_2 \\ (f')' &= f = (m_0 + m_1 + m_2)' = m_0' \cdot m_1' \cdot m_2' = M_0 M_1 M_2 \\ &= \prod M(0, 1, 2) \\ f' &= (m_3 + m_4 + m_5 + m_6 + m_7)' = m_3' \cdot m_4' \cdot m_5' \cdot m_6' \cdot m_7' \\ &= M_3 M_4 M_5 M_6 M_7 = \prod M(3, 4, 5, 6, 7) \end{aligned}$$

Minterm & Maxterm Expansions (4/10)



Another				Example		
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>	<i>g</i>	<i>g'</i>	
0	0	0	0	0	1	m_0
0	0	0	1	0	1	m_1
0	0	1	0	1	0	m_2
0	0	1	1	1	0	m_3
0	1	0	0	1	0	m_4
0	1	0	1	0	1	m_5
0	1	1	0	1	0	m_6
0	1	1	1	1	0	m_7
1	0	0	0	0	1	m_8
1	0	0	1	0	1	m_9
1	0	1	0	1	0	m_{10}
1	0	1	1	1	0	m_{11}
1	1	0	0	0	1	m_{12}
1	1	0	1	0	1	m_{13}
1	1	1	0	1	0	m_{14}
1	1	1	1	0	1	m_{15}

$$\begin{aligned}
 g &= \sum m(2, 3, 4, 6, 7, 10, 11, 14) \\
 \text{or } &= \prod M(0, 1, 5, 8, 9, 12, 13, 15) \\
 g' &= \sum m(0, 1, 5, 8, 9, 12, 13, 15) \\
 g &= [\sum m(0, 1, 5, 8, 9, 12, 13, 15)]' \\
 &= \prod m'(0, 1, 5, 8, 9, 12, 13, 15) \\
 &= \prod M(0, 1, 5, 8, 9, 12, 13, 15)
 \end{aligned}$$

Minterm & Maxterm Expansions (5/10)



Ex1: Find "Minterm Expansion" of $f = a'(b' + d) + acd'$

$$\begin{aligned} f &= a'b' + a'd + acd' \\ &= a'b'(c + c')(d + d') + a'd(b + b')(c + c') + acd'(b + b') \\ &= a'b'c'd' + a'b'c'd + a'b'cd' + a'b'cd + a'b'c'd + a'b'cd \\ &\quad + a'bc'd + a'bcd + abcd' + ab'cd' \\ &= 0000 + 0001 + 0010 + 0011 + 0101 + 0111 + 1110 + 1010 \\ &= \sum m(0, 1, 2, 3, 5, 7, 10, 14) \\ &\text{Find Maxterm Expansion } f = \prod M(4, 6, 8, 9, 11, 12, 13, 15) \end{aligned}$$

Ex2: Find "Maxterm Expansion" of $f = a + \bar{b}c$

Minterm & Maxterm Expansions (6/10)



Ex3: Prove $a'c + b'c' + ab = a'b' + bc + ac'$

$$\begin{aligned} LHS &= a'c(b + b') + (a + a')b'c' + ab(c + c') \\ &= m_3 + m_1 + m_4 + m_0 + m_7 + m_6 \\ &= \sum m(0, 1, 3, 4, 6, 7) \end{aligned}$$

$$\begin{aligned} RHS &= a'b'(c + c') + (a + a')bc + ac'(b + b') \\ &= m_1 + m_0 + m_7 + m_3 + m_6 + m_4 \\ &= \sum m(0, 1, 3, 4, 6, 7) \end{aligned}$$

Minterm & Maxterm Expansions (7/10)



A	B	C	F
0	0	0	a_0
0	0	1	a_1
0	1	0	a_2
0	1	1	a_3
1	0	0	a_4
1	0	1	a_5
1	1	0	a_6
1	1	1	a_7

$$F = a_0m_0 + a_1m_1 + a_2m_2 + \dots + a_7m_7 = \sum_{i=0}^7 a_i m_i \dots\dots (a)$$

If i_{th} term exists $\Rightarrow a_i = 1$

OR

$$F = (a_0 + M_0)(a_1 + M_1)(a_2 + M_2) \dots\dots (a_7 + M_7) \\ = \prod_{i=0}^7 (a_i + M_i) \dots\dots (b)$$

If i_{th} term does not exist $\Rightarrow a_i = 1$

$$\therefore (1 + M_i) = 1$$

Minterm & Maxterm Expansions (8/10)



<i>A</i>	<i>B</i>	<i>C</i>	<i>F</i>		
0	0	0	0	m_0	M_0
0	0	1	1	m_1	M_1
0	1	0	1	m_2	M_2
0	1	1	0	m_3	M_3
1	0	0	0	m_4	M_4
1	0	1	0	m_5	M_5
1	1	0	1	m_6	M_6
1	1	1	1	m_7	M_7

$$\begin{aligned} F &= 1 \cdot m_1 + 1 \cdot m_2 + 1 \cdot m_6 + 1 \cdot m_7 \\ &= (0 + M_0)(0 + M_3)(0 + M_4)(0 + M_5) \end{aligned}$$

Minterm & Maxterm Expansions (9/10)



From (b)

$$\begin{aligned} F' &= \left[\prod (a_i + M_i) \right]' = \sum (a_i + M_i)' \\ &= \sum (a_i' \cdot M_i') = \sum (a_i' \cdot m_i) \end{aligned}$$

From (a)

$$\begin{aligned} F' &= \left[\sum (a_i \cdot m_i) \right]' = \prod (a_i' + m_i') \\ &= \prod (a_i' + M_i) \end{aligned}$$

*m_i not in F , will be in F'
 M_i not in F , will be in F'*

Minterm & Maxterm Expansions (10/10)



$$\Rightarrow \text{General Form : } F = \sum_{i=0}^{2^n-1} a_i m_i = \prod_{i=0}^{2^n-1} (a_i + M_i)$$

$$F' = \sum_{i=0}^{2^n-1} a_i' m_i = \prod_{i=0}^{2^n-1} (a_i' + M_i)$$

property : $m_i m_j = 0$ if $i \neq j$ Ex: $(ABCD)(AB\bar{C}D) = 0$


$$\text{So: } f_1 = \sum_{i=0}^{2^n-1} a_i m_i \quad f_2 = \sum_{j=0}^{2^n-1} b_j m_j$$

$$\begin{aligned} f_1 f_2 &= \left(\sum_{i=0}^{2^n-1} a_i m_i \right) \left(\sum_{j=0}^{2^n-1} b_j m_j \right) = \sum_{i=0}^{2^n-1} \sum_{j=0}^{2^n-1} a_i b_j m_i m_j \\ &= \sum a_i b_i m_i \quad (i \neq j \text{ terms} = 0) \end{aligned}$$

$$\text{Ex: } f_1 = \sum m(0,2,3,5,9,11) \quad f_2 = \sum m(0,3,9,11,13,14)$$

$$f_1 f_2 = \sum m(0,3,9,11)$$

Incompletely Specified Functions (1/2)

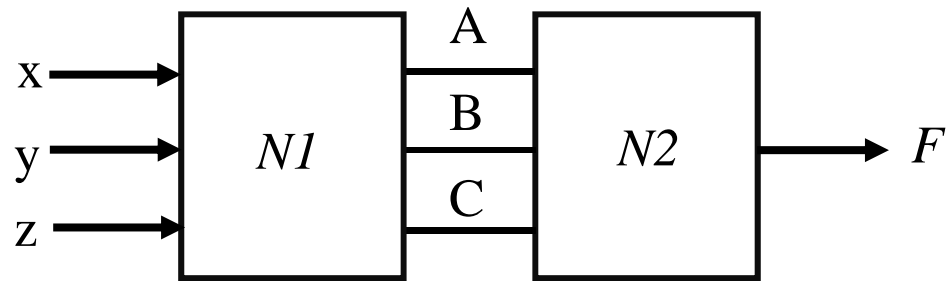

	x	y	z	A	B	C
N_1	0	0	0	0	0	0
	0	0	1	0	0	0
	0	1	0	0	1	0
	0	1	1	0	1	1
	1	0	0	1	0	0
	1	0	1	1	0	1
	1	1	0	1	0	1
	1	1	1	1	1	1

Incompletely Specified Functions (2/2)



I. $X, X=0, 0$

$$\begin{aligned} F &= A' B' C' + A' BC + ABC \\ &= A' B' C' + BC \end{aligned}$$

II. $X, X=1, 0$

$$\begin{aligned} F &= A' B' C' + A' B' C + A' BC + ABC \\ &= A' B' + BC \end{aligned}$$

III. $X, X=1, 1$


$$\begin{aligned} F &= A' B' C' + A' B' C + A' BC + ABC' + ABC \\ &= A' B' + BC + AB \end{aligned}$$

	A	B	C	F
	0	0	0	1
	0	0	1	X ← don' t care
	0	1	0	0
N_2	0	1	1	1
	1	0	0	0
	1	0	1	0
	1	1	0	X
	1	1	1	1

$$\begin{aligned} F &= \sum m(0,3,7) + \sum d(1,6) \\ \text{or} &= \prod M(2,4,5) \cdot \prod D(1,6) \end{aligned}$$

Binary Adders & Subtractors (1/9)

- **Half Adder:**

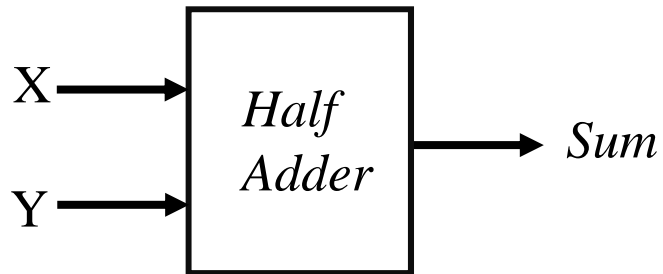


<i>X</i>	<i>Y</i>	<i>Sum</i>
0	0	0
0	1	1
1	0	1
1	1	0

$$Sum = X'Y + XY'$$

Binary Adders & Subtractors (2/9)



- **Full Adder:**

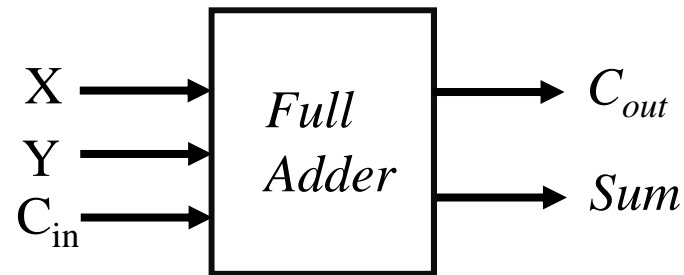

X	Y	C_{in}	C_{out}	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Binary Adders & Subtractors (3/9)



- The logic equation for the **full adder**:

$$Sum = X'Y'C_{in} + X'YC'_{in} + XY'C'_{in} + XYZ_{in}$$

$$= X'(Y'C_{in} + YC'_{in}) + X(Y'C'_{in} + YC_{in})$$

$$= X'(Y \oplus C_{in}) + X(Y \oplus C_{in})' = X \oplus Y \oplus C_{in}$$

$$C_{out} = X'YC_{in} + XY'C_{in} + XYZ'_{in} + XYZ_{in}$$


$$= (X'YC_{in} + XYZ_{in}) + (XY'C_{in} + XYZ_{in}) + (XYZ'_{in} + XYZ_{in})$$

$$= YC_{in} + XC_{in} + XY$$

Binary Adders & Subtractors (4/9)




- The logic circuit of full adder:

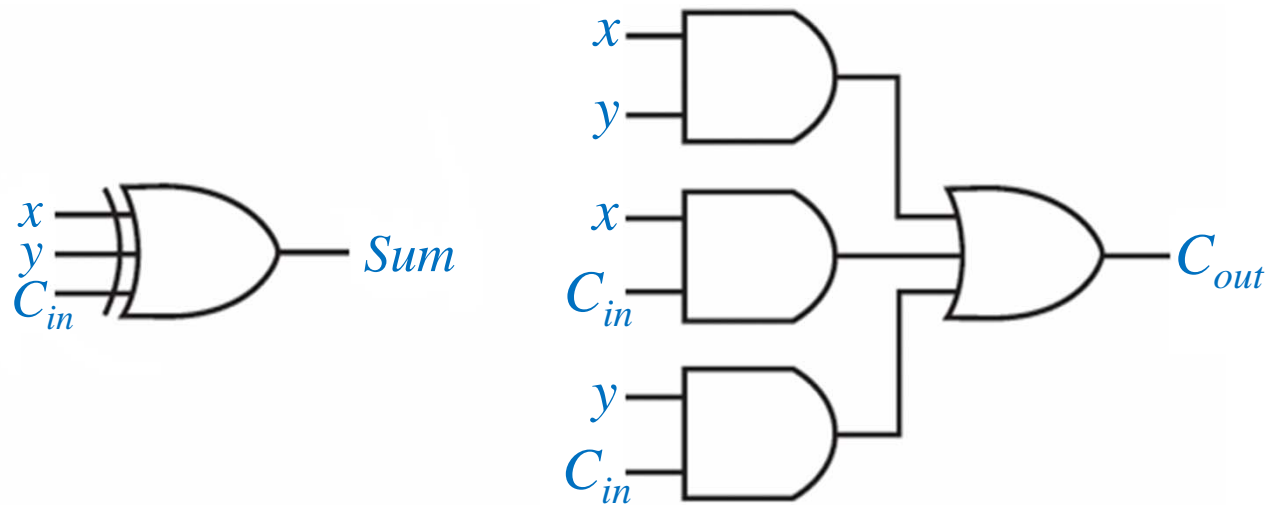

Binary Adders & Subtractors (5/9)

- **4-Bit Parallel Adder (Ripple Carry Adder)**

Adds two 4-bit unsigned binary numbers

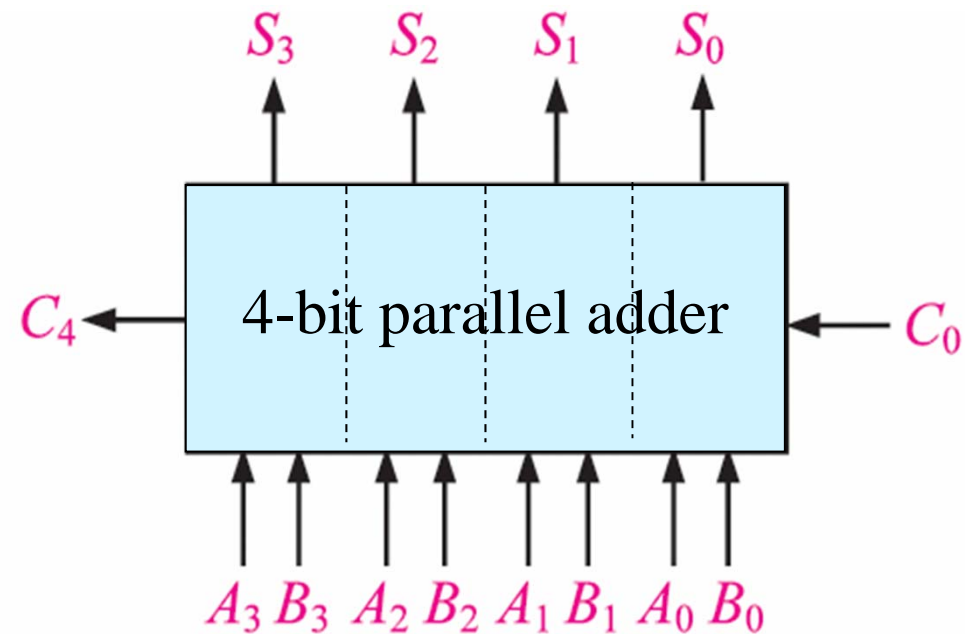


Binary Adders & Subtractors (6/9)

- 4-Bit Parallel Addder

Parallel Addder Composed of Four Full Addders

10110	(carries)
1011	
+1011	


10110	

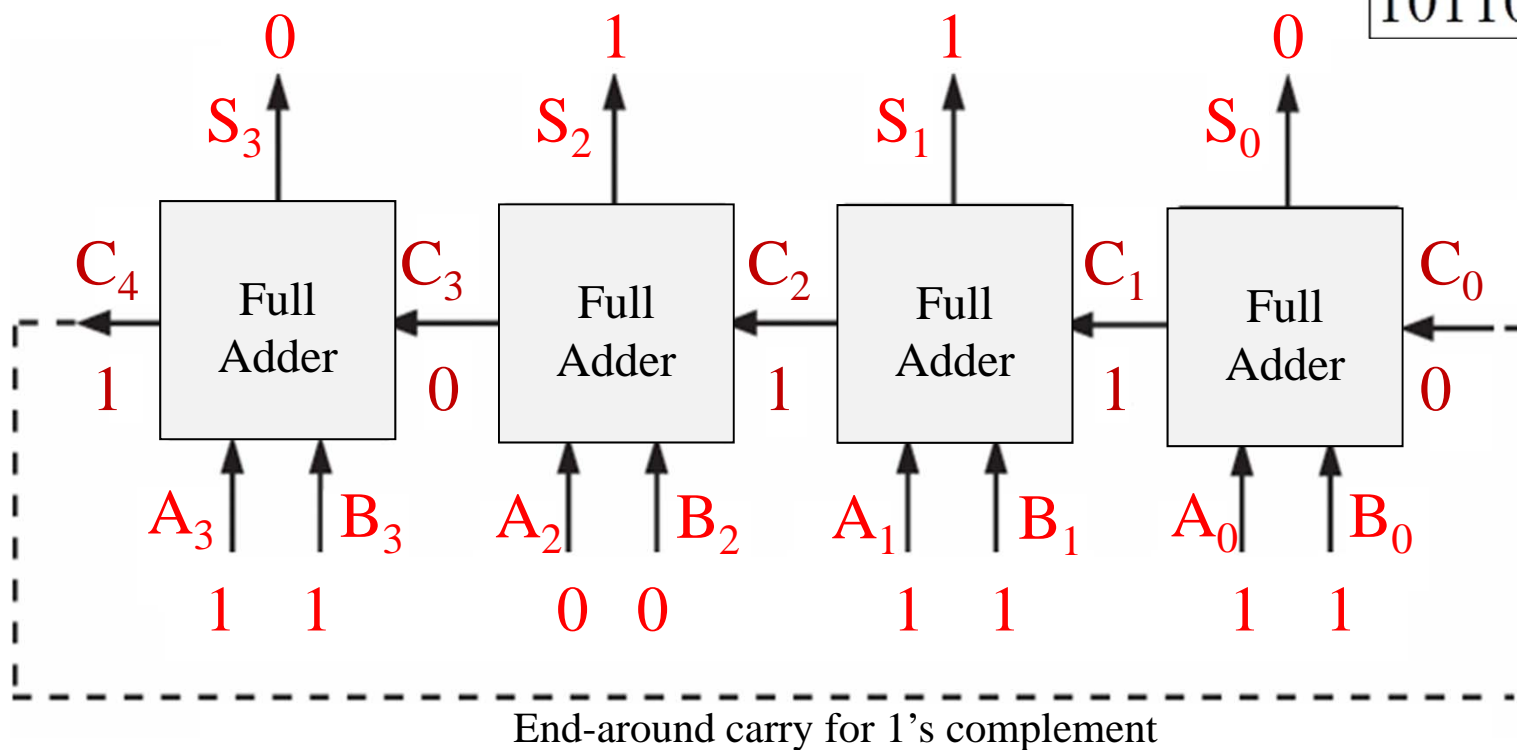

Binary Adders & Subtractors (7/9)

- Binary Subtractor Using Full Adders:

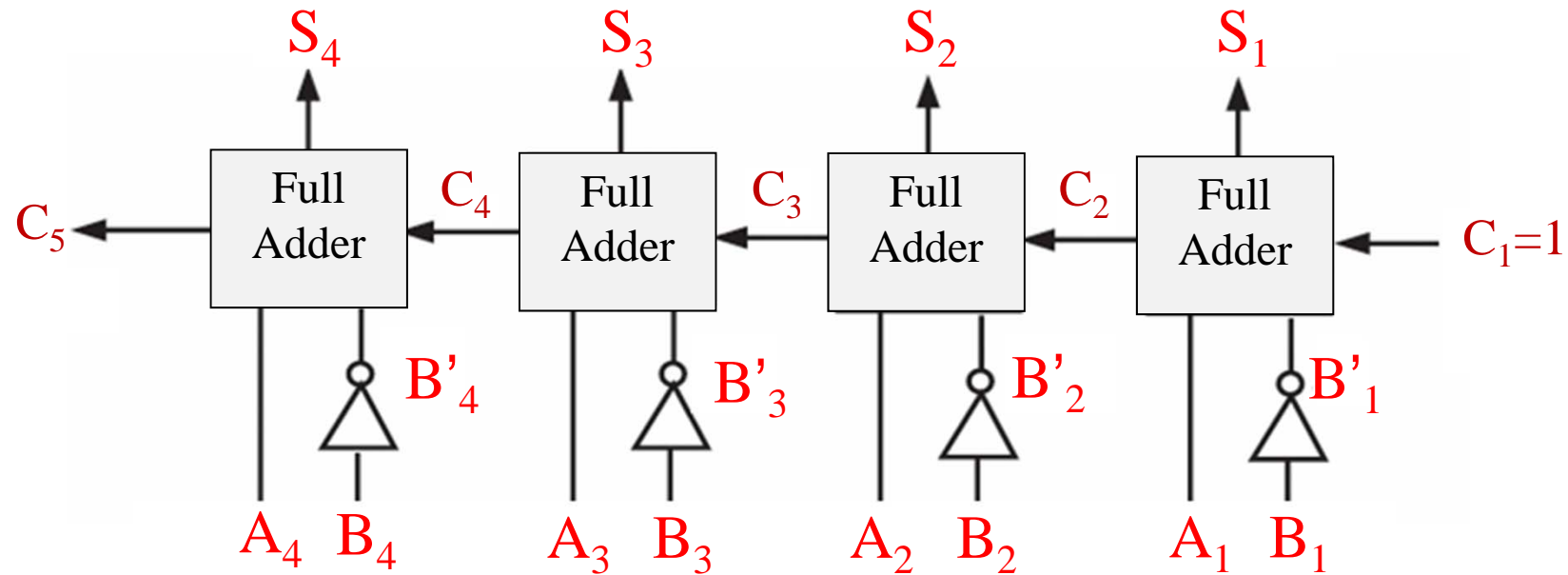Subtraction of binary numbers is most easily accomplished by adding the complement of the number to be subtracted



Binary Subtractor Using Full Adder

Binary Adders & Subtractors (8/9)



- Full Subtractor

x_i	y_i	b_i	b_{i+1}	d_i
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Truth Table for Binary Full subtracter


$$x_i=0, y_i=1, b_i=1$$

	Column i Before Borrow	Column i After Borrow
x_i	0	10
$-b_i$	-1	-1
$-y_i$	<u>-1</u>	<u>-1</u>
d_i		0 ($b_{i+1} = 1$)

Binary Adders & Subtractors (9/9)

- **Parallel Subtractor :**

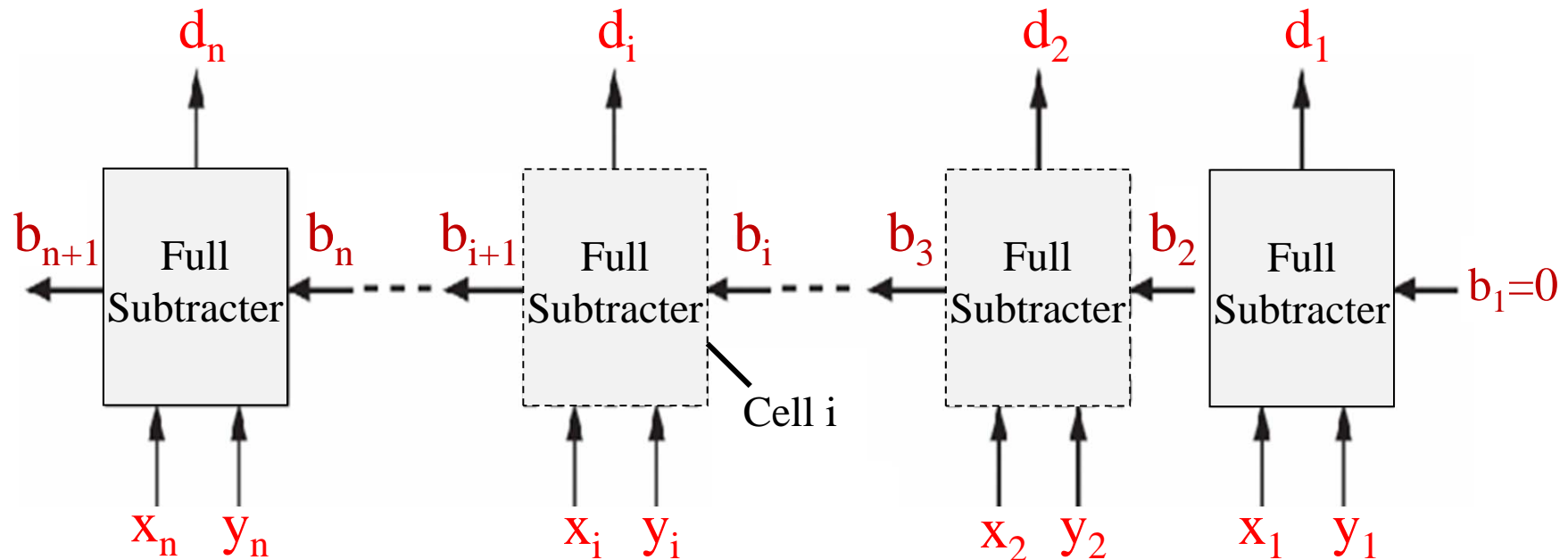Direct subtraction can be accomplished by employing a subtracter.




Speeding Up Integer Additions

- Ripple carry adder
 - Simple, regular
 - Long delay
 - Last carry out needs $2n$ delay for n -bit adder
- Carry Lookahead Adder (CLA)
- Carry Select Adder

Carry Lookahead Adder (1/4)

$$Sum = A \oplus B \oplus C_{in}$$

$$C_{out} = AB + (A + B)C_{in}$$

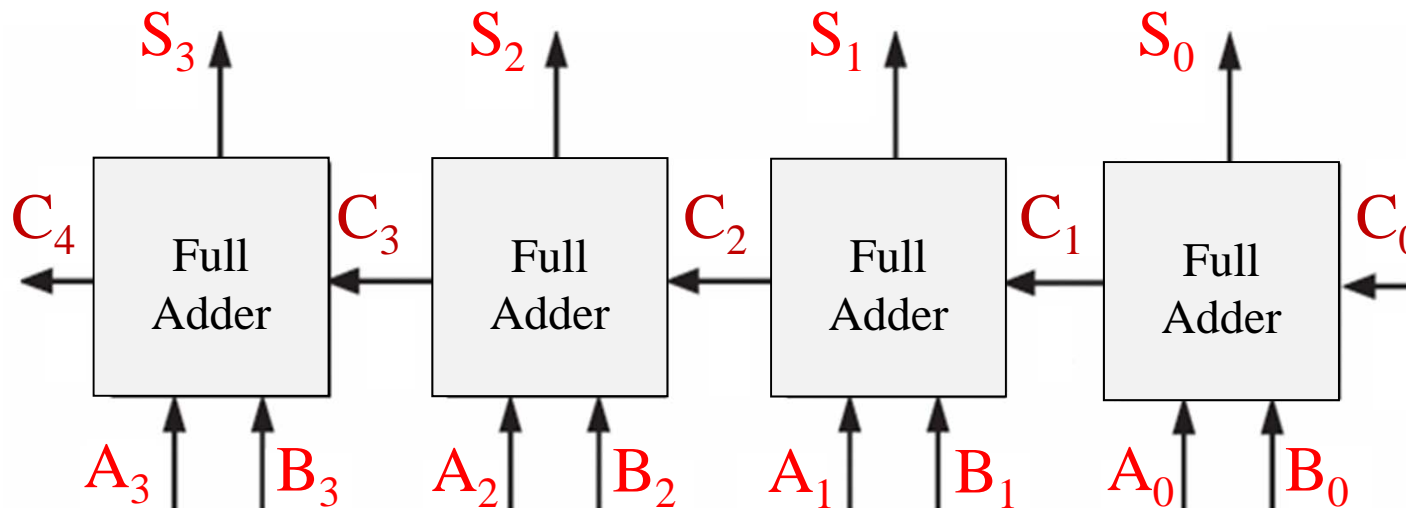

$$C_i = AB + (A + B)C_{i-1}$$

$$C_i = A_{i-1}B_{i-1} + (A_{i-1} + B_{i-1})C_{i-1}$$

Carry Lookahead Adder (2/4)

$$C_i = A_{i-1}B_{i-1} + (A_{i-1} + B_{i-1})C_{i-1}$$

$$g_{i-1} = A_{i-1}B_{i-1}; \quad \text{generate function}$$

$$p_{i-1} = A_{i-1} + B_{i-1}; \quad \text{propagate function}$$

$$C_i = g_{i-1} + p_{i-1}C_{i-1}$$

$$C_1 = g_0 + p_0C_0$$

$$C_2 = g_1 + p_1C_1 = g_1 + p_1(g_0 + p_0C_0)$$

$$= g_1 + p_1g_0 + p_1p_0C_0$$

Carry Lookahead Adder (3/4)

$$C_3 = g_2 + p_2 C_2 = g_2 + p_2 (g_1 + p_1 g_0 + p_1 p_0 C_0)$$

$$= g_2 + p_2 g_1 + p_2 p_1 g_0 + p_2 p_1 p_0 C_0$$


$$C_n = g_{n-1} + p_{n-1} g_{n-2} + p_{n-1} p_{n-2} g_{n-3} + \dots$$

$$+ p_{n-1} p_{n-2} \dots p_1 g_0 + p_{n-1} p_{n-2} \dots p_0 C_0$$

Delay of 4-bit adder: $2 + 2 \times 3 = 8$ (ripple carry adder)

$2 + 3 = 5$ (CLA)


Carry Lookahead Adder (4/4)

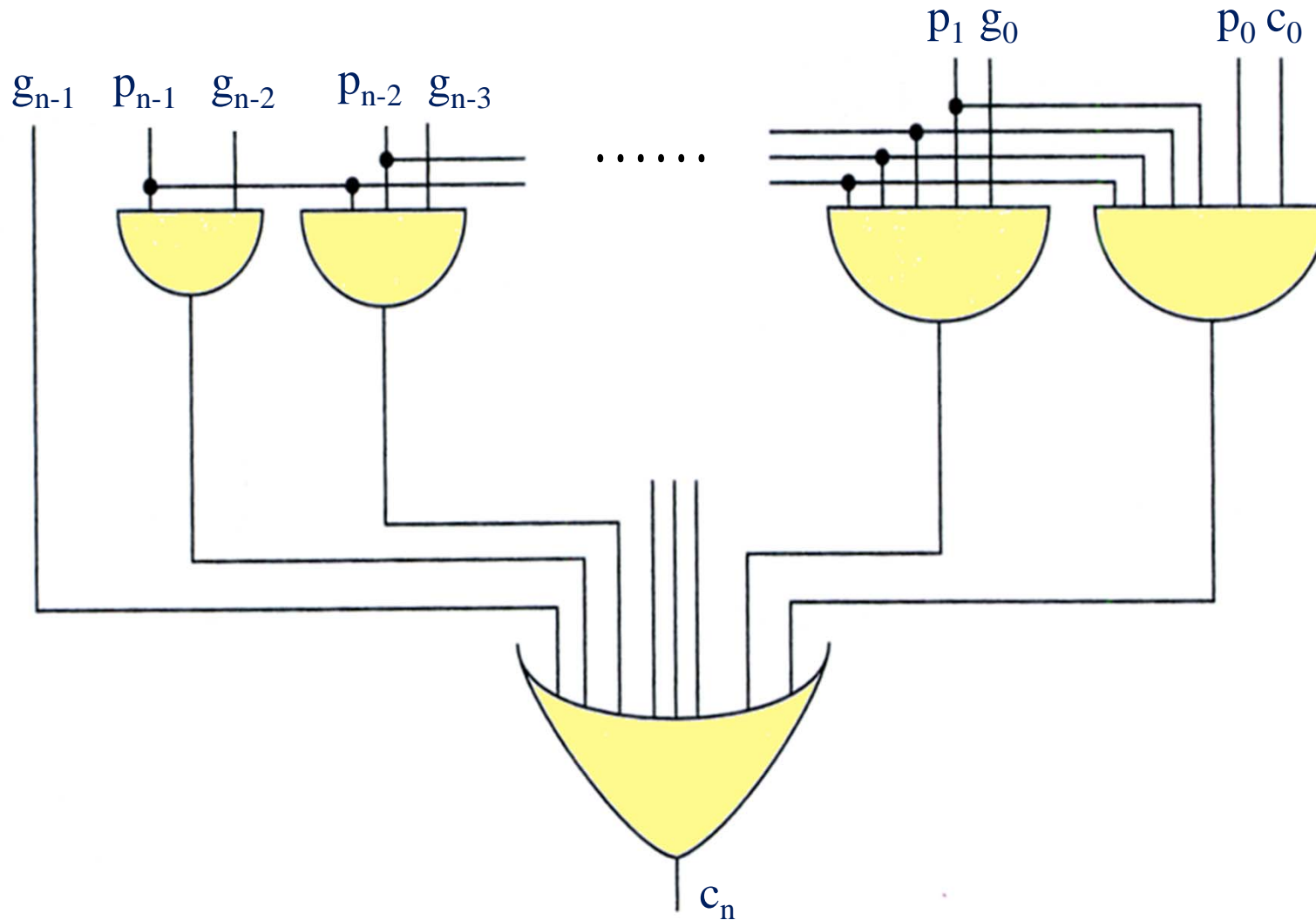


$$c_n = g_{n-1} + p_{n-1}g_{n-2} + \dots + p_{n-1}p_{n-2}\dots p_1g_0 + p_{n-1}p_{n-2}\dots p_0c_0$$

Carry Select Adder (1/2)

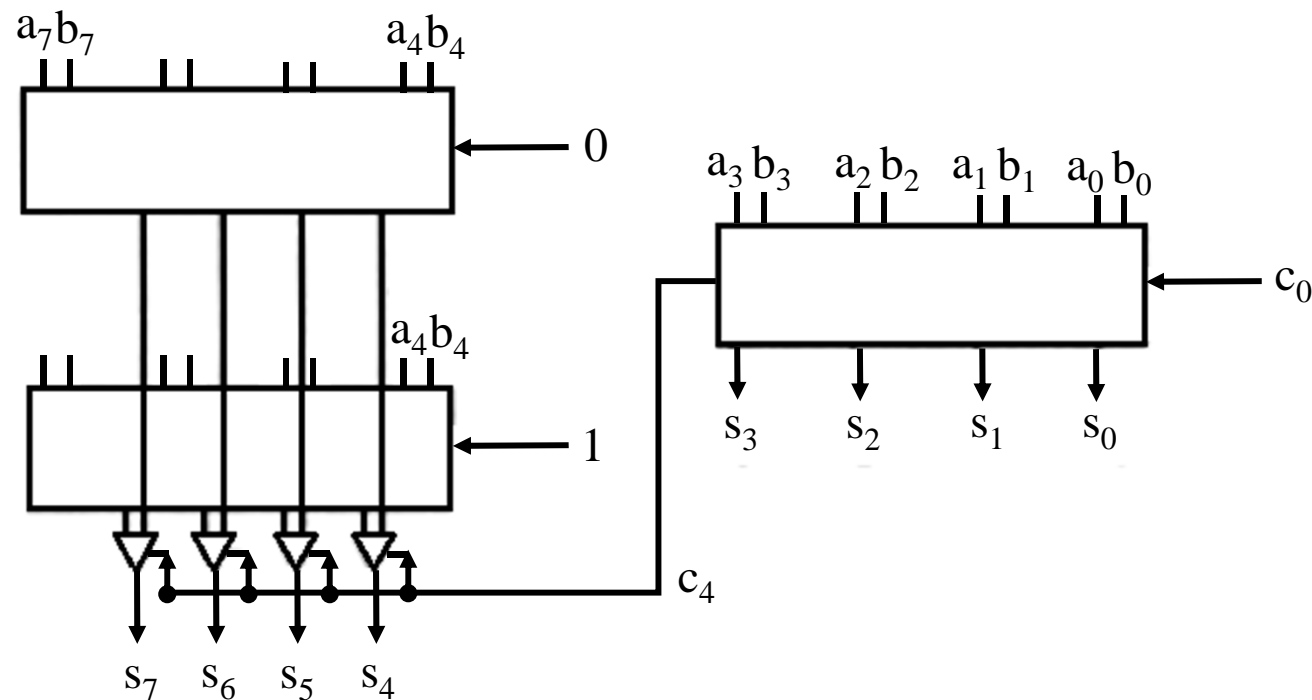- Two additions are performed in parallel
 - One assumes the carry-in is 0; the other assumes 1
- When the carry-in is finally known, the correct sum is selected (has been precomputed)



Carry Select Adder (2/2)

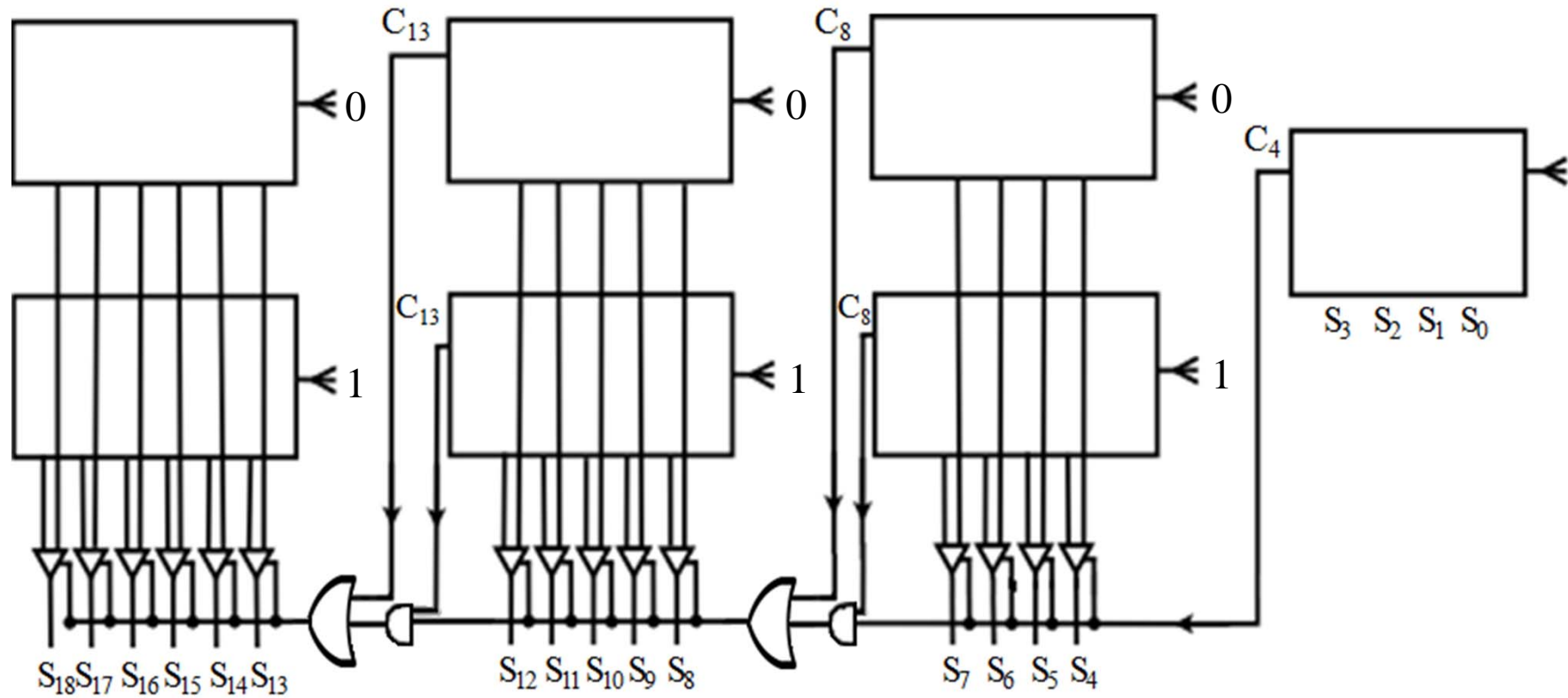

Binary Multiplication

- Performed in the same way as with decimal numbers
 - Multiplicand B, multiplier A
 - Partial product
 - Shift one bit left
 - Sum of partial products B

		B_1	B_0
	A_1	$A_1 B_1$	$A_1 B_0$
	A_0	$A_0 B_1$	$A_0 B_0$
	C_3	C_2	C_1

